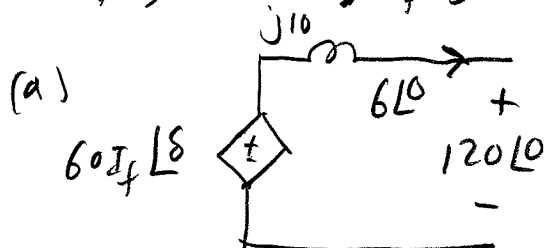


ECE431 Exam 2, Spring 2006 Solution

#1. $k_f \omega_s \times 2 = 120$, $k_f \omega_s = 60 \Omega$, $60 \times 1 = 6 X_s$, $X_s = 10 \Omega$




$$60jI_f \angle \delta = 60(90 + 120 = 120 + j60 = 134 \angle \delta)$$

$$I_f = 2.23 \text{ Amps}$$

(b) $\delta = 90^\circ$ $2100 = \frac{3 \times 120 \times 60jI_f}{10}$ $I_{f_{min}} = 0.97 \text{ Amps}$
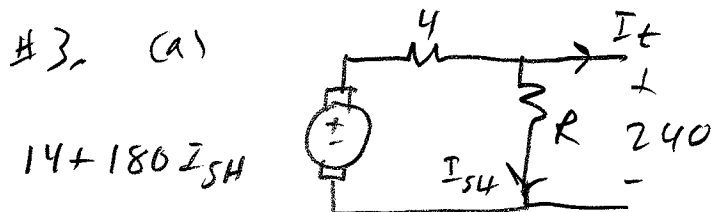
#2. $k_f \omega_s \times 3 = 120$, $k_f \omega_s = 40 \Omega$ $40 \times 2 \angle 0 = 5 X_s 5 \angle \theta + 120 \angle 0$
 $80 = 5 X_s \angle 0 + 120$ $X_s = 8 \Omega$

$$P_{max_{sudden}} = \frac{3 \times 120 \times 40 \times 2}{8} \sin 46^\circ = 2590 \text{ W}$$



$$I_t = 0 \quad 14 + 180jI_{SH} = 4I_{SH} + 240$$


$$I_{SH} = 1.28 \Omega$$

$$R = \frac{240}{1.28} = 187.5 \Omega$$

(b) $(14 + 180jI_{SH}) \frac{1050}{1100} = 4 \left(\frac{6000}{240} + I_{SH} \right) + 240$ $I_{SH} = 1.95$

$$R = \frac{240}{1.95} = 123 \Omega$$

#4. neglect R_a & $2R$

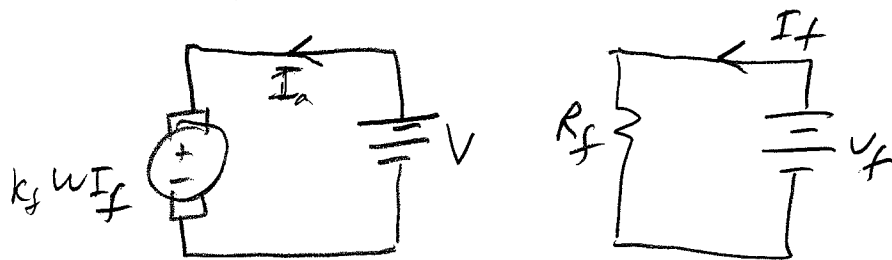

$$V = k_f \omega I_f$$

$$T = \frac{E_a I_a}{\omega} = k_f I_f I_a$$

(a) $V = \text{const}$, $I_f = \text{double} \rightarrow \omega = \text{half}$, $T = \text{const} \rightarrow I_a = \text{half}$

(b) $V = \text{half}$ $I_f = \text{const} \rightarrow \omega = \text{half}$, $T = \text{const} \rightarrow I_a = \text{constant}$

(c) $V = \text{half}$ $I_f = \text{const} \rightarrow \omega = \text{half}$, $T = 1/4 \rightarrow I_a = \text{quarter}$

(d) $V = \text{half}$ $I_f = \text{const} \rightarrow \omega = \text{half}$, $P = k_f \omega I_f I_a = \text{const} \rightarrow I_a = \text{double}$

(e) $V = \text{half}$ $I_f = \text{half} \rightarrow \omega = \text{const}$, $P = \text{const} \rightarrow I_a = \text{double}$