

ECE 431 Electric Machinery Name: _____

Test #2 April 5, 2019 NetID: _____

You may use one 2-sided sheet of your own hand-written notes as reference.

Please do all work on this test. Label any solutions that are written on the backs of pages or on any spare sheets.

Q1. (35 Points)

A 480V (line voltage), 4 pole, 60 Hz synchronous motor is drawing 30A from the grid at 0.95 lagging power factor. The motor is operating with a field current of 5A and a synchronous reactance of 10 ohms.

- a) Calculate the internal voltage and load angle.
- b) Draw the phasor diagram corresponding to this operating condition, and using dashed lines, overlay the phasor diagram when operating at unity power factor with constant excitation.
- c) Calculate the armature current, internal voltage, load angle of the synchronous motor when it is operated at unity power factor with constant excitation.

Q2. (30 Points)

A synchronous generator with a synchronous reactance of 0.5pu is supplying the grid at rated voltage, rated KVA and 0.85 lagging power factor. A fault occurs and reduces the generator output voltage to 0.5pu. After the fault is cleared, the output voltage is restored to rated voltage.

- a) Calculate the initial internal voltage(pu) and load angle.
- b) Draw the power curves for the generator and mark out the areas and angles that are required to evaluate generator stability using the equal area criterion.
- c) Write out the equations required to calculate the critical angle. DO NOT solve for the critical angle.

Q3. (35 Points)

A DC shunt motor has an armature resistance of 0.05 Ohms and a field resistance of 180 Ohms. A no-load speed of 1840 rpm is obtained when the motor is connected to a 200V supply. The motor is now connected to a load at the same voltage. Assume the load torque can be approximated by the following relationship,

$$T_{\text{load}} = 36 + 0.5\omega \text{ Nm}$$

- a) Calculate the motor speed at load
- b) Calculate the speed if the supply voltage is reduced to 120V
- c) What is the efficiency of the DC motor when operated at the new voltage?