

FINAL EXAM SOLUTION

SPRING 1991

Solution #1

$$T_{FL} = \frac{2 \times 746}{1180 \times \frac{2\pi}{60}} = 12.07 \text{ Nm}$$

$$s_{FL} = \frac{1200 - 1180}{1200} = 0.01667$$

Estimate T vs slip linear $12.07 = \frac{3 \times \left(\frac{230}{\sqrt{3}}\right)^2 \times 0.01667}{\frac{2\pi \times 60}{3} r_r'}$

$$r_r' = 0.158 \Omega \quad P_{T0} = 3 \times |I_r'|^2 r_r'$$

rotor
start

Assume $|I_r'| \approx 20 \text{ amps}$

$$P_{T0} = 696 \text{ W}$$

rotor
start

$$T_{start} = \frac{696}{\frac{2\pi \times 60}{3}} = 5.5 \text{ Nm}$$

Solution #2

O.C. test $K_f \omega_s = \frac{120}{2} = 60$


S.C. test $K_f \omega_s \times 1 = 6 \times X_s \quad X_s = 10 \Omega$

$$60 \angle 0^\circ = j10(6 \angle 0^\circ) + 120 \angle 0^\circ = 120 + j60$$

$$I_f = 2.24 \text{ A}$$

Solution #3
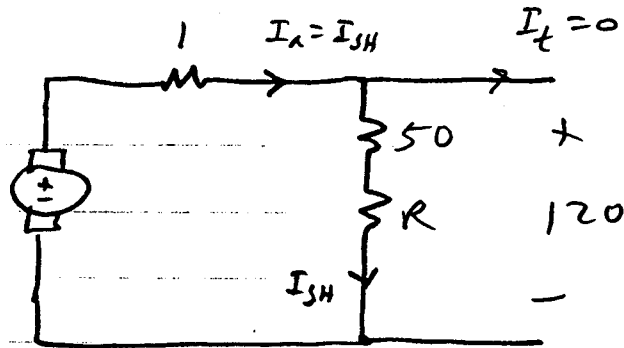
$$\frac{1200}{1160} \left(12 + \frac{500 I_{SH}}{3 + I_{SH}} \right)$$



$$\frac{1200}{1160} \left(12 + \frac{500 I_{SH}}{3 + I_{SH}} \right) = I_{SH} + 120$$

$$\frac{1200}{1160} (36 + 512 I_{SH}) = 360 + 123 I_{SH} + I_{SH}^2$$

$$I_{SH}^2 - 406.655 I_{SH} + 322.759 = 0$$

$$I_{SH} = 203.328 \pm 202.532 \quad I_{SH} = 0.8 \text{ A}$$

Neglecting r_a gives

$$\frac{1200}{1160} \left(12 + \frac{500 I}{3 + I} \right) = 120$$

$$36 + 512 I = 348 + 116 I$$

$$I = .788$$


$$R = 102$$

OR

$$V_t \approx \frac{E_a}{\omega_c} \text{ at } 1200$$

$$120 = (50 + R) 0.8$$

$$R = 100 \Omega$$

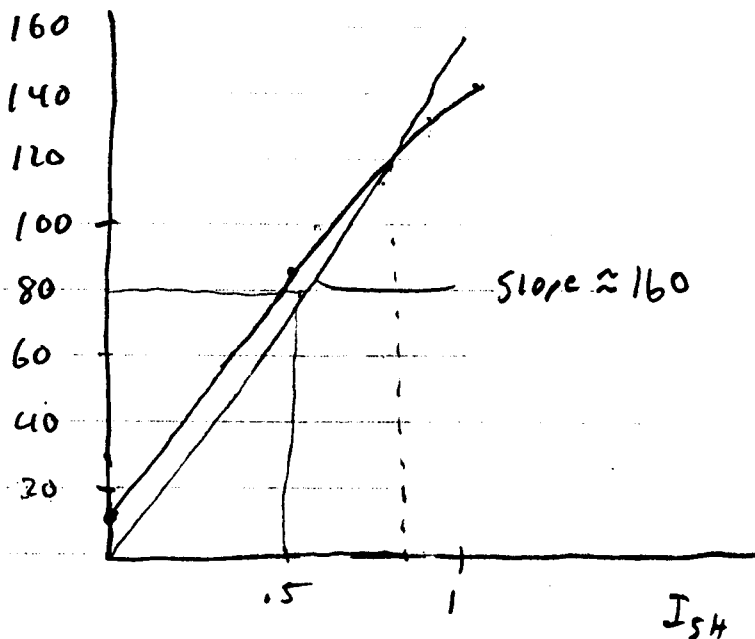

slope ≈ 160 so $R \approx 110 \Omega$

using 1160

gives with $r_a = 0$

$$36 + 512 I = 360 + 120 I$$

$$I = 0.83$$

$$R = 95$$

Solution #4

$$125 = (30 + R_1) I_{SH1}$$

$$125 = I_{a1} + 10 + 100 I_{SH1}$$

$$10 + 100 I_{SH2} = I_{a2} + 120$$

$$(30 + R_2) I_{SH2} = 120$$

$$I_{a2} = I_{SH2} + \frac{120}{10}$$



$$10 + 100 I_{SH2} = I_{SH2} + 12 + 120$$

$$I_{SH2} = 1.2323 \text{ A}$$

$$R_2 = 67.4 \Omega$$

Assume lossless power transfer

$$E_{a1} I_{a1} = E_{a2} I_{a2}$$

$$(10 + 100 I_{SH1}) I_{a1} = (10 + 123.73) (1.2323 + 12)$$

$$\overset{1763}{1763}$$

$$125 = I_{a1} + 10 + 100 I_{SH1}$$



$$(10 + 100 I_{SH1}) \underbrace{(125 - 10 - 100 I_{SH1})}_{115} = 133.23 \times 13.2323 = 1763$$

$$1150 - 1000 I_{SH1} + 11500 I_{SH1} - 10^4 I_{SH1}^2 = 1763$$

$$I_{SH1}^2 - 1.05 I_{SH1} + .06 = 0$$


$$I_{SH1} = .525 \pm .464$$

$$I_{SH1} = 0.988$$

$$I_{a1} = 16.2$$

$$R_1 = 96.5 \Omega$$

Solution #5

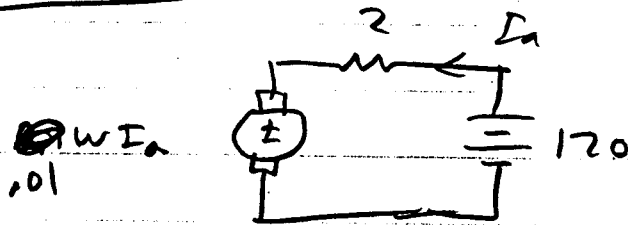

$$120 = (2 + 0.1W) I_n$$

$$I_n = \frac{120}{2 + 0.1W}$$

$$T = \frac{(0.1W I_n) I_n}{W} = 0.1 I_n^2$$

$$T = \frac{1440}{(2 + 0.1W)^2}$$

~~$W = 10 \text{ nm}$~~

~~$20 + W = 1990$~~

~~$W =$~~

~~$50 \text{ nm} \quad 1000 + 5W = 1940$~~

~~$5W = 440$~~

~~$W = 88$~~

~~$T = 20$~~


~~$44 \text{ nm} \quad W = 125$~~

Solution #6

$$\text{MMF} = N_a \cos \alpha i_a + N_b \sin \alpha i_b$$

want mmf to contain $K \cos(\alpha \pm \omega_s t + \gamma)$ and possibly other terms which do not exactly cancel out the rotation.

Hook up capacitor as follows:

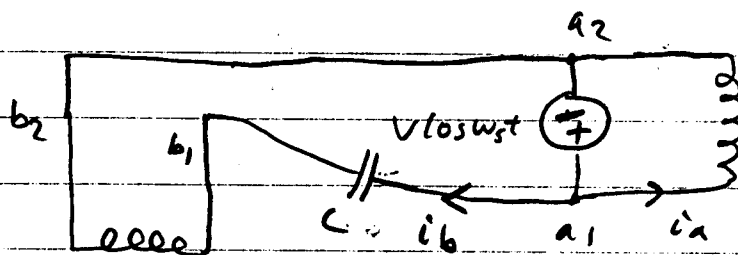

$$v_{L0s\omega_s t} = r_a i_a + L_a \frac{di_a}{dt}$$

$$v_{L0s\omega_s t} = v_c + r_b i_b + L_b \frac{di_b}{dt}$$

$$i_b = C \frac{dv_c}{dt}$$

In steady state, $v_{L0} = (r_a + jx_a) \bar{I}_a$

$$v_{L0} = (r_b + jx_b - j\frac{1}{\omega_s C}) \bar{I}_b$$

Proper C will give flexibility to design a phase shift into i_b to get rotation of the field