

## Final Exam Solution


Spring 1997

#1 (a)  $\bar{I} = \frac{100}{10 + j10} + \frac{500 - j500}{100} = 5 - j5 + 5 - j5 = 10 - j10 \text{ A}$

(b)  $\omega_{\text{ant}} \frac{100}{1/337\mu\text{C}} = j10 \quad j33,700\text{C} = j10 \quad \underline{C = 265 \mu\text{F}}$

(c)  $\bar{I} = 10 \angle 0$

#2

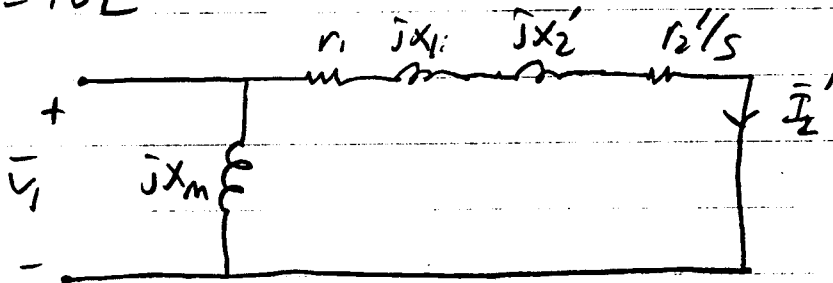

(a) 
$$T_{\text{To}} = \frac{P_{\text{To}}}{\omega_s} = \frac{3 \times |\bar{I}_2'|^2 r_2'/s}{\omega_s} = \frac{3 \times (|\bar{V}_1|^2 / ((r_1 + r_2'/s)^2 + (x_1 + x_2')^2)) r_2'/s}{\omega_s}$$

$$= \frac{3 |\bar{V}_1|^2 r_2'/s}{\omega_s [(s r_1 + r_2')^2 + s^2 (x_1 + x_2')^2]}$$

(b) maximize  $P_{\text{To}}$ ;  $\frac{r_2'}{s} = \pm \sqrt{r_1^2 + (x_1 + x_2')^2}$

$$s_{\text{max}} = \frac{\pm r_2'}{\sqrt{r_1^2 + (x_1 + x_2')^2}}$$

#3

(a) 2400V gives  $\frac{100}{5} = 20$  times rated current,  
so apply  $\frac{2400}{20} = \underline{120 \text{ V}}$


(b)  $20.833 \times 2400 = \underline{50 \text{ kVA}}$

(c)  $\frac{120}{120} \times \frac{100}{5} \times 20.833 \times \frac{20}{1} = \underline{8,333 \text{ A}}$

#4 (a)  $S = \frac{1200 - 1100}{1200} = \frac{1}{12}$   $f_r = \frac{1}{12} \times 60 = \underline{\underline{5 \text{ Hz}}}$

(b)  $T_{\text{sh}} = \frac{1700}{1200 \times \frac{2\pi}{60}} = \underline{\underline{13.5 \text{ Nm}}}$

#5

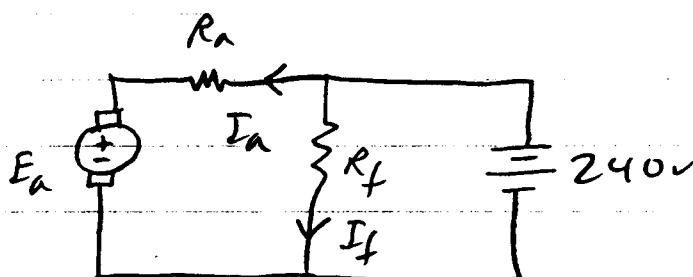

At no load  $I_a = 0$   $E_a = K_f^{sh} \times 1200 \times \frac{2\pi}{60} \times \frac{240}{R_f} = 240$

so  $\frac{K_f^{sh}}{R_f} = \frac{.025}{\pi} = .0079577$



At full load  $E_a I_a = 5 \times 746 = .0079577 \times 1000 \times \frac{2\pi}{60} \times 240 I_a$ ,

so  $I_a = 18.65 \text{ A}$

$240 = 18.65 R_a + .0079577 \times 1000 \times \frac{2\pi}{60} \times 240$

$R_a = \underline{\underline{2.14 \Omega}}$

#6

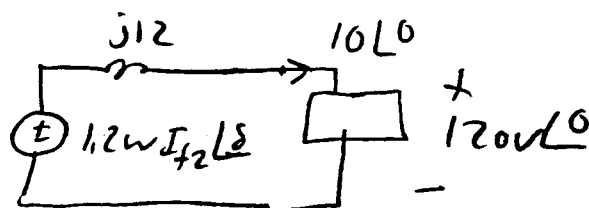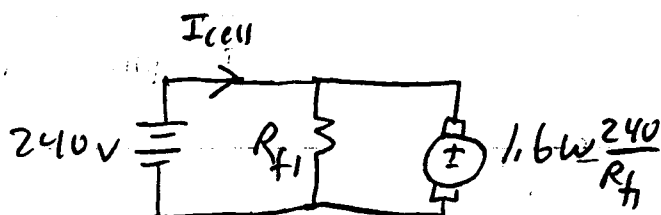

(A)  $1.2 \times \frac{377}{3} \times I_{f2} \angle \delta = j120 + 120 \angle 0 = 120 \sqrt{2} \angle 45^\circ$

$I_{f2} = 1.125 \text{ A}$

$R_{f2} = \frac{240}{1.125} - 100 = \underline{\underline{113 \Omega}}$

$1.6 \times \frac{377}{3} \times \frac{240}{R_{f1}} = 240$

$R_{f1} = \frac{1.6 \times 377}{3} - 150 = \underline{\underline{51 \Omega}}$

(b)  $P_{dc} = P_{ac} = 3 \times 120 \times 10 = 3600 \text{ W}$

$I_{cell} = \frac{3600}{240} + \frac{240}{201} + 1.125 = \underline{\underline{17.32 \text{ A}}}$