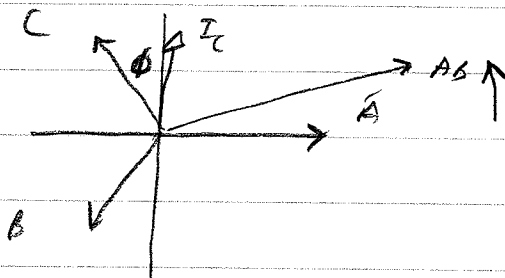


#1

$$WM = V_{LL} I_L \cos(\angle V_{AB} - \angle I_L)$$




$$= V_{LL} I_L \cos(30^\circ - (120 - \phi))$$

$$= V_{LL} I_L \cos(\phi - 90^\circ)$$

$$= V_{LL} I_L \sin \phi = Q_{3\phi} / \sqrt{3}$$

$$= \boxed{866 \text{ Watts}}$$

#2

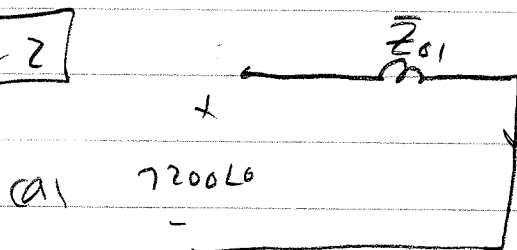


$$4000 \left(\frac{240}{7200} \right)$$

$$|Z_{01}| = 54 \Omega$$

$$Z_{\text{refers}} = \frac{7200}{50 \text{ kV} / 7200} = 1037 \Omega$$

$$|Z_{01}| = 0.052 \rightarrow \boxed{5.2\%}$$

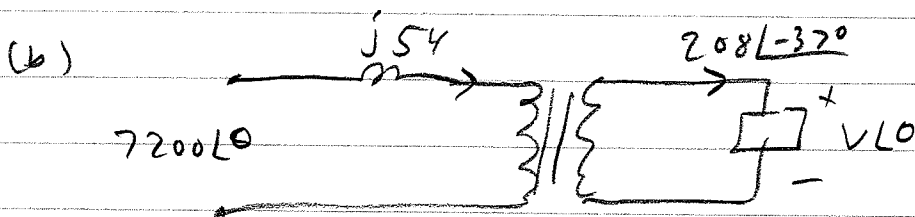

$$7200 \angle \theta = j54 \left(208 \times \frac{240}{7200} \angle -37^\circ \right) + \frac{7200}{240} V_{L0}$$


$$7200 \cos \theta = 374 \cos 53^\circ + 30V$$

$$7200 \sin \theta = 374 \sin 53^\circ \rightarrow \theta = 3^\circ$$

$$7190 = 225 + 30V$$

$$\rightarrow \boxed{V = 232V}$$

3

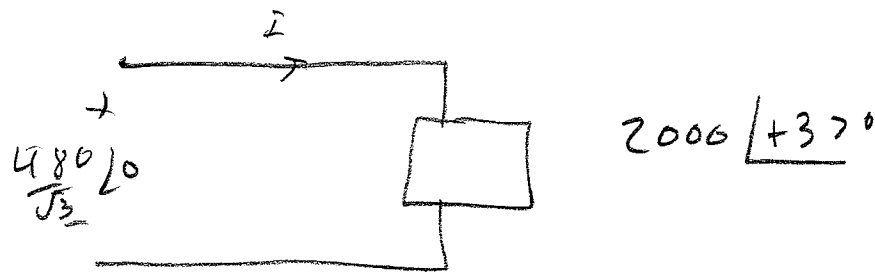

$$(a) \quad (277 \angle 0) \bar{I}^* = 2000 \angle +37^\circ \quad (|\bar{I}| = 7.22 \text{ A})$$


$$(b) \quad Q_{\text{load}} = 1204 / \text{phase} = 480^2 \times 2000 \angle C \quad (C = 14 \mu\text{F})$$

$$(c) \quad 277 \angle 0 \bar{I}^* = 2000 \times 0.8 = 1600 \quad (|\bar{I}| = 5.8 \text{ A})$$

4

$$(a) \quad f_r = 5 f_s = \frac{1700 - 1100}{1200} \times 60 = 5 \text{ Hz}$$

(b)

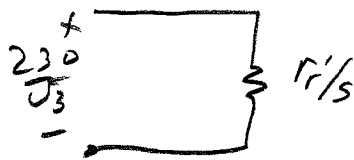


$$T = \frac{P_{\text{To Rotor}}}{\omega_{\text{sync}}} = \frac{3 \times (230 / \sqrt{3})^2 S / r_r'}{2\pi 60 / 3}$$

$$8 = \frac{52900 \left(\frac{100}{1200} \right)}{\frac{377}{3} r_r'}$$

$$r_r' = 4.38 \Omega$$

$$I_{\text{start}} = \frac{230 / \sqrt{3}}{4.38} = 30 \text{ A}$$

45

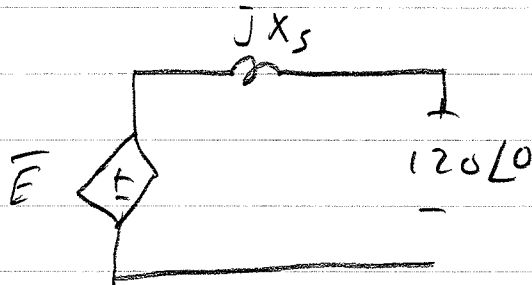

(a)

$$P_{in} = \frac{3 \times 120 \times E}{X_s} \sin(-\delta) \quad -3730 = \frac{3 \times 120 E}{X_s} \sin(-30^\circ)$$

$$\frac{E}{X_s} = 20.72$$

When $\delta = 0$, $|I| = 5 \text{ amps} \rightarrow \begin{cases} P = 0 \\ Q_{in} = 600 / \text{phase} \end{cases}$

$$Q_{in} = \frac{3 \times 120^2}{X_s} - \frac{3 \times 120 E}{X_s} \cos(-\delta) = 1800$$

$$\frac{3 \times 120^2}{X_s} - 3 \times 120 \times 20.72 = 1800$$

$$\frac{3 \times 120^2}{X_s} = 1800 + 7459$$


$$X_s = 4.66 \rightarrow E = 96.67$$

To make $\text{pf} = 1.0$ with $P = 3730$,


$$\left. \begin{aligned} 3730 &= \frac{3 \times 120 \times E}{4.66} \sin(-\delta) & E \sin(-\delta) &= 48.3 \\ 0 &= \frac{3 \times 120^2}{4.66} - \frac{3 \times 120 E}{4.66} \cos(-\delta) & E \cos(-\delta) &= 120 \end{aligned} \right\}$$

$$\frac{129}{96.67} = 1.34 \quad (34\%) \quad E^2 = 48.3^2 + 120^2 \quad E = 129$$

#6

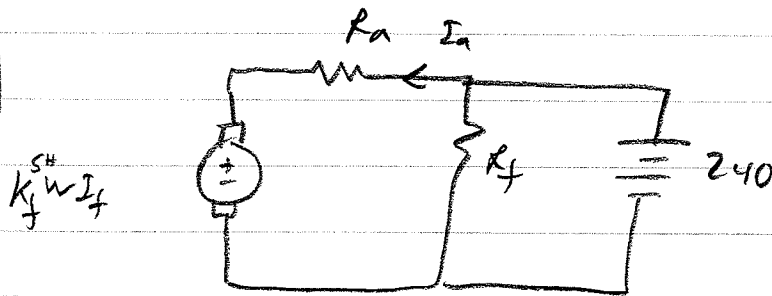

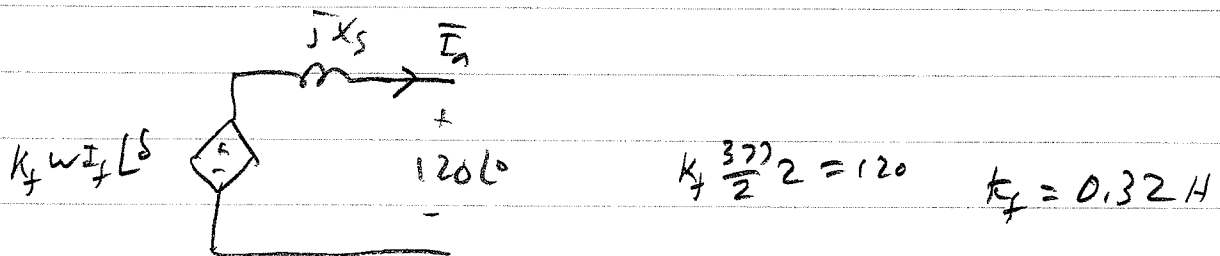no load $I_a = 0$ $K_f^{SH} \times \frac{377}{2} \times 3 = 240$ $K_f^{SH} = 0.424 H$



Full load $= 5 \times 746 = 3730 \text{ Watts}$

unity pf $\bar{I}_a = \frac{3730}{3 \times 120} \angle 0 = 10 \angle 0$

$I_f = 3$

$0.32 \times \frac{377}{2} \times 3 \angle 8 = jX_s 10 \angle 0 + 120 \angle 0$

$181 \angle 8 = 120 + j10X_s$ $10X_s = \sqrt{181^2 - 120^2} = 135$

(b)

$X_s = 13 \Omega$

(a) $0.424 \times \frac{377}{2} \times 2.8 I_a = 3730 \text{ W}$ $I_a = 16.7 \text{ A}$

$240 = 16.7 R_a + 0.424 \times \frac{377}{2} \times 2.8$

$R_a = 0.97 \Omega$