



UNIVERSITY OF  
**ILLINOIS**  
URBANA-CHAMPAIGN

# Electric Dog Teeth Cleaning Toy

Electrical & Computer Engineering

Angela Jiang (angela<sup>j4</sup>), Youhan Li (youhan<sup>l2</sup>), Yilong Zhang (yilong<sup>z3</sup>)

May 3, 2023



# OVERVIEW



Figure 1: February is Pet Dental Month  
Source: Adapted from [2]

## Objective

- Problem: Pet Dog Dental Issues

Many dog owners don't put in adequate effort to brush their dog's teeth frequent enough or thorough enough. Nowadays, at least 80% of dogs over the age of three have oral problems [1].

## Solutions

The solution we have is to develop a log-shaped electric dog toy that is capable of cleaning the dog's teeth and monitoring the cleaning.

There are two essential targets:

- Brush off plaque
- Build a habit

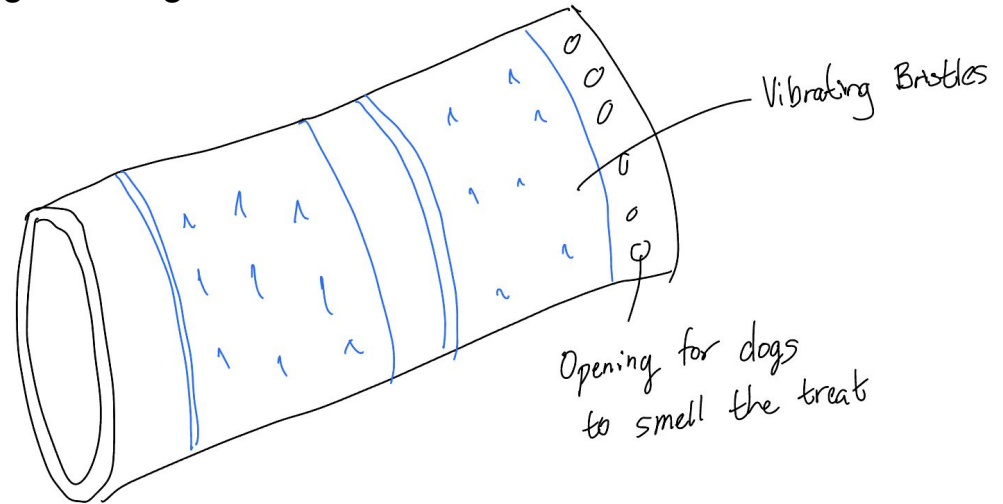


Figure 2: Original Draft

## Original Mechanical Design

- The proposed system featured a log-shaped toothbrush for the dog to bite on.
- A mount was conceived so that the system can be safely stored.
- A ramp was present for the treat dispenser.

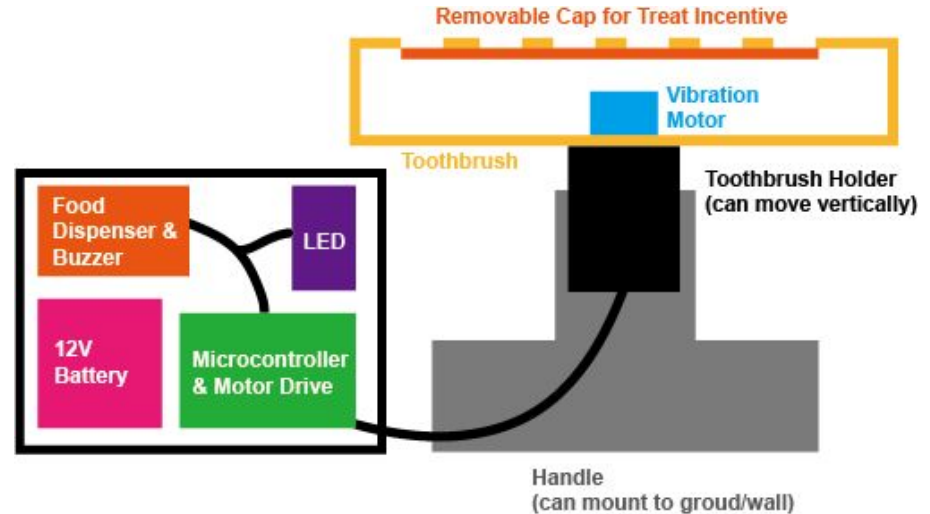


Figure 3: Original System

## Revisions to Mechanical Design

The final system now takes a more refined form.

There are now three parts:

- Brush Handle
- Treat Dispenser (PCB Compartment)
- Battery Compartment

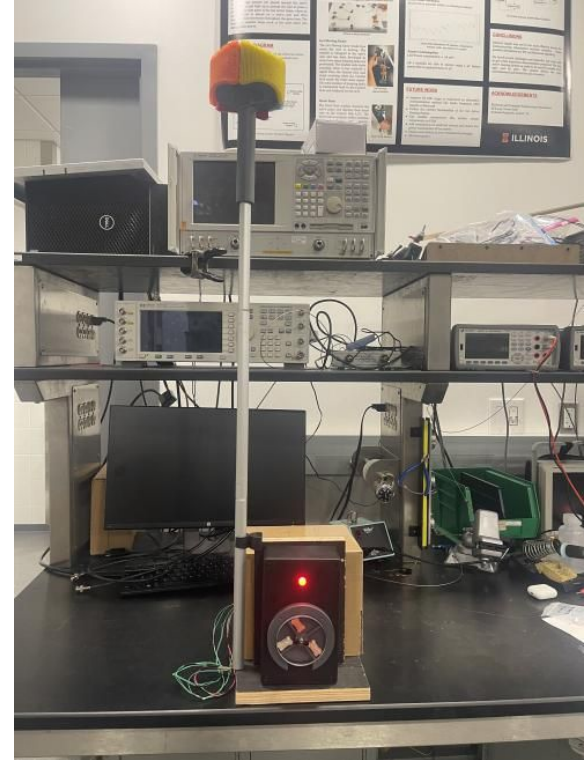


Figure 4: Final Design

## High Level Requirements

1. The dog toy will be able to brush away food with similar properties of plaque off model teeth through the vibration of the bristles.
2. The dog toy will use treats and a buzzer sound to help make brushing their teeth a habit for dogs.
3. The electronic system will be solid enough to withstand the vibration, and the shell should be strong enough to withstand a small dog's bite (about 100 psi).

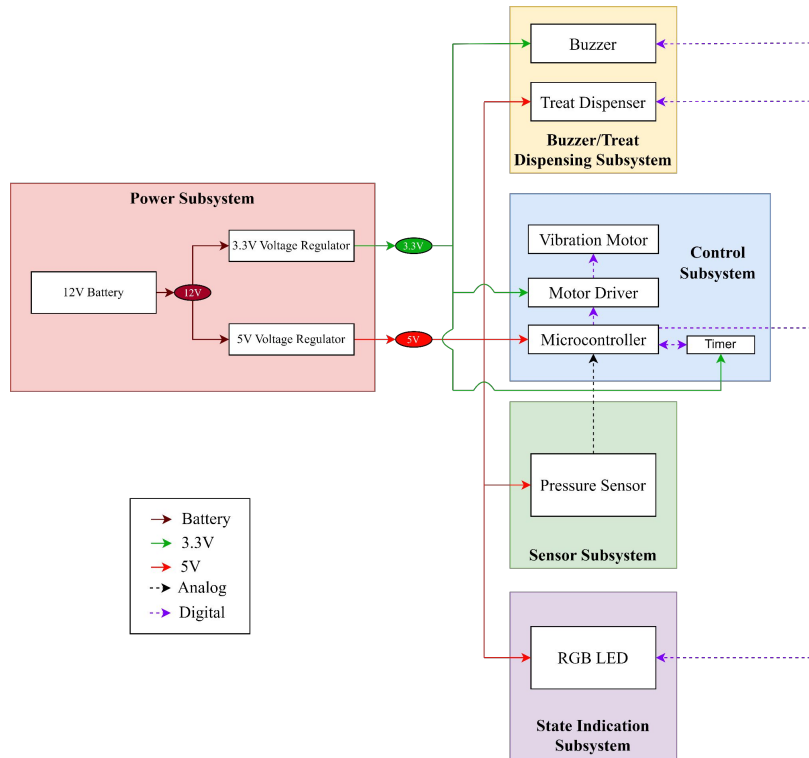


Figure 11: Block Diagram

## Block Diagram

There are 5 subsystems:

1. Control Subsystem
2. Sensor Subsystem
3. Buzzer/Treat Dispensing Subsystem
4. State Indication Subsystem
5. Power Subsystem





# CONTROL SUBSYSTEM

## Software – Goals

- Control the toy automatically, help dogs to develop a habit of brushing their teeth constantly
- Analyze pressure readings
- Provide control signal to vibration motor, stepper motor, buzzer, LED
- Be able to enter sleep mode to save power

## Software – Requirements

- When the required brushing time is reached, the pressure sensor will not trigger a transition in state
- When the timer's alarm raises during vibration, the system will reset only after the vibration has stopped

## Control Subsystem

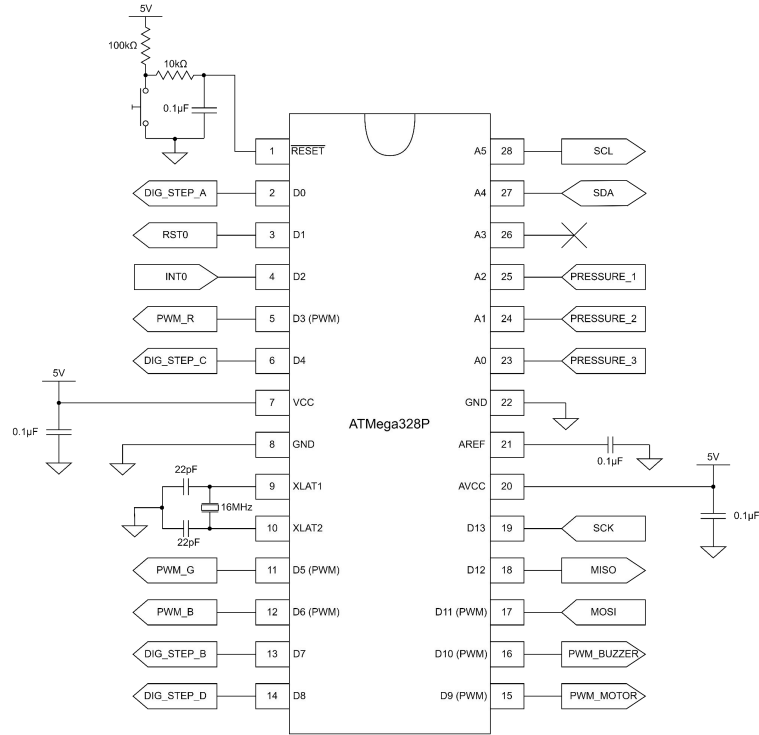


Figure 12: Microcontroller Circuit

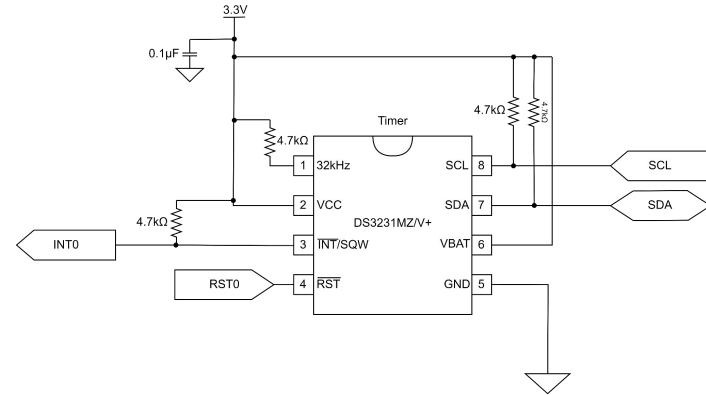


Figure 13: Timer Circuit

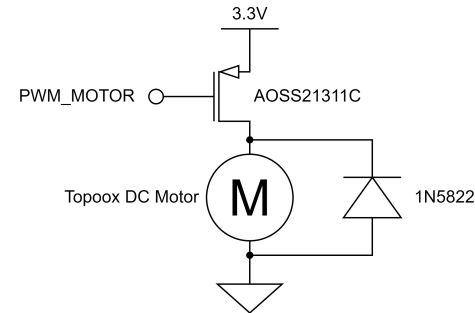


Figure 14: Vibration Motor Circuit

## Software – Control Flow

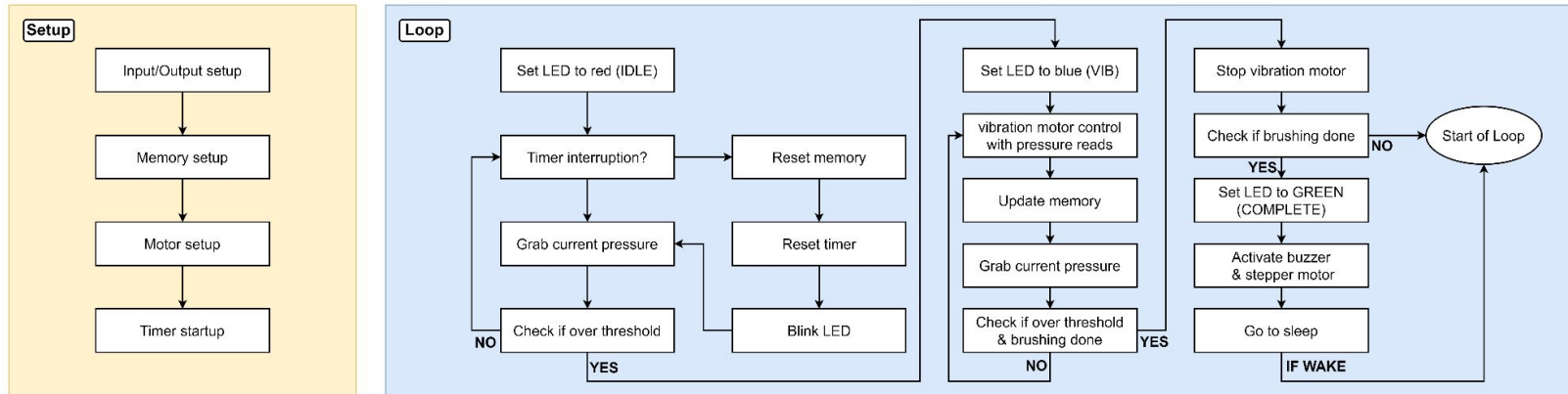


Figure 24: Software Flow Diagram

## Software – Pressure vs. Vibration

As dog bites harder, frequency of vibration should increase

Range of pressure sensor readings: 0.5~1.6V

Vibration motor optimal dutycycle: 20~60% (details are covered in sensor subsystem).

A linear relationship can be generated.

When our system starts vibrating, it will adjust the vibration frequency in real time according to the pressure reading.

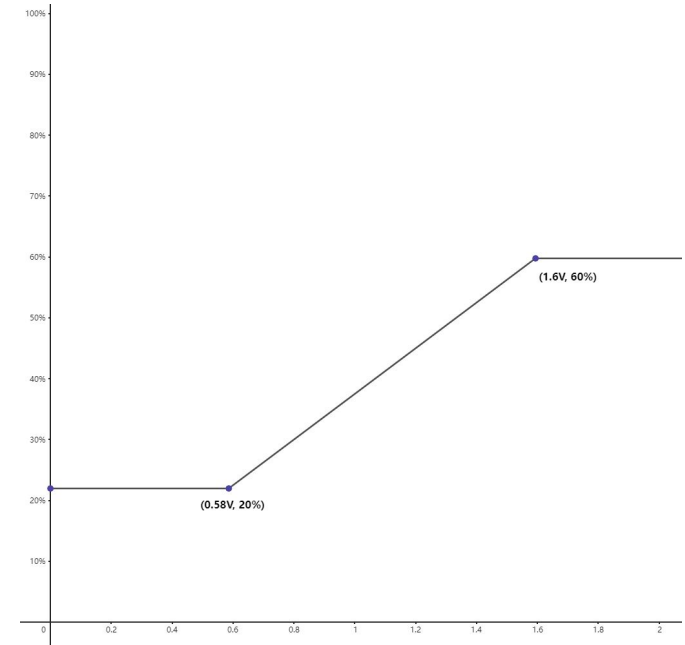


Figure 25: pressure - vibration speed relation

## Software – Timer

Since the system work in a daily basis, it is appropriate to put the MCU into sleep if brushing goal is met before the next brushing session (i.e., 12hrs).

Two timers can be used to wake up MCU again after a deep sleep: external (DS3231) and internal (WD)

- DS3231 requires I2C communication, but requires no additional manipulation during sleep
- Watchdog is a built-in timer for ATmega328P, but its timing setting is only up to 8s (i.e., frequent reset is needed if we want to sleep MCU for a long time)

We implemented both to provide some degree of insurance, user can choose the one they want to use.



# SENSOR SUBSYSTEM

## Sensor – Goals

- Generate a voltage that varies according to the thin film resistance
- Consumes minimal current

## Sensor – Requirements

- The output voltage should at least swing from 0.5V to 4.9V as thin film resistance varies from 10k $\Omega$  to 1k $\Omega$
- Each sensor circuit should consume  $\leq 2\text{mA}$



## Sensor Subsystem

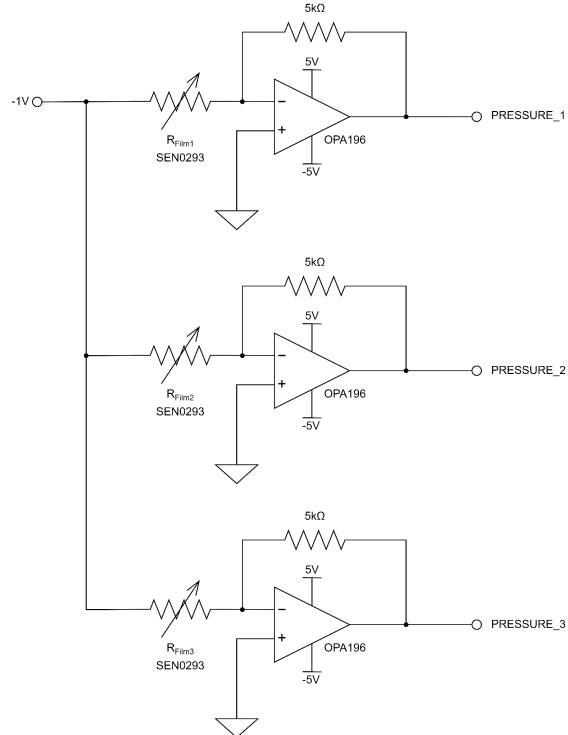


Figure 15: Pressure Sensor Circuit

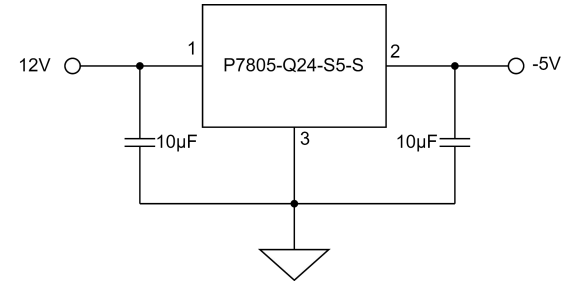


Figure 16: -5V Biasing Circuit

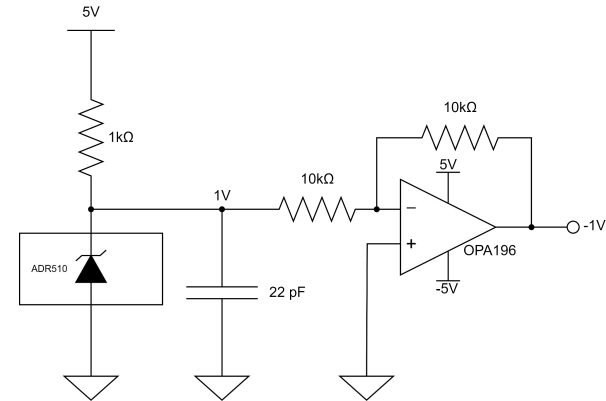


Figure 17: -1V Reference Circuit

## Sensor Subsystem

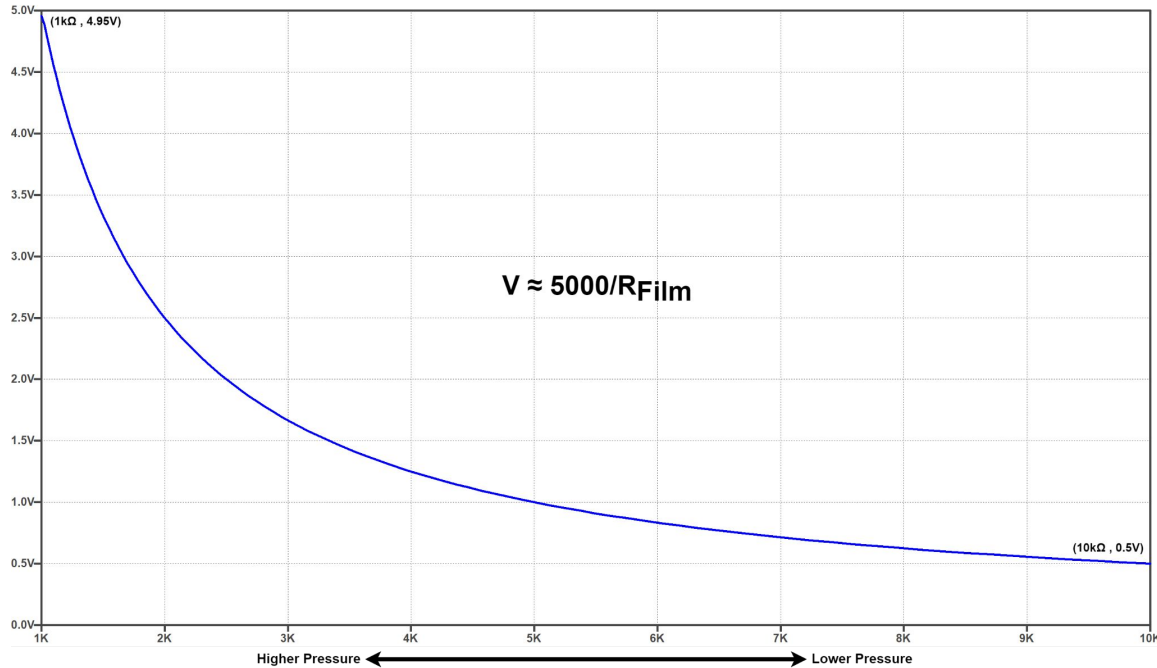


Figure 24: Pressure Sensor Circuit Output

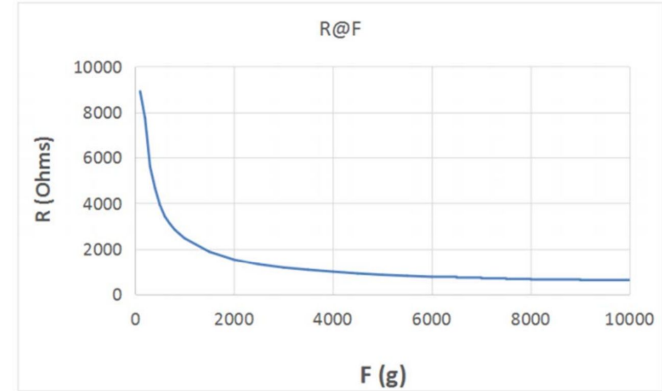


Figure 25: Thin Film Resistance  
Source: Adapted from [4]

$V_{\text{MIN}}$	$V_{\text{MAX}}$	I
0.03V	4.95V	<2mA

Table 3: Pressure Sensor Performance



# **BUZZER/TREAT DISPENSING SUBSYSTEM**

## Buzzer/Treat Dispenser– Goals

- Create a loud sound when a the cleaning is done
- Rotates the wheel appropriately to dispense a treat when a cleaning is done
- Consumes minimal current

## Buzzer/Treat Dispenser – Requirements

- The treat dispenser can rotate  $90^\circ$  at a time and releases a treat.
- The buzzer is audible enough to mark the end of a cleaning session.
- The buzzer should draw  $\leq 20\text{mA}$ .

## Buzzer/Treat Dispensing Subsystem

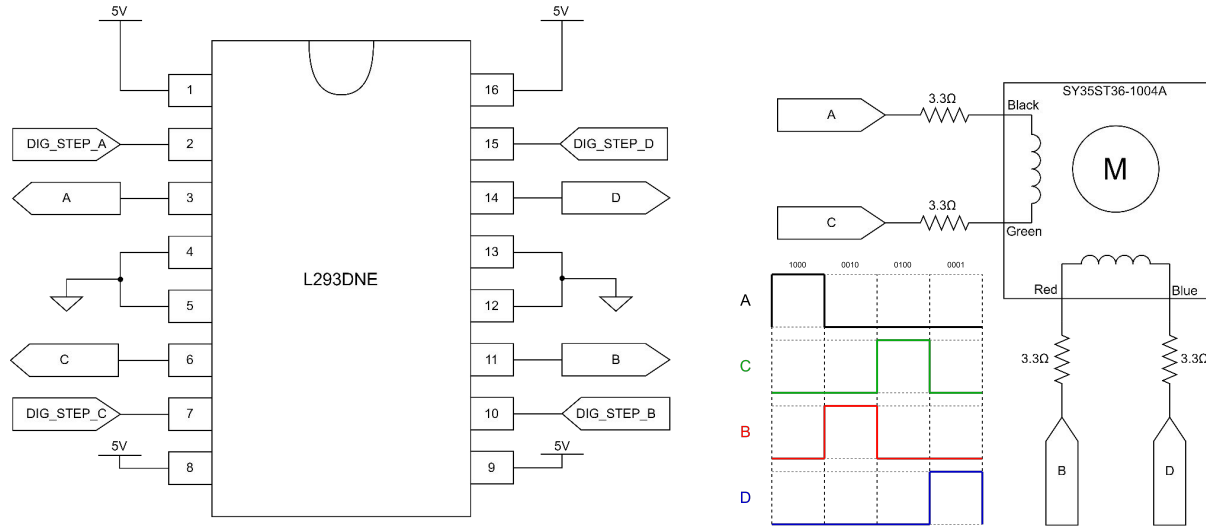


Figure 18: Stepper Motor Circuit & Stepping Sequence

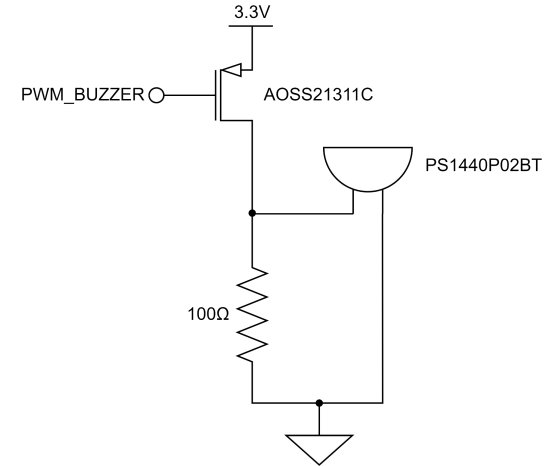


Figure 19: Buzzer Circuit



# STATE INDICATION SUBSYSTEM

## State Indication – Goals

- Communicates the current status to the user
- Consumes minimal current

## State Indication – Requirements

- The LED should be bright enough so that they are easy to identify.
- Each color of the LED consumes  $\leq 20\text{mA}$

## State Indication Subsystem

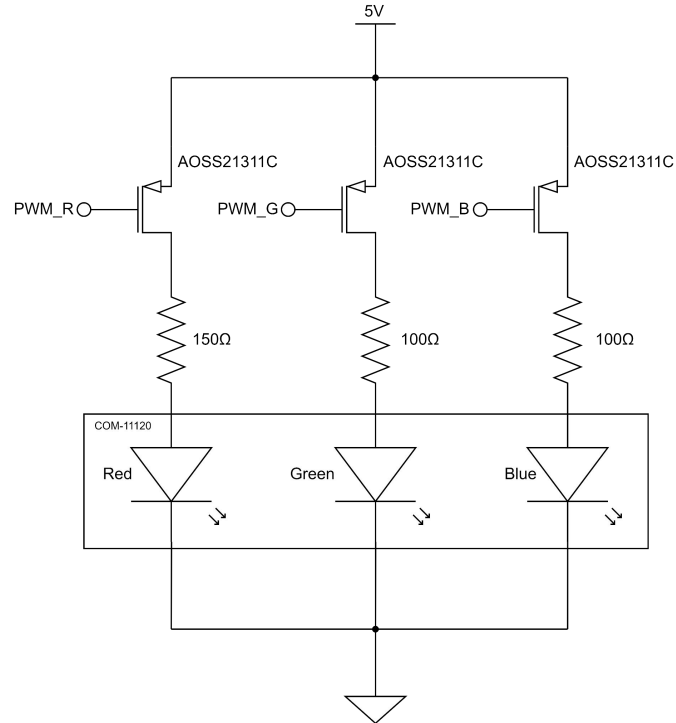


Figure 20: RGB LED Circuit





# POWER SUBSYSTEM

## Power – Goals

- The battery should be charged well over 12V
- 3.3V voltage regulator and 5V voltage regulator outputs the appropriate voltage

## Power – Requirements

- The battery should output  $\geq 12V \pm 2\%$ .
- The 3.3V voltage regulator should output  $3.3V \pm 0.066V$ .
- The 5V DC voltage should be maintained at  $5V \pm 0.1V$ . Also, the voltage ripple needs to be less than 50mV peak-to-peak.

## Power Subsystem

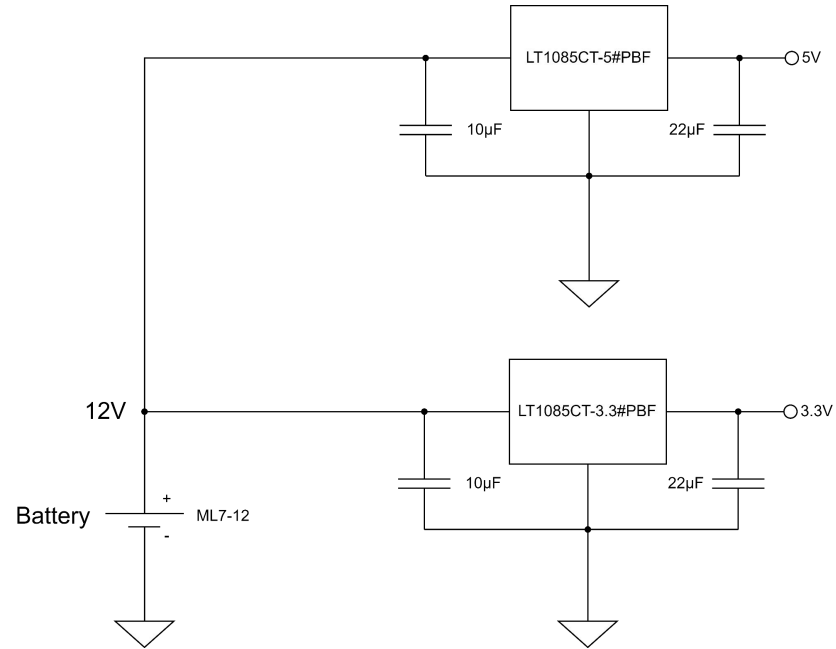


Figure 21: Power Supply Circuit

## Power Supply Subsystem

Regulator	$V_{OUT}$	$I_{MAX}$	$V_{Ripple}$	$I_{Quiescent}$
LT1085CT-3.3#PBF	3.314V	3A	N/A	8mA
LT1085CT-5#PBF	5.000V	3A	<50mV	8mA

Table 1: Power Supply Performance

Condition	Battery Voltage
No Load	12.998V
Loaded	12.700V

Table 2: Battery Performance



# PCB

# IMPLEMENTATION



## PCB

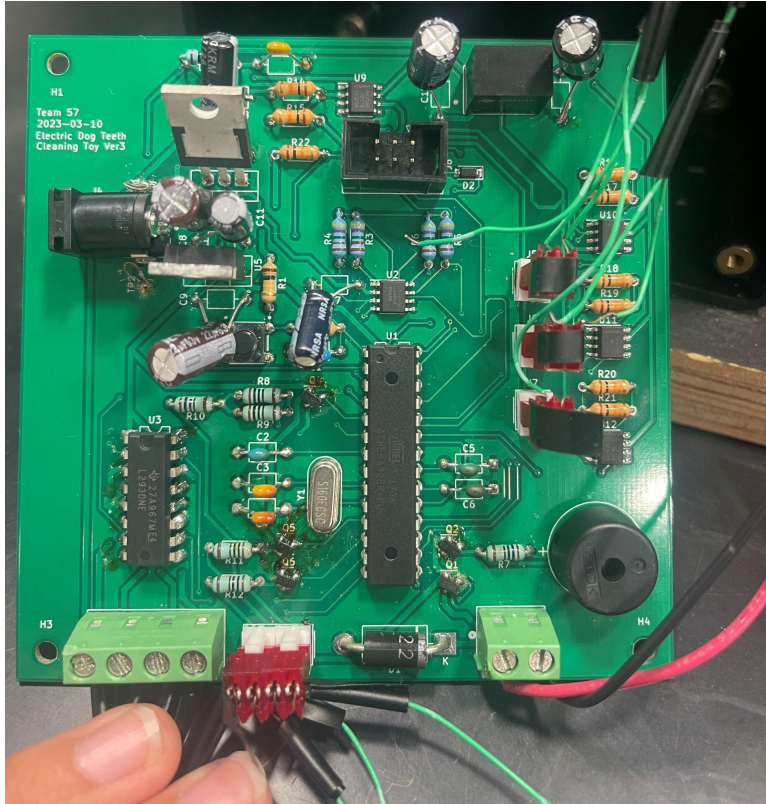


Figure 22: Finished PCB


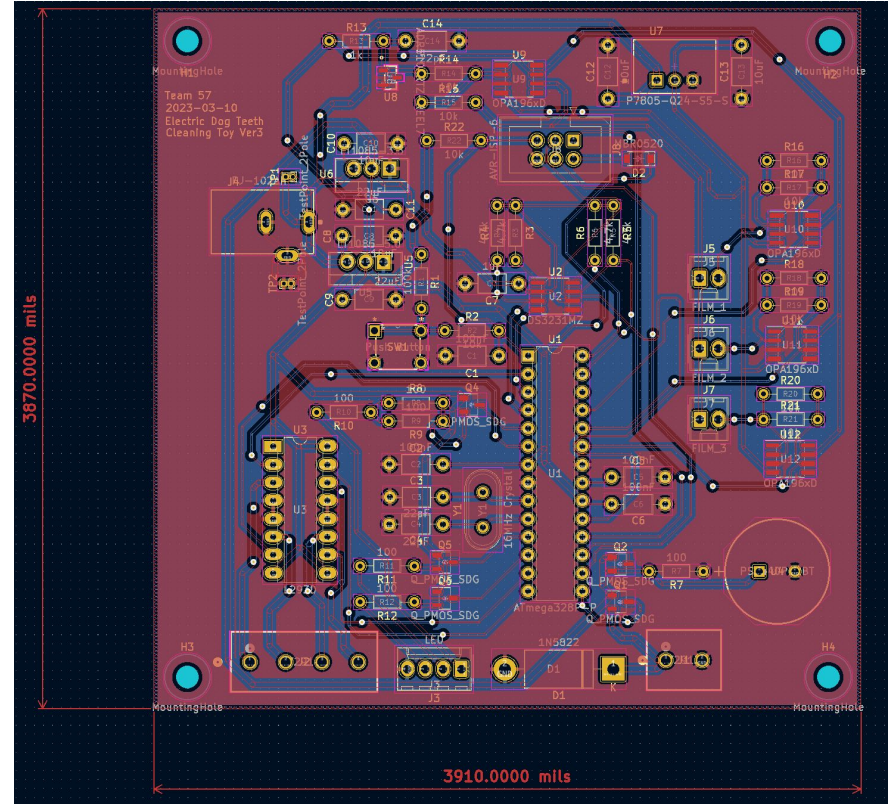


Figure 23: PCB Layout

 

# RESULT





## Major Current Draw

Duty Cycle	%Power	Vibration Motor Current
85%	15%	0.893A
23.5%	76.5%	2.016A

Table 4: Vibration Motor Current Draw

Device	Current
Stepper Motor	<0.5A
Digital IC	50mA - 80mA
Buzzer	17mA
Red LED	20mA
Green LED	17mA
Blue LED	17mA

Table 5: Other Major Current Draws



# CONCLUSION

## Ethical Issue

- Major Issue

The use of a large battery may be dangerous in a household environment. There is a potential fire hazard and a health hazard.

- Mitigation

1. The battery itself and relevant wiring are properly concealed.
2. The circuit board uses a barrel connector. If desired, any voltage source  $>6V$  can be used as long as it can supply 2-3A.

## Success

- Met all of our high level requirements
- Able to protect our system to keep it user and dog friendly
- Able to prove concepts that would make this project a success in the real world
  - Vibration in the shape of a toy that a dog can play with
  - Used materials equivalent to dog friendly materials and proved that they can at least withstand a pressure of 100 psi

## Challenges

- The total size of the circuit is large
- Inaccuracy and inconsistency of thin film sensors compromised resolution of sensor
- Inductive loads created interfering ripples that is higher than expected
- Potential heating issue when the vibration motor is operated at high power for a long time

## Future Development

- Use dog friendly material
- Implement some user interfaces
  - Adjust brushing time/frequency; timer selection
- Integrate our project with existing dog food dispensing systems
- Make the brush portion more bone shaped and smaller
- Separate digital and analog components completely to different LDOs
- Add heat sink



# QUESTIONS?

## References

- [1] K. B. Enlund *et al.*, “Dog Owners’ Perspectives on Canine Dental Health—A Questionnaire Study in Sweden,” *Front. Vet. Sci.*, vol. 7, p. 298, Jun. 2020, doi: 10.3389/fvets.2020.00298.
- [2] B. Young, “Dental Month,” *Companion Pet Clinic of North Phoenix*, 2019. [Online]. Available: <https://www.companionpetclinicphoenix.com/archives/2017/02/04/dental-cleanings/>.
- [3] Institute of Electrical and Electronics Engineers, “IEEE Code of Ethics,” *IEEE*. [Online]. Available: <https://www.ieee.org/about/corporate/governance/p7-8.html>.
- [4] DFRobot, “RP-L-170 Thin Film Pressure Sensor,” SEN0293 datasheet, n.d.. Available: [https://media.digikey.com/pdf/Data%20Sheets/DFRobot%20PDFs/SEN0293\\_Web.pdf](https://media.digikey.com/pdf/Data%20Sheets/DFRobot%20PDFs/SEN0293_Web.pdf).





# The Grainger College of Engineering

UNIVERSITY OF ILLINOIS URBANA-CHAMPAIGN