

USB 3.0 Outlet Conversion

Cindy Fok, Andrew Moruzi, and Tyler Neyens

University of Illinois at Urbana-Champaign



Spring 2012

Introduction


- Addresses the growth of external DC converters for consumer products.
- Objective:
 - Modify an AC wall outlet
 - Include two DC power ports:
- Eliminates the need for DC converters outside the wall outlet or in appliances.

Product Features

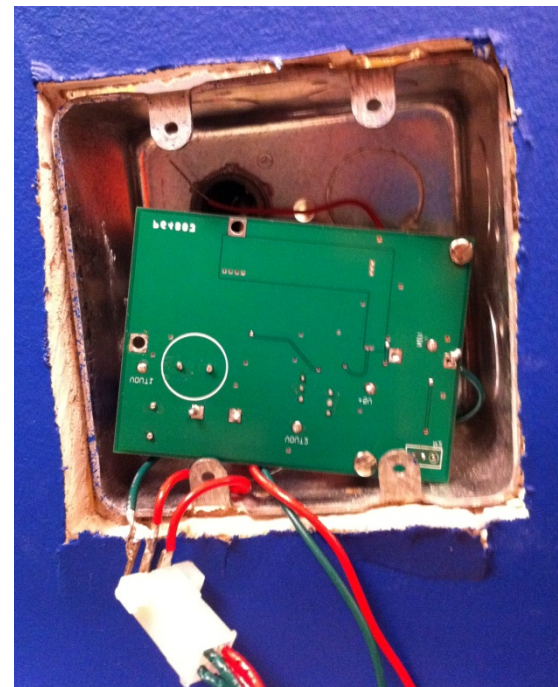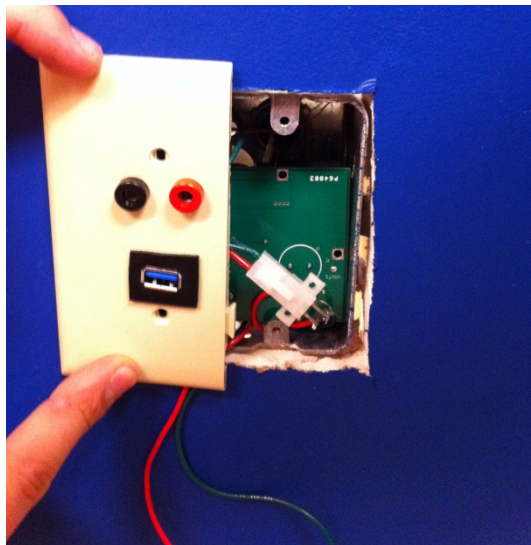- Two DC outputs with different power levels options
- Eliminated need of additional power converter
- High efficiency
- In-wall installation
- Simple installation process




Design Overview

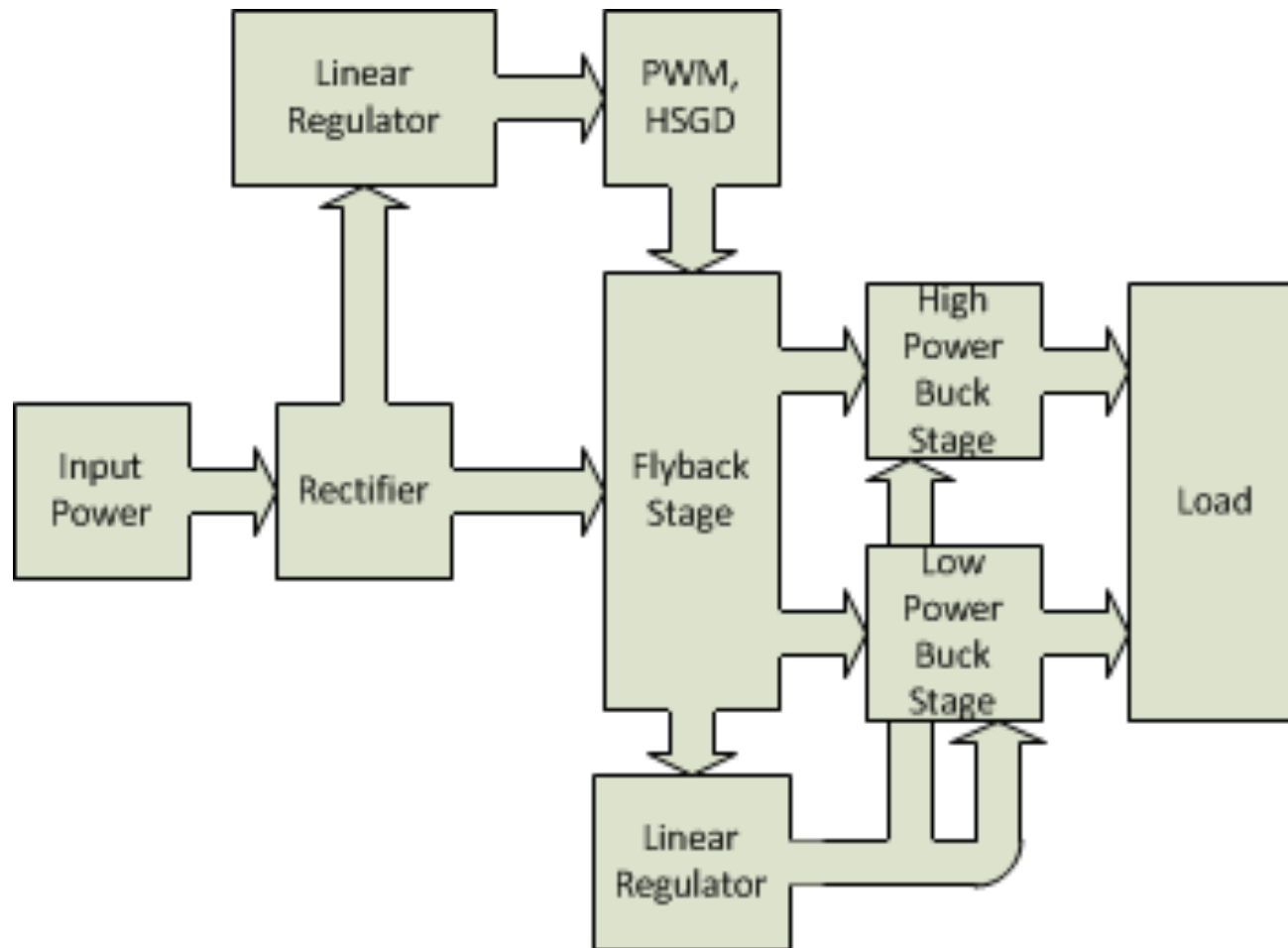





Rectifier

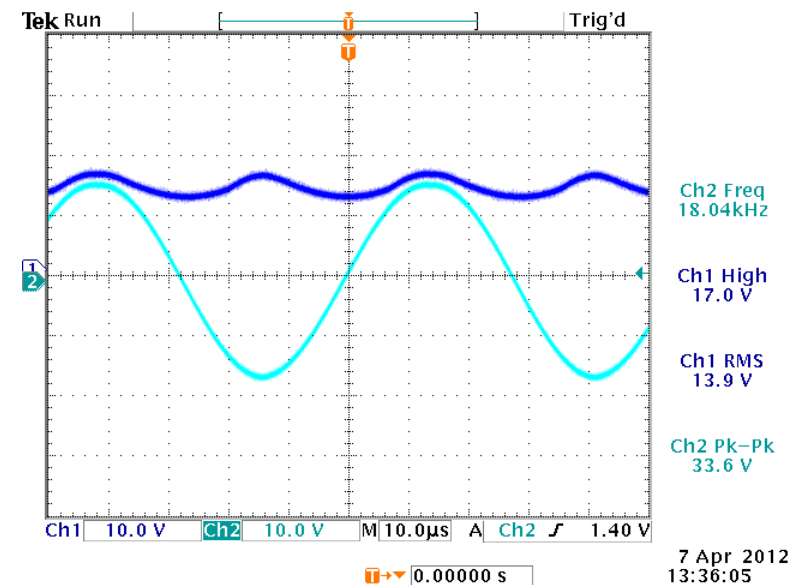- H-bridge rectifier chip
 - convert 120Vac power from the wall to 108Vdc
- Efficiency: 97.37%
- Ripple: $\pm 1.7\text{V}$
 - With capacitor bank of $156\mu\text{F}$
- Waveform:
 - Channel 1 Output Voltage
 - Channel 2 Input Voltage from the Function Generator



Linear Regulators

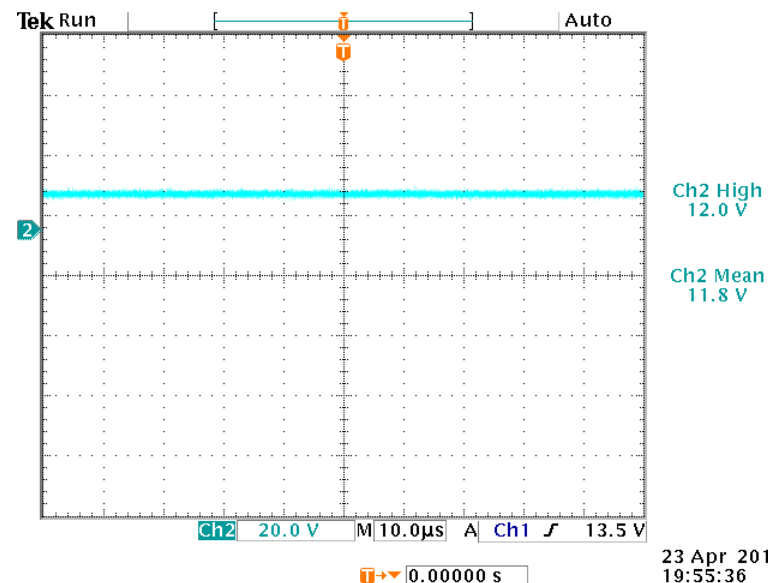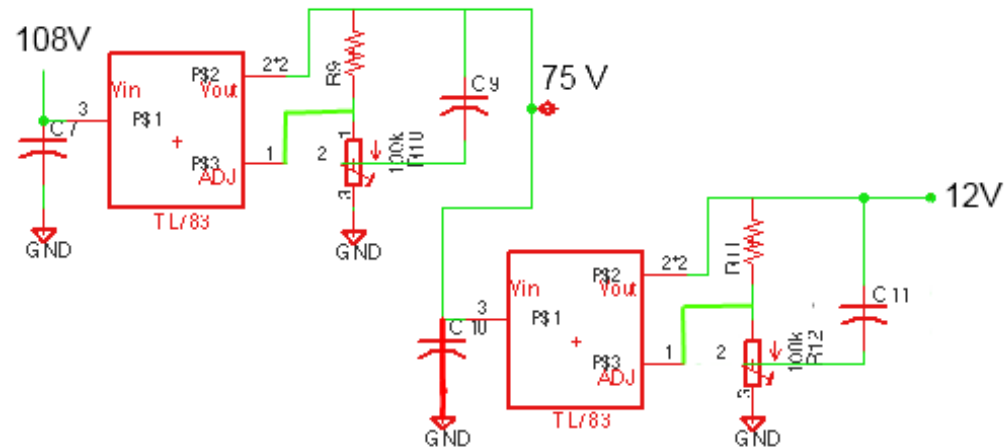- Design:
 - Used two linear regulators
 - Step down from 108V to 75V
 - Step down from 75V to 12V
 - Avoid over stressing the components
- Waveform:
 - Input 25 V from DC power supply.
 - Pot adjusted to voltage.
 - Range from 20V-8V tested.




FLYBACK CONVERTER




Flyback Converter

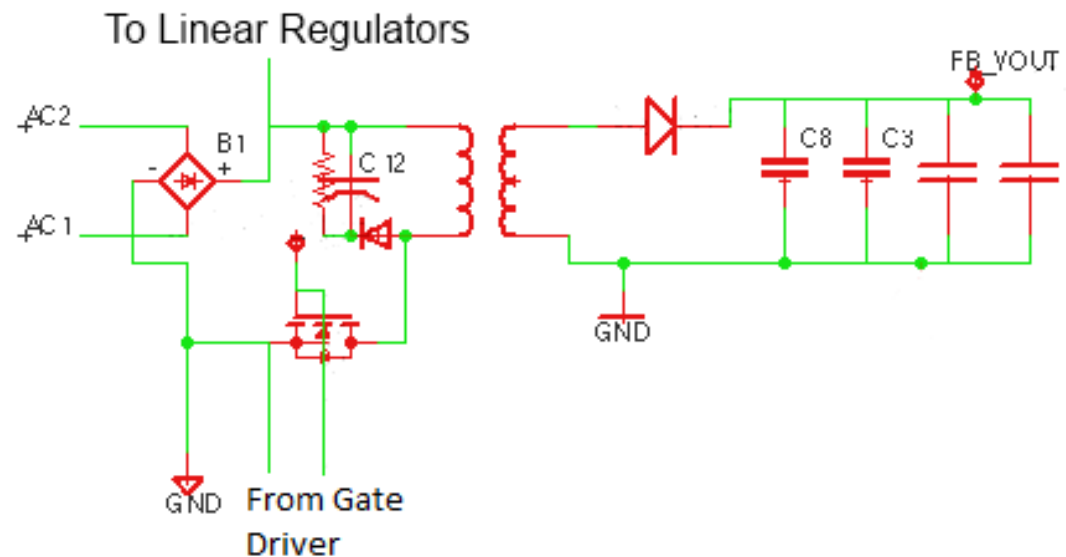
- Provides:
 - galvanic isolation between the output and input
 - an additional layer of surge protection
- Ratings:
 - Input: 108V/3 A
 - Output: 25V/8.1 A



Flyback MOSFET Control

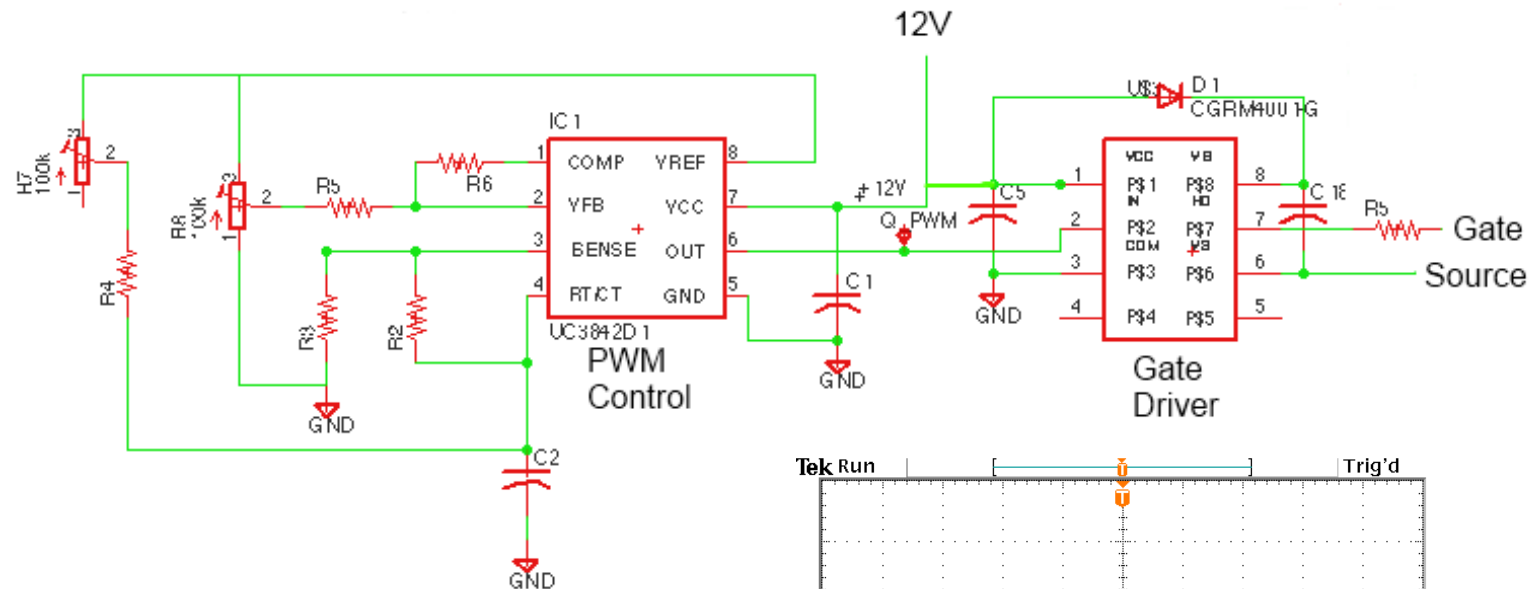


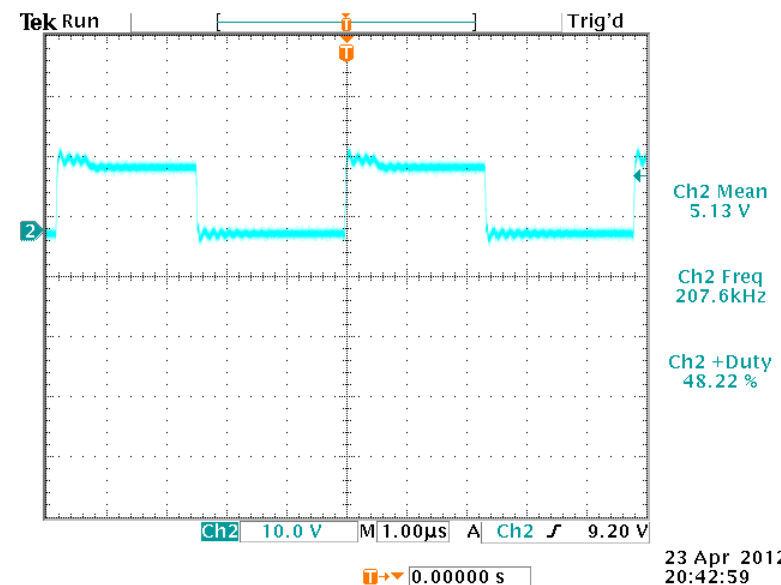
- Waveform of PWM control signal for the flyback converter



23 Apr 2012
20:42:59

Flyback Converter Challenges

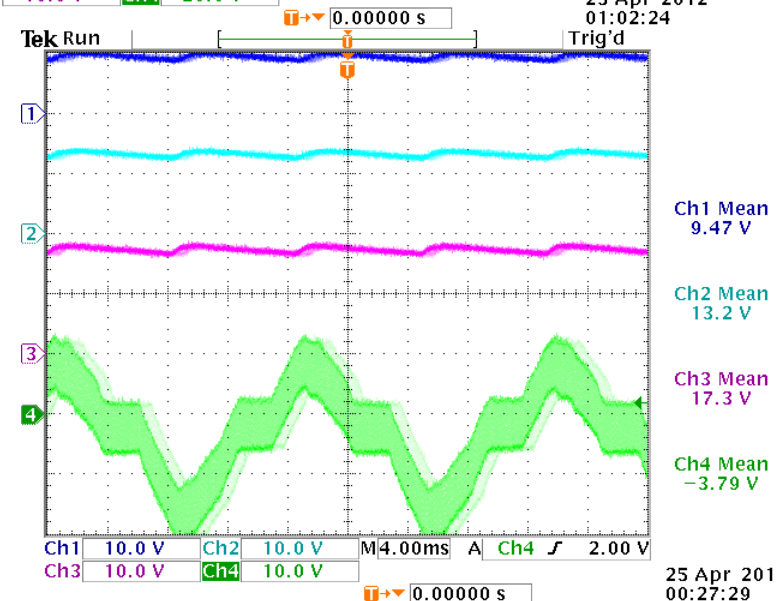
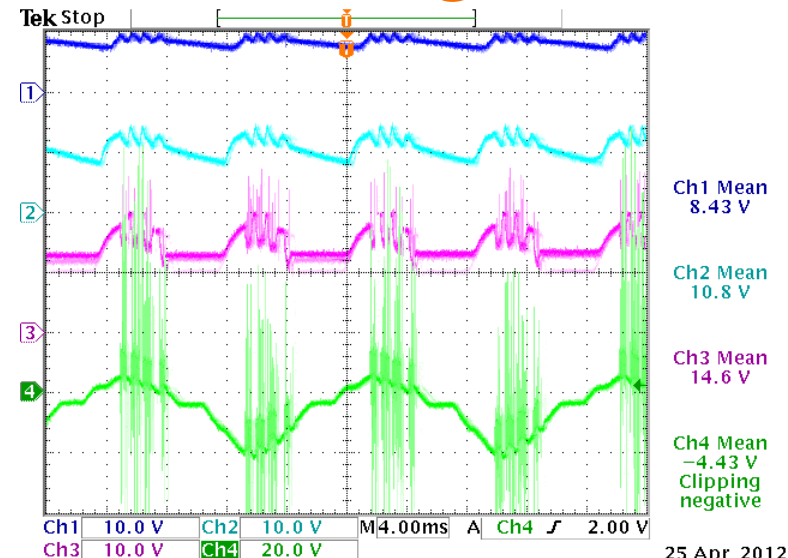
- Top Waveforms:
 - Noise on the switching signal
- Bottom Waveforms:
 - Floating ground
- Channels:
 1. second voltage regulator output
 2. first voltage regulator
 3. bridge rectifier output.
 4. switching signal (not on differential probe)



LOW BUCK CONVERTER


Low Buck Converter

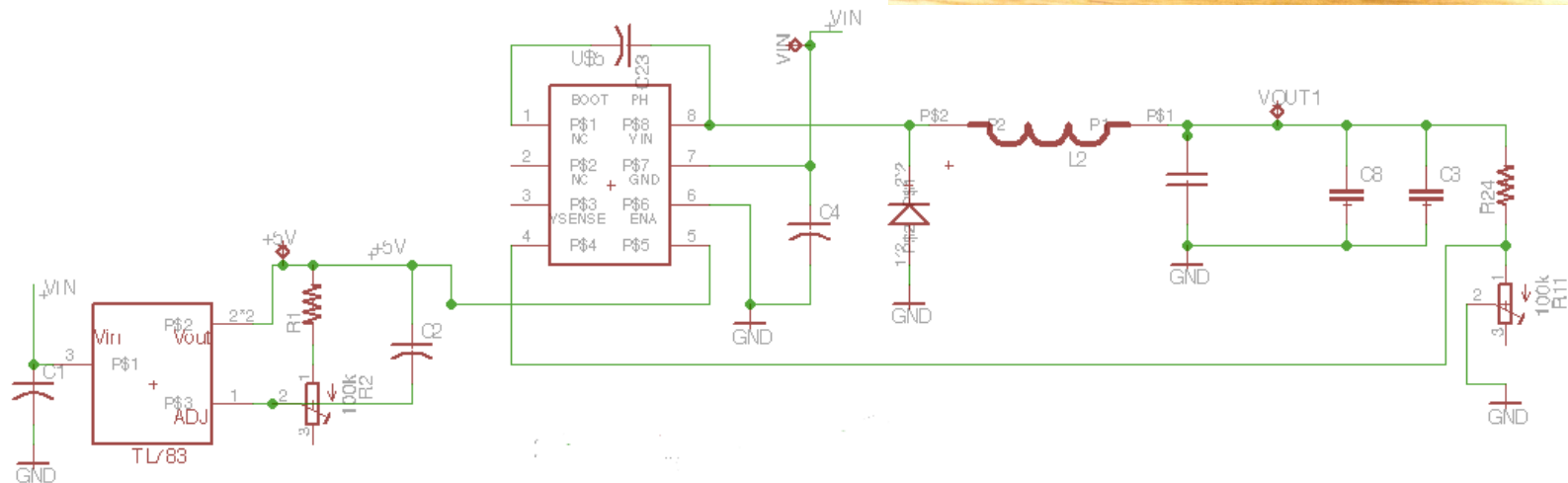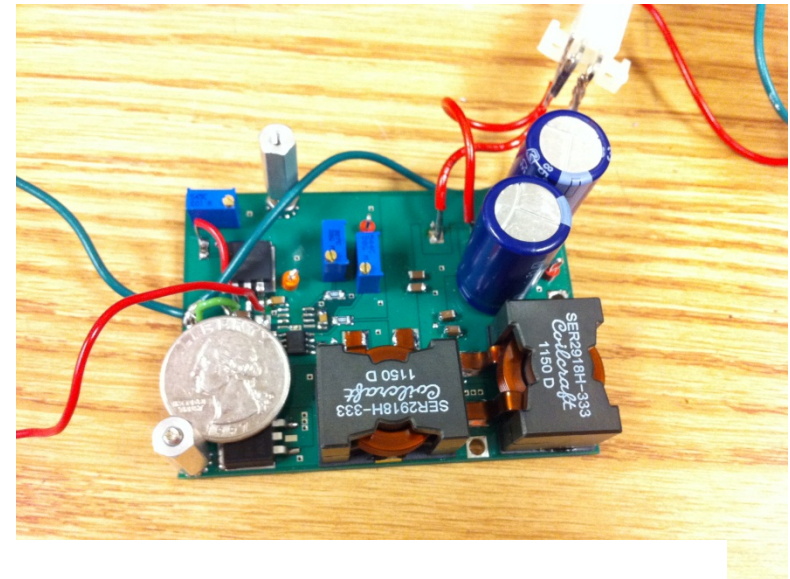- Ratings:
 - Input: 25V/1A
 - Output: 5V/5A
 - Switching Frequency 300 kHz




Low Buck Control

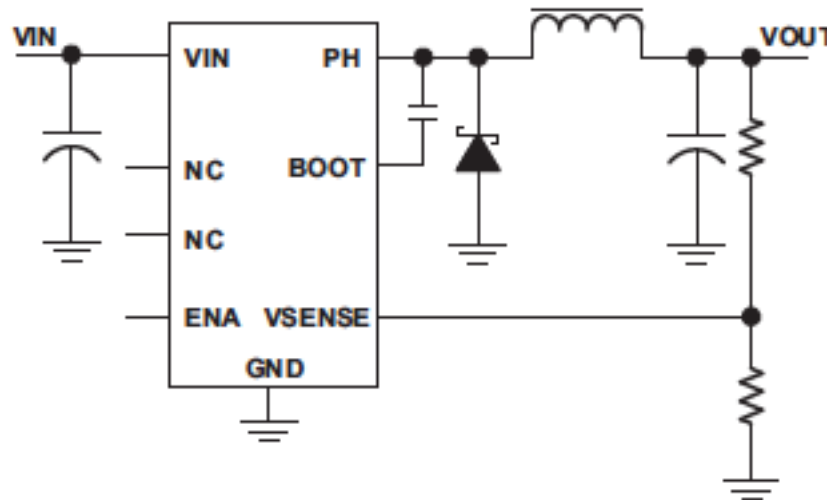- Used IC chip: TSP5450
- Included the MOSFET and controls for linear regulations
 - Voltage output regulated itself to be 5V




Low Buck Output

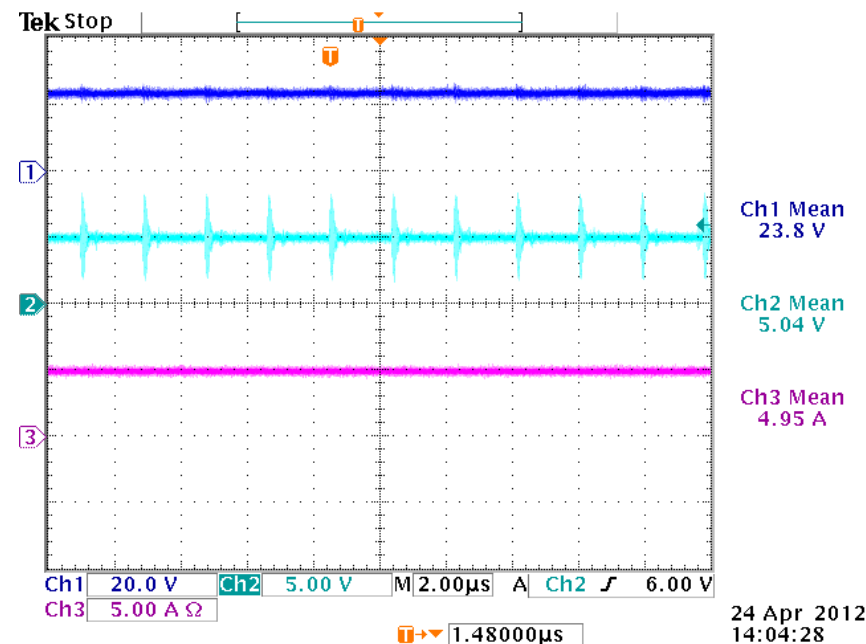- Average Voltage: 5V
- Ripple: $\pm 100\text{mV}$
- Waveform:
 - Low buck converter with an electronic load.
 - The electronic load with set output current of 4.75A
 - Channels:
 1. Input Voltage
 2. Output Voltage
 3. Output Current



Efficiency Curve

- Average Efficiency is 80.3%

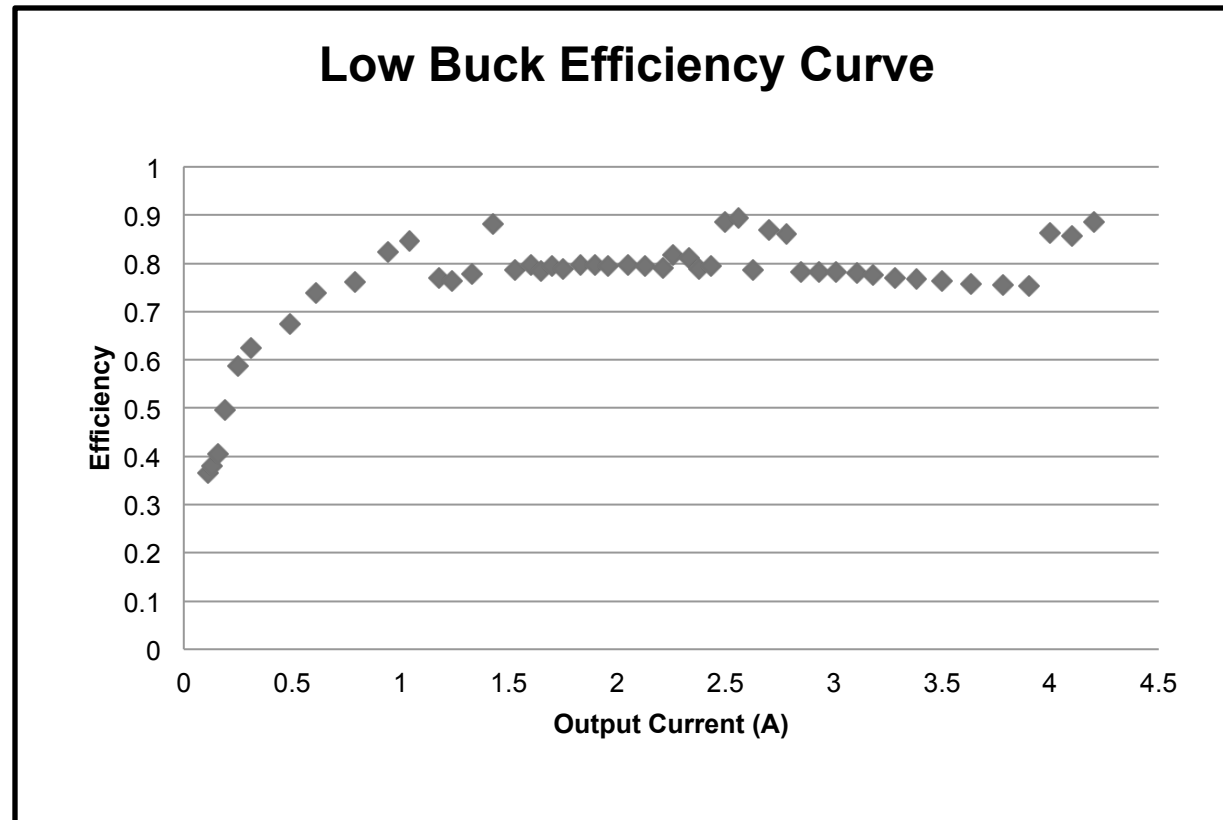




HIGH BUCK CONVERTER

High Buck Converter

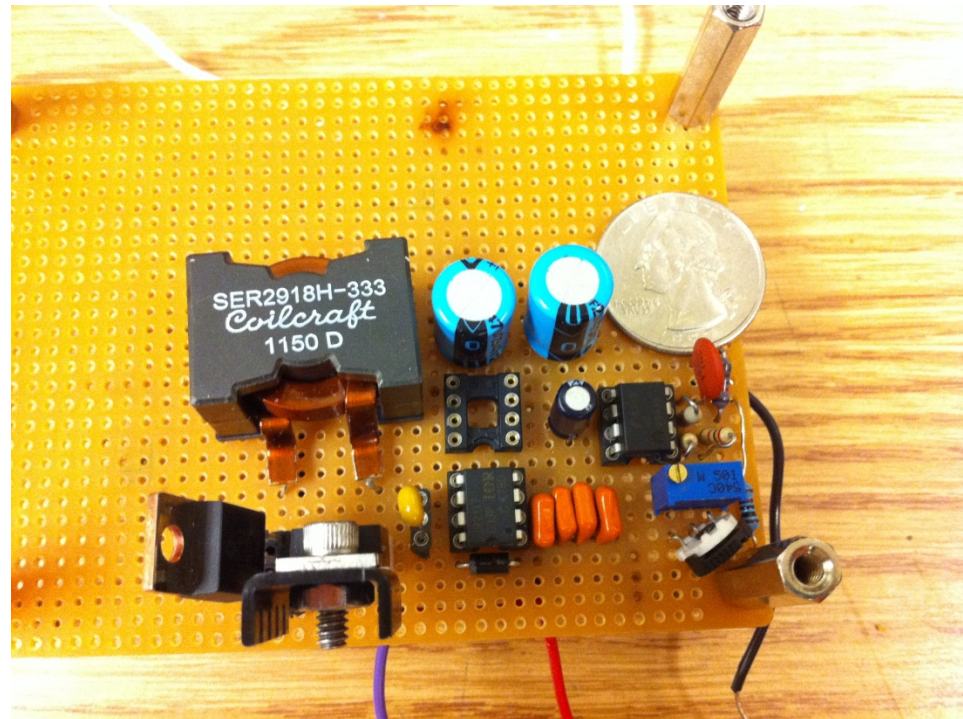- Rating:
 - Input: 25V/7.2A
 - Output: 12V/15A
 - Switching Frequency 115 kHz




High Buck Control

- Original Idea:
 - TI Buck Controller (TPS40020)
 - Over Current Protection mode
- Alternative Approach:
 - PWM (UC3843)
 - High Side Gate Driver (IR2117)

High Buck Output

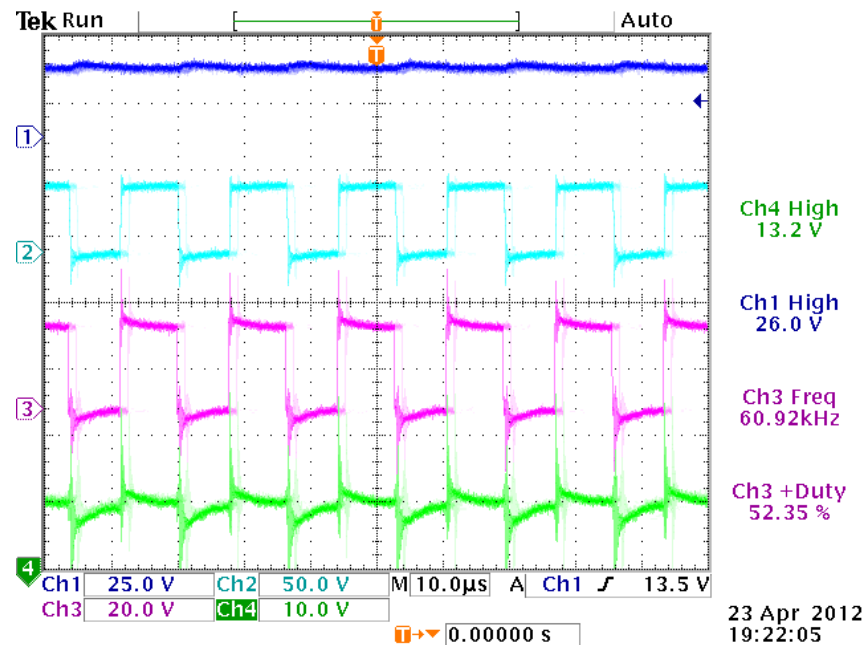
- Waveform:
 - loaded with drill 25V input from DC power supply.
 - Channels:
 1. Voltage output (unadjusted)
 2. Gate signal
 3. PWM output
 4. Input Voltage load drawing 3.5A






Efficiency Curve


- Average Efficiency is 88.93%

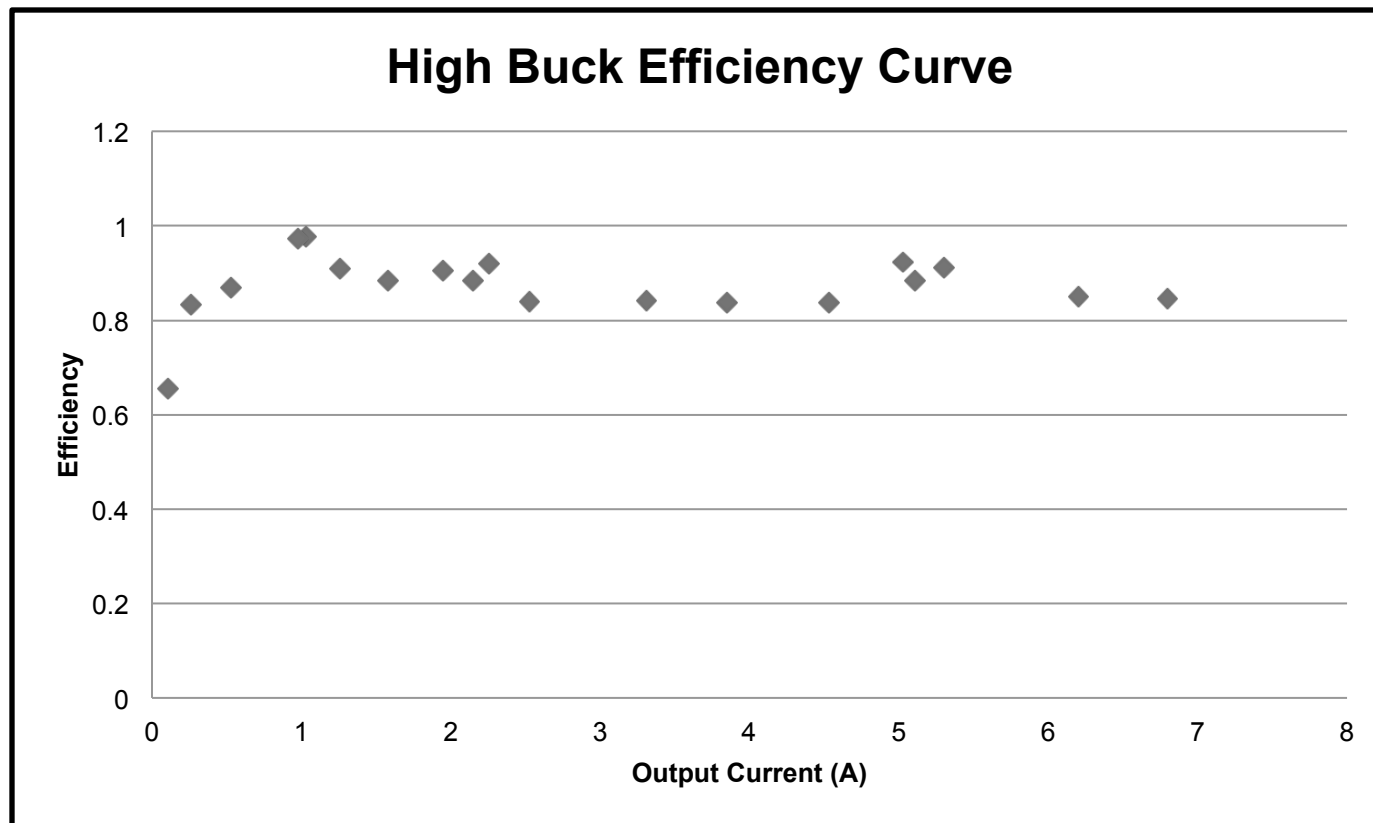

Loads

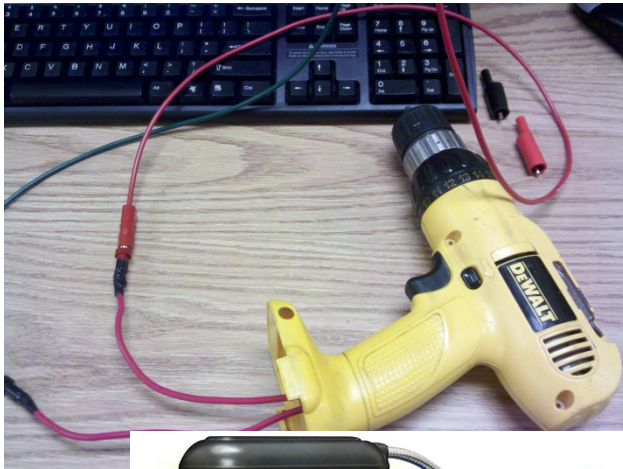


Wall Construction

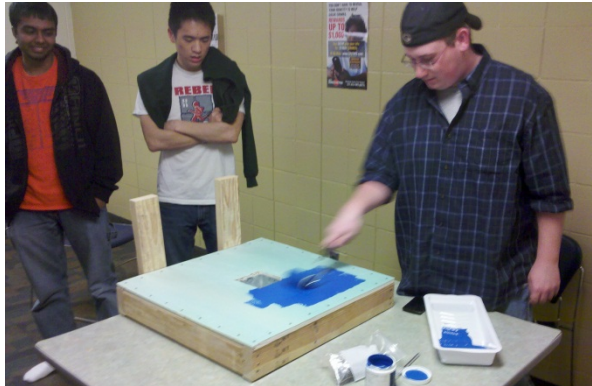


Overall Results

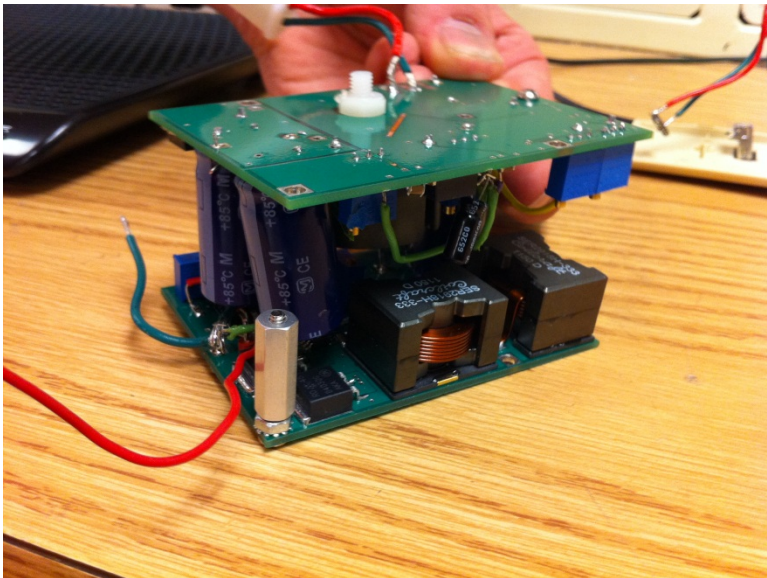- Each PCB worked
- Problems with Flyback PCB
- 100% operational Buck Modules



Lessons Learned

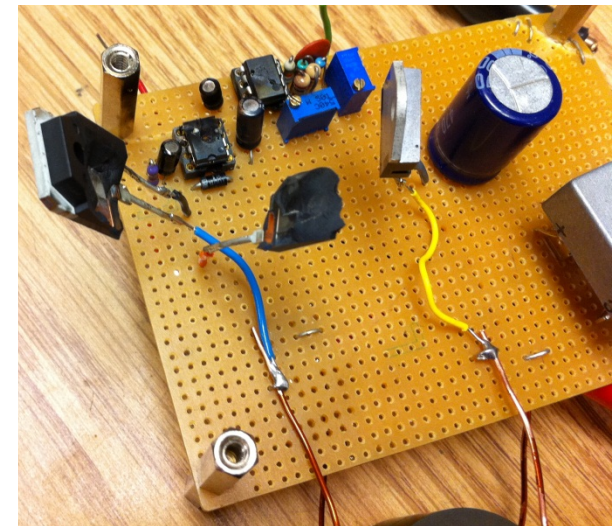- Check Circuit (signals)
- Ground
- Don't plug in the circuit with power on during the demo
- Cindy is a good cook



Future

- Smaller Components
 - Potentiometers, higher switching frequency, inductor, PCB layout
- Lower ESR Capacitors
- PCB High Buck
- Commercialize

The Battle Continues...

Questions

