

# iPHONE ULTRASOUND

By

Jonathan Adam

Adam Keen

Dean Santarinala

Final Report for ECE 445, Senior Design, Spring 2012

TA: Mustafa Mir

2 May 2012

Project No. 2

## Abstract

Commercially-available, portable ultrasound devices are increasingly ubiquitous, but they all utilize ad-hoc processing and display hardware. This inevitably drives up the cost of these devices and usually results in poor user-interface. Many doctors now already carry this hardware around in their pocket on a smartphone, so why not use it to drive down medical device costs and provide a familiar user-interface? Our project involved development of an A-scan biometry ultrasound device that seamlessly connects to an iPhone 4S. Results demonstrate that the concept is feasible as an ultrasound device, but its complete functionality was not attainable in the time allotted.

## Contents

1	Introduction .....	1
1.1	Purpose .....	1
1.2	Functions .....	2
1.3	Blocks .....	2
2	Design .....	3
2.1	DGH Ultrasound Probe .....	3
2.2	T/R Switch .....	3
2.3	Transmit Pulser .....	3
2.4	Analog Front End .....	4
2.5	FPGA .....	5
2.6	iPhone Software .....	8
2.7	Power Electronics .....	9
3	Design Verification .....	11
3.1	DGH Ultrasound Probe .....	11
3.2	T/R Switch .....	13
3.3	Transmit Pulser .....	13
3.4	Analog Front End .....	14
3.5	FPGA .....	16
3.6	iPhone Software .....	17
3.7	Power Electronics .....	17
4	Costs .....	18
4.1	Parts .....	18
4.2	Labor .....	18
5	Conclusion .....	19
5.1	Accomplishments .....	19
5.2	Uncertainties .....	19
5.3	Ethical considerations .....	19
5.4	Future work .....	20
	References .....	21
Appendix A	Design Supplements .....	23
Appendix B	Requirement and Verification Table .....	33

# 1 Introduction

## 1.1 Purpose

The purpose of our project is to create a low-cost, portable A-scan biometric ultrasound circuit driven by an iPhone 4S. This would provide an inexpensive ultrasound alternative with a more user-friendly interface compared to existing optical ultrasound solutions.

 


Figure 1. Typical Biometric A-Scan [1]

Traditional A-scan machines perform 1-dimensional biometric scans that ophthalmologists use to measure the axial lengths of eyeball components. These measurements of the eye are used to calculate intraocular lens (IOL) power for cataract surgeries. Ultrasound transducers typically operate at 10MHz, since the short distances in the eyeball require high resolution. While there are handheld ultrasound probes available, they all use processor/video/input hardware created specifically for that device - driving up its cost while having a poor user interface. In addition, many third-world countries lack structured landline communication networks, making the sharing of this kind of medical information a heavy task. A system of sharing this information over modern, conventional wireless networks may aid in the health-care of ailing citizens. Our project aims to alleviate these problems by improving upon the user interface of existing devices, driving down costs with the use of hardware many doctors already own (the iPhone 4S), and securely sending eye scan results over established cellular networks.

## 1.2 Functions


A user can expect the following benefits from using our device:

- Lower medical device costs with the use of existing hardware
- Highly portable form factor
- Immediate/live ultrasound measurements
- Axial Eye Length (AEL) measurements accurate to within 0.1mm for anterior chamber depth, lens depth, vitreous length, and axial eye length

A user can expect the following functionality from our device:

- 10 MHz single-element ultrasonic transducer probe
- Manchester Encoded Transmission of A-scan data to iPhone 4S over 3.5mm Headphone Audio Jack
- Provides user with one echogram per second
- User-friendly interface on 3.5" iPhone 4S LCD display with touch user interface
- Choice of contact or immersion measurement
- Numeric values displayed for anterior chamber depth, lens thickness, vitreous length, and AEL with 0.1 mm resolution
- Integrated IOL power calculator
- Storage of up to 500 echograms for review and critiquing
- Ability to send echogram images over MMS or e-mail

## 1.3 Blocks

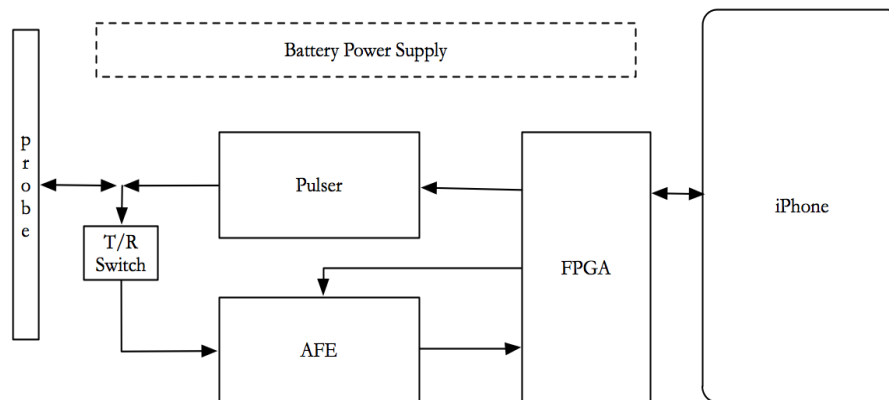

**Figure 2. Project Block Diagram Overview**

- **Ultrasound Probe:** Responsible for transmitting and receiving ultrasonic pulses.
- **Transmit Pulser:** Generates the high-frequency, high-voltage pulses sent to the ultrasound probe.
- **Analog Front End (AFE):** Amplifies and samples the received signal.
- **T/R Switch:** Protects the AFE from the Pulser's high-voltage output.
- **FPGA:** Controls the transmit/receive circuit, buffers sampled data, communicates with the iPhone.
- **iPhone:** Provides data processing and user-interface, communicates with the FPGA.
- **Power Electronics:** Regulates voltages and supplies power to all device components.

## 2 Design

### 2.1 DGH Ultrasound Probe

The DGH 6000 Scanmate A transducer provides the basis of our pulse-echo system. It allows for the production of longitudinal sound waves resulting from piezoelectric excitation by voltage pulses. The transducer consists of a single piezo-ceramic element that runs at a center frequency of 10.0 MHz nominal. It focuses an acoustic beam at 23.0 mm nominal and has a circular patient contact area 0.275" in diameter. It also contains a fixation LED to help center the patient's iris upon examination [2].

At the start of our project, we had a sample ultrasound transducer formerly made by the company Storz, but no longer in production. Given that we had no documentation or product support for this probe, we sought out sponsorship from DGH Technology, who graciously donated their DGH 6000 transducer probe. Probe dimensions and pin-outs are provided in Figure 3 of Appendix A.1.

### 2.2 T/R Switch

The TX810 chip protects the receiver circuit's amplifiers from high voltage pulses on the probe transmission line. It is an 8-channel, programmable T/R switch for medical ultrasound applications, but since our project is only a 1-dimensional ultrasound with a single element transducer, only one channel is required. Internally, it consists of a diode bridge, bias network, clamp diodes, and logic controller. This T/R switch can be programmed to allow for different bias currents, but for our purposes, the mode that allows for the minimum amount of insertion loss is the most ideal (B1,B2,B3 inputs set to HIGH) [3]. National Semiconductor provides a similar option for an ultrasound T/R switch chip in its LM96530 offering. However, we deemed the cost of the TX810 more economical, given both chips offer the same functionality in similar chip packages. A pin assignment schematic and construction of our TX810 breakout board is provided in Figures 4 and 5 of Appendix A.2.


### 2.3 Transmit Pulser

The transmit pulser's primary function is to accept a digital pulse from a controller (in our case, the FPGA) and relay a high-voltage pulse to the transducer probe [2]. Specifically in our application, we will send a 50ns-wide digital pulse to the pulser and expect a +30V output pulse of equivalent width. Recall that this ultrasound device operates at 10MHz, thus 50ns corresponds to a unipolar half-period of that frequency. Our original design employed Texas Instrument's LM96550 ultrasound transmit pulser. After several failed attempts to achieve correct operation, however, we used Maxim IC's MAX4940 high-voltage digital pulser instead. The MAX4940's design includes four channels, as well as positive and negative high-voltage supplies up to +220V and -220V, respectively. Since our application is a one-dimensional scan, only one channel was utilized. In addition, no complex beamforming (typical of multi-dimensional ultrasounds) was required, so we simply sent one unipolar (positive) pulse. This allowed us to avoid the need for a negative high voltage. For the positive high voltage, however, the DGH probe's specifications require that the pulse voltage be no higher than 32V [2]. In accordance with this, we selected +30V as the positive high-voltage supply (VPP). In order to operate correctly, the pulser also requires +10V and -10V output driver supplies (VCC, VEE), as well as a +3.3V logic voltage supply (VDD). Other than the positive digital pulse input from the FPGA (INP1A), all other digital input lines are grounded. This configuration drives output channels to high-impedance when not pulsing at high-voltage. Since we are only interested in utilizing one channel, all high-voltage outputs other than that of channel 1A are left floating. In order to keep the chip enabled, we tie the enable pin to the logic voltage supply [4]. Finally, 3.3nF AC-coupling capacitors are placed between each channel's amplifier and switch, and 0.1μF decoupling capacitors bypass all power supply inputs. A pin assignment schematic and construction of our MAX4940 breakout board is provided in Figures 6 and 7 of Appendix A.3.

## 2.4 Analog Front End

The AFE5801 is the receiver of our ultrasound circuit, taking in echoed voltage pulses and amplifying, then digitizing the received signals. To accomplish this, the AFE5801 includes an 8-channel variable-gain amplifier (VGA) and an 8-channel, 12bit, high-speed analog-to-digital converter (ADC) based on a switched capacitor design. Again, since our design only uses a single element transducer and makes a 1-D measurement, only one of these channels is implemented, while pin-outs of other channels are either grounded or left floating. National Semiconductor provides a similar option for a variable gain amplifier and data sampling chip in its LM96511 offering. However, we deemed its 376-pin BGA configuration too complicated for our circuit design given the soldering complexity compared to other surface mount packages, like the AFE5801's QFN package. A pin assignment schematic and construction of our AFE5801 breakout board is provided in Figures 8 and 9 of Appendix A.4.

Programming the modes of operation for the AFE5801 occurs over a Serial Peripheral Interface bus and is controlled by the FPGA. Upon power-up, the chip's internal registers are initialized to the default (zero) value by applying a positive pulse to the Reset pin. The SPI bus is formed by the following pins: (SEN)', SCLK, SDATA, and RESET. Serial shifting of bits on the SDATA line into the device occur when (SEN)' is set to low. Input bits on the SDATA line are latched on rising edges of SCLK, loading a new instruction to completion on every 24th rising edge. The first 8 of the 24 bits comprise of a register address, while the remaining 16 comprise of the data to be loaded onto the addressed register. Figure 10 below illustrates this process:

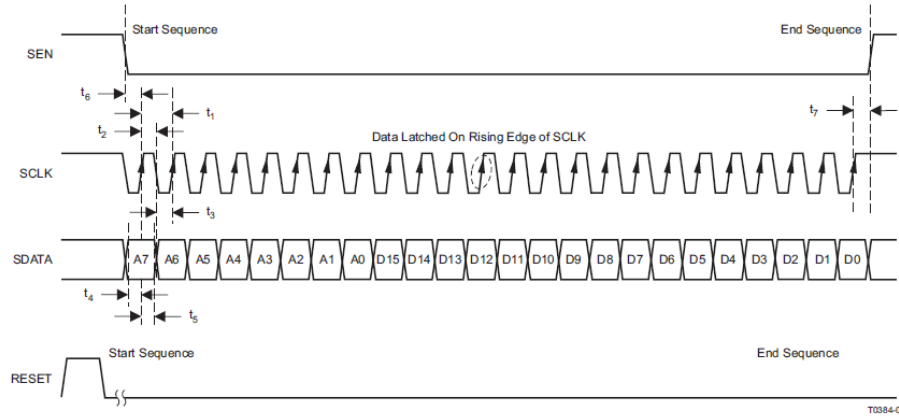

**Figure 10. Timing Diagram for AFE Serial Data Protocol [5]**

Internal registers are divided into two groups: general-purpose registers and gain control operation registers. Access to gain control registers is granted when bit 2 of address zero (labeled "TGC\_REGISTER\_WREN" is set to 1. Various modes of operation are adjusted in this way. A "TGC calculator" document accompanying the AFE chip helped specify register values for correct time gain curve application [5]. Table 1 in Appendix A.4 lists register configurations that were deemed necessary to achieve correct operation of the AFE.

On the output end of the AFE, sampled data from ADC is sent to the FPGA using Low Voltage Differential Signaling (LVDS). The LVDS output is sent out to the FPGA on pins D1P/M, along with LVDS frame clocks FCLKP/M and bit clocks DCLKP/M. In order to properly convert the analog input from the amplifier side of the chip to digital data, the sampling rate of our ADC can simply be calculated at the Nyquist Rate:

$$f_N = 2B = 2(10\text{MHz}) = 20\text{MHz} = 20\text{MSPS} \quad (1)$$

Achieving this data rate for the 10MHz probe operating frequency ensures a resolution of 0.075mm, well below our target accuracy of 0.1mm. Since our anti-aliasing filter will not attenuate signals above 10MHz perfectly, the next highest sampling rate is chosen instead (25MHz). Since each sample is 12 bits in resolution, the actual output data rate equals 300Mbps – necessitating the use of an FPGA with LVDS to buffer data [6].

## 2.5 FPGA

The Altera Cyclone III is a powerful Field-Programmable Gate Array (FPGA) featuring 10,320 Logic Elements. Its 144 pins are divided into three sections below by function, and the communication protocol with the iPhone is discussed.

### 2.5.1 Power

Four different DC voltage levels power the FPGA: 1.2V, 1.8V, 2.5V, and 3.3V. All supplies have 0.1uF capacitors connected to ground to filter out any AC noise. Internal logic voltages (VCCINT) and PLL digital power (VCCD\_PLL) are all set to 1.2V. PLL analog power (VCCA) and I/O Bank 2 (VCCIO2) are set to 2.5V. I/O Bank 2 handles communications with the AFE over Low-voltage Differential Signaling (LVDS), a high-speed communication protocol requiring 2.5V supply. I/O Bank 3 (VCCIO3) is set to 1.8V, the logic level used for serial communication with the AFE. All other I/O bank supplies are set to 3.3V. VREF pins are not used and tied to ground. The power pin assignment schematic is provided as Figure 11 in Appendix A.5.

### 2.5.2 I/O

The FPGA features eight I/O banks, five of which are utilized for our circuit. I/O Bank 1 is used solely for sending a control signal (ASDI) to the serial programming device to read out configuration data. I/O Bank 2 accepts LVDS waveform data from the AFE. A 100Ω resistor is connected between the positive and negative leads of the differential signal as recommended by Altera for signal stability. 25Ω pull-up and pull-down resistors are connected to RUP and RDN to enable on-chip termination, which improves signal clarity. I/O Bank 3 handles serial programming of the AFE using one input (AFE SDATA) and three outputs (AFE SELECT, AFE RESET, and AFE SOUT). I/O Bank 4 has two outputs: the 10MHz pulsing signal (Pulser CTRL) and an LED to indicate if a scan is in progress. I/O Bank 5 is unused. I/O Bank 6 is unused except for a required connection to 3.3V across a 10k resistor. I/O Bank 7 transmits and receives data from the iPhone. I/O Bank 8 is unused. The I/O pin assignment schematic is provided as Figure 12 in Appendix A.5.

### 2.5.3 Programming and Clocks

An ASV-30.000MHZ-EJ-T oscillator is used as a 30MHz clock for the FPGA and AFE ADC. This is the primary clock for the FPGA and I/O Bank 1. I/O Bank 2 receives two clock signals from the AFE to synchronize LVDS communication: a frame clock and bit clock. An Altera EPCS16 chip serves as the interface for Active Serial (AS) non-volatile programming of the FPGA. The chip can be programmed using Quartus II software and a Serial-USB Blaster cable, which connects to a 10-pin male connector on the board. Per Altera recommendations, 10k resistors are connected serially with voltage sources and a 25Ω resistor is connected serially on the DATA line. See [7] for the connection guide between the FPGA and EPCS16. The programming and clock pin assignment schematic is provided as Figure 13 in Appendix A.5. Four changes made since the Design Review are included in Figure 13: rearranging of the SerialUSB Port's pin locations, connecting nStatus only to 3.3V through a 10k resistor, connecting Vcc to the EPCS16 and ASV30Mhz *ahead* of their respective 10k resistors, and connecting Conf\_Done separately to 3.3V through a 10k resistor and to AS pin 2.

### 2.5.4 FPGA Software

VHDL code loaded onto the FPGA enables the desired functionality of: accepting iPhone scan commands and changing the scan state accordingly, sending out 3.3V logic level 50ns pulses to the HV pulser, accepting and



buffering LVDS scan data to memory, and reading the buffered memory out to the iPhone. The system clock is fed into a fractional clock divider that generates a clock signal at 16 times the chosen iPhone communication baud rate. This clock, along with the input from the iPhone, is fed into the Manchester decoder block where the data is deserialized. The received data then goes into the message decoder block where each received byte is interpreted to be a start or stop command. On the data sending side, scan data is read from a scan memory block sequentially every time a pulse command is generated. The data at each address and a ready bit is sent to the Manchester encoder block where the data is serialized for output to the iPhone [8].

### 2.5.5 iPhone Communication

Data is sent to and from the iPhone over the headphone audio jack using a Manchester encoded signal. Manchester encoding allows for digital encoding with a sinusoidal analog signal. A positive voltage represents digital “1”, and negative voltage represents digital “0”. Since a long string of 1s or 0s would saturate the audio channel, each bit is encoded using a complete AC cycle as either “01” for 0 or “10” for 1. Data is transmitted according to the UART protocol in 10 bit packets, including 1 data byte, 1 start bit, and 1 stop bit. A test signal was generated from the iPhone and probed with an oscilloscope as shown below. This shows transmission of x02 with a start bit 1 and stop bit 0. When no data is being sent, the UART line is high and represented by a long string of 01s. The start bit creates a double baud length 1 pulse, resynchronizing the receiver with the incoming data byte. iPhone code libraries to produce and receive Manchester encoded audio are provided by University of Michigan’s Project HiJack [9]. This communication protocol was chosen for its simplicity over Bluetooth and Wi-Fi, and due to the inaccessibility of the iPhone’s USB data protocol.

 


Figure 14. Sample Manchester Encoded x02 from iPhone Left Audio

#### Data Rate

The limiting factor for data transmission rate is the iPhone’s audio sampling rate of 44.1 kHz, corresponding to 22.05 kbaud in Manchester encoding. The calculation below shows what this corresponds to in kB/sec.


$$Rate = \frac{(22.05 \text{ kBaud})(0.8 \text{ data in a packet})}{8 \text{ bits/byte}} = 2.205 \text{ [kB/sec]} \quad (2)$$

The faster data is transmitted the higher the likelihood of dropped bits, so a safer data rate of 4900 baud (0.49 kB/sec) is chosen. This data rate corresponds to the ability to send nearly 1 ultrasound image per second to the iPhone. Calculations for the size of one ultrasound image are below.

$$Samples \text{ per image} = \frac{30 \text{ mm axial length}}{.05 \text{ mm desired resolution}} = 600 \left[ \frac{\text{samples}}{\text{image}} \right] \quad (3)$$


$$Image\ Size = \left(600 \frac{samples}{image}\right) \left(1 \frac{bytes}{sample}\right) = 0.6\ [kB/image] \quad (4)$$

#### *Sending Data from the iPhone*

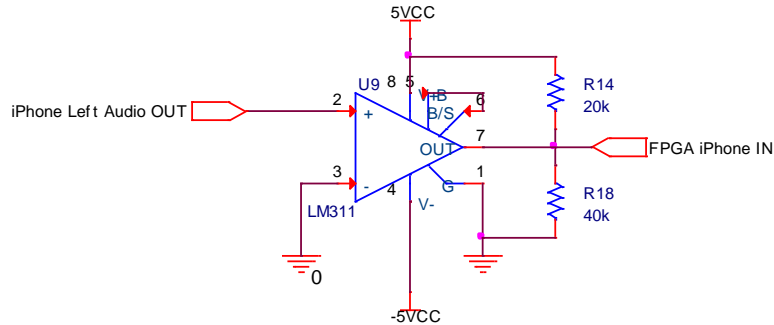


**Figure 15. iPhone Receiver Circuitry**

The Manchester encoded AC data signal is generated on the iPhone's left audio channel at a maximum  $V_{pp}$  of 2.76V. This signal must be converted to a digital signal with 3.3V logic before entering the FPGA. To accomplish this, an LM311 comparator is used with a  $V_{ref} = 0V$  to convert positive voltages to 3.3V and negative voltages to 0V. A simple voltage divider at the output regulates the 5V chip supply to 3.3V. This chip replaces the LMV331 specified in the design review as the LMV331's output voltage was too low to be used as logic input. Simulation of this circuit operating is shown below with the analog input sinusoid in green and digital output signal in red.

 

**Figure 16. iPhone Receiver Circuitry PSpice Simulation**

#### *Sending Data from the FPGA*

 


**Figure 17. iPhone Transmission Circuitry**

Manchester encoded data from the FPGA is a digital signal at 3.3V logic and must be converted to an AC signal. The signal will be received by the iPhone's microphone input, which expects AC signals with no DC offset and  $V_{pp}$  of less than 20mV. The 10uF capacitor in series AC couples the DC signal, and the two resistors attenuate the incoming signal using the voltage divider rule. The 1k resistor in parallel is necessary for the circuit to be recognized as a microphone input by the iPhone.

$$V_{pp, out} = \frac{(V_{pp, in})(R1)}{R1 + R2} = \frac{(2.76V)(1k)}{1k + 220k} = 12.5 [mV] \quad (5)$$

Simulation of this circuit is shown below with a 3.3V logic signal input in green and attenuated, AC coupled signal output in red.

 

**Figure 18. iPhone Transmission Circuitry PSpice Simulation**

## 2.6 iPhone Software

The device's corresponding iPhone application is written in Objective-C using the iPhone 5.1 SDK. Since the circuit communication protocol is over the audio jack, this application can operate on any iOS device. While an Android or Windows phone application could foreseeably be written for our project, iOS was chosen for this project since no ultrasound application existed on the platform at the time. The application serves a variety of purposes, including: cataloguing patient identification and scan data, initiating new scans, viewing scans and calculating eye measurements, exporting scan data, and performing IOL calculations. A navigation style XCode storyboard is utilized to lay out the application's views, provided as Figure 19 in Appendix A.6. Each view requires its own view controller class, to be instantiated when its view is displayed. The initial view is a list of patients, from which the user can select a patient, search for a patient, or add a patient. Selecting or adding a patient will bring up a details view. This allows the user to edit the patient's name, date of birth, and eye type. Here the user can also start a new scan or access saved scans for the left or right eye. Starting a new scan displays a view containing a graph of the current data, live measurements from the scan, a stop button, and a save button. The user can repeatedly press the save button to capture the current scan data or press the stop button and return to the details view. At the saved scans view, the user can scroll through saved scans, email the currently displayed scan, open the currently displayed scan image in another program, or delete scans. Most importantly, pressing the IOL Calculator button pulls up a view where the user can calculate required lens power from the currently displayed scan. Many different IOL formulas exist, including the Holladay, Haigis, SRK/T, and HofferQ. This application uses the SRK II formula [10], both for its simplicity and general-purpose use. Given in Equation 6, the formula takes into account axial length  $L$ , corneal refractive power  $K$ , and lens constant  $A$ .  $K$  is found using a keratometer instrument,  $A$  is selected in the application from a list of implantable lenses, and  $L$  is automatically entered for the scan selected. In the SRK II formula,  $A$  changes not only based on the lens but by the axial length as well.

$$P = A - 0.9K - 2.5L \quad (6)$$

Several other classes handle data and background tasks. The HiJack class encodes and decodes Manchester audio signals for use within the application. The Sparkline class [11] handles drawing the scan graphs as they are updated by incoming data. The AppDelegate class generally acts as the central class for the application, passing data between view controllers and dealing with system notifications.

## 2.7 Power Electronics

A single 9-volt battery, the Energizer LA522 in particular, provides power to our device's front-end circuitry. Due to the relative complexity of this circuitry, nine different voltage levels require regulation: +30V, +10V, -10V, +5V, -5V, +3.3V, +2.5V, +1.8V, and +1.2V. The hierarchy below describes how these levels will be achieved.

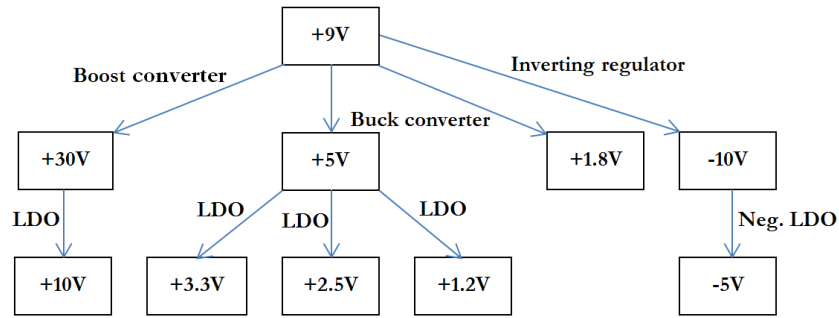


Figure 20. Power Electronics Hierarchy

The above approach was taken for several reasons:

- Boost converters, buck converters, and inverting regulators require more area and components than linear regulators, but they provide better power conversion efficiency
- The analog front end's high-speed ADC (+1.8V) pulls a significant amount of current compared to the other components, so we wanted to achieve high conversion efficiency for that voltage level, in particular
- We couldn't find a suitable LDO to regulate +1.2V from a +1.8V supply, so we chose one that regulated from a +5V supply, instead

In order to maximize battery life while maintaining a relatively small form factor, we chose to implement a scheme that would provide a fair tradeoff between area and energy efficiency. Furthermore, to estimate the power drawn from our front-end circuitry, we examined each component's data sheet and made conservative approximations of current draw. These estimates are summarized in the table below.

Table 2. Current Draw from Device Components

	+30V	+10V	-10V	+5V	-5V	+3.3V	+2.5V	+1.8V	+1.2V
<b>FPGA [8]</b>	-	-	-	-	-	10mA	17mA	-	41mA
<b>Analog Front End [9]</b>	-	-	-	-	-	9mA	-	220mA	-
<b>T/R Switch [10]</b>	-	-	-	7mA	7mA	0.05mA	-	-	-
<b>Transmit Pulser [6]</b>	6mA	30mA	0.2mA	-	-	0.1mA	-	-	-
<b>Total</b>	6mA	30mA	0.2mA	7mA	7mA	19.15mA	17mA	220mA	41mA

Using this information, the following calculations were made:

Approximate power drawn by major components:

$$P_{\text{comp}} = \sum_i |V_i| \times I_i \approx 1,103\text{mW} \quad (7)$$

Approximate power dissipated in LDOs:

$$P_{\text{LDO}} = \sum (|V_H| - |V_L|) \times I_L \approx 866\text{mW} \quad (8)$$

Approximate power dissipated in other converters (assume 70% efficiency):

$$P_{\text{conv}} = \sum (1 - 0.7) \times |V_L| \times I_L \approx 591\text{mW} \quad (9)$$

Approximate total power drawn from 9V battery source:

$$P_{\text{total}} \approx P_{\text{comp}} + P_{\text{LDO}} + P_{\text{conv}} = 2,560\text{mW} \quad (10)$$

When drawing 500mA, the capacity of an Energizer LA522 is about 750mAh and operates at 7V [12]. Given this information, the ultrasound device can last

$$t_{\text{life}} = \frac{Q_{\text{capacity}} V_{\text{operating}}}{P_{\text{total}}} \approx 2.1 \text{ hours} \quad (11)$$

Two hours of battery life seems reasonable, considering that it's a portable ultrasound device which would typically require a larger, rechargeable battery. In addition, it's worth emphasizing that these calculations were fairly conservative.

As indicated in the voltage regulation tree above, the power electronics module consists of nine voltage converters and regulators. At the time of our design review, we had selected converters and regulators to be ordered online. Soon after the review, however, we found different ones that were much more appropriate for our project. Specifically, the ECE Parts Shop carries a configurable DC/DC converter that can serve as a boost, buck, or inverting converter, depending on how the external components are wired. Additionally, this IC comes in a DIP package, making it very easy for bread board prototyping. We also found much simpler voltage regulators that provide a fixed voltage output and merely require input and output decoupling capacitors.

The following devices are an updated list of the power electronics ICs we employed in our design:

- TL497ACN configurable boost, buck, inverting DC/DC converter [13]
- KA78L10AZTA +10V fixed positive voltage regulator [14]
- MC79L05ACPG -5V fixed negative voltage regulator [15]
- MCP1700-3302E/TO +3.3V fixed positive voltage regulator [16]
- MCP1702-1202E/TO +2.5V fixed positive voltage regulator [16]
- MCP1700-2502E/TO +1.2V fixed positive voltage regulator [16]

Appendix A.7 provides detailed design procedures related to the power electronics circuit.

## 3 Design Verification

### 3.1 DGH Ultrasound Probe

In order to verify the proper operation of our T/R switch, we tested the TX810 under the conditions prescribed by the power electronics requirements and verifications. First, we must ensure that the fixation LED lights up, provided that it receives 3.3V with a series 100 Ohm resistor to limit the LED bias current. We observed that the LED correctly lit up in this configuration.

Next, we measured the input impedance of the transducer probe. The datasheet of the transducer probe, given to us by DGH, did not provide information regarding the input impedance of the probe at 10MHz. This information is important because it determines the maximum current that the probe will draw during a nominal 30V, 10MHz pulse. In order to find this, we set up a test bench in which a pulse generator sends 50ns-wide pulses to the transducer probe with a period of 5ms. We placed a 50.15Ω resistor in series for current measurement, and employed an oscilloscope to measure voltage drops across the resistor and transducer probe. The test setup is illustrated in Figure 25 below.

 


Figure 25. Probe Input Impedance Test Setup


Upon generating a 50ns-wide pulse, the voltage across the resistor measured 3.625V and the voltage across the probe measured 4.000V. According to Ohm's Law, the current through this system calculates out as:

$$I = \frac{V_R}{R} = \frac{3.625 [V]}{50.15 [\Omega]} = 72.3 [mA] \quad (36)$$

and the impedance of the transducer probe at its nominal operating frequency calculates as:


$$Z_P = \frac{V_P}{I} = \frac{4.000 [V]}{72.3 [mA]} \cong 55 [\Omega] \quad (37)$$

Moving forward, we verified the focus and frequency of operation for the DGH transducer probe with the help of Prof. William O'Brien's group at the University of Illinois Bioacoustics Research Laboratory. The equipment we used there included an Olympus Panametrics 5900 Pulser/Receiver, Labview DAQ system, an ultrasound tank, and a probe clamp on an actuating stepper motor. The setup for our testing is shown in the figure below, followed by test results.

 


**Figure 26. Probe Nominal Frequency and Focus Test Setup**

With research assistant Michael Kurowski's help, we determined that the nominal operating frequency occurred at 10MHz as expected.

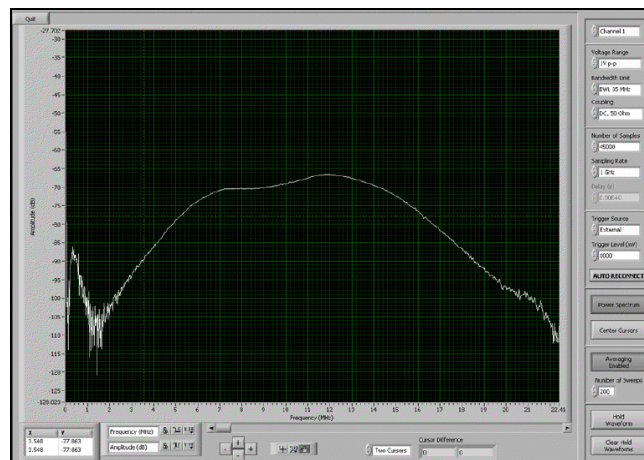

**Figure 27. Transducer Probe Bode Plot**

We also tested the depth of focus of the probe and found that the optimum focus occurred at 23mm.

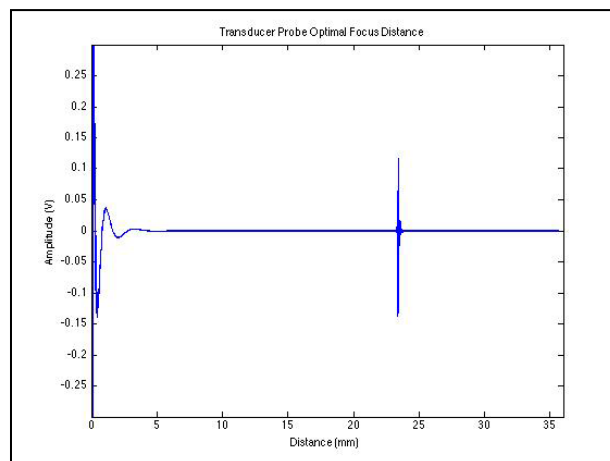

**Figure 28. Transducer Probe Focus**

### 3.2 T/R Switch

In order to verify the proper operation of our T/R switch, we tested the TX810 under the conditions prescribed by the power electronics requirements and verifications. Specifically, upon receiving a high voltage input signal at the channel 0 input pin, the channel 0 output pin must yield an analogous signal, scaled down to within 2 Vpp. We achieved the required input by configuring the Maxim Pulser to generate 50ns-wide, 23V pulses every 1 ms. The high-voltage output pin of the pulser and input of T/R switch shared a transmission line connection with the input of the transducer probe. Both the input and output of the T/R switch were captured using an oscilloscope. The test setup described is illustrated below in Figure 29, followed by test results.

 


Figure 29. TX810 Test Setup

 


Figure 30. High Voltage Input Pulse to TX810

 


Figure 31.  $<2V_{pp}$  Output Pulse from TX810

### 3.3 Transmit Pulser

In order to verify the proper operation of our transmit pulser, we tested the MAX4940 under the conditions prescribed by the power electronics requirements and verifications. Specifically, upon its digital input pulse pin receiving a 50ns-wide, positive pulse at logic-level voltage, its high-voltage output pin must generate a 50ns-wide, positive pulse at +30V. This required input was achieved by configuring the FPGA to generate 50ns-wide digital pulses every 5ms. The high-voltage output pin of the pulser was connected to the input of the transducer probe. Both the input and output of the pulser were captured using an oscilloscope. The test setup described is illustrated below in Figure 32, followed by test results.



 


Figure 32. Transmit Pulser Test Setup

 


Figure 33. Digital Input Pulse to MAX4940

 


Figure 34. High-voltage Output Pulse from MAX4940

As evident in Figure 33, the FPGA correctly sends a 50ns-wide pulse at logic-level voltage to the transmit pulser about every 5ms. At the output, Figure 34 shows that the MAX4940 correctly generates +30V, 50ns-wide pulses with the same periodicity. These results verify that the transmit pulser operates correctly.

### 3.4 Analog Front End

In order to verify the proper operation of our AFE chip, we tested the AFE5801 under the conditions prescribed by the power electronics requirements and verifications. Specifically, the SPI communications bus must have a logic level high between 1.4-3.6V and logic level low less than 0.8V. In addition, data sent over the SDATA line must correctly latch on the rising edge of SCLK and be correctly framed within the SEN signal.

The test setup described is illustrated below in Figure 35, followed by test results.

 


Figure 35. AFE SPI Verification Setup

As shown in the Figure 36 below, we were able to verify that SPI data lines were sending correct programming sequences at a 3.3V logic level and were being correctly latched and framed.

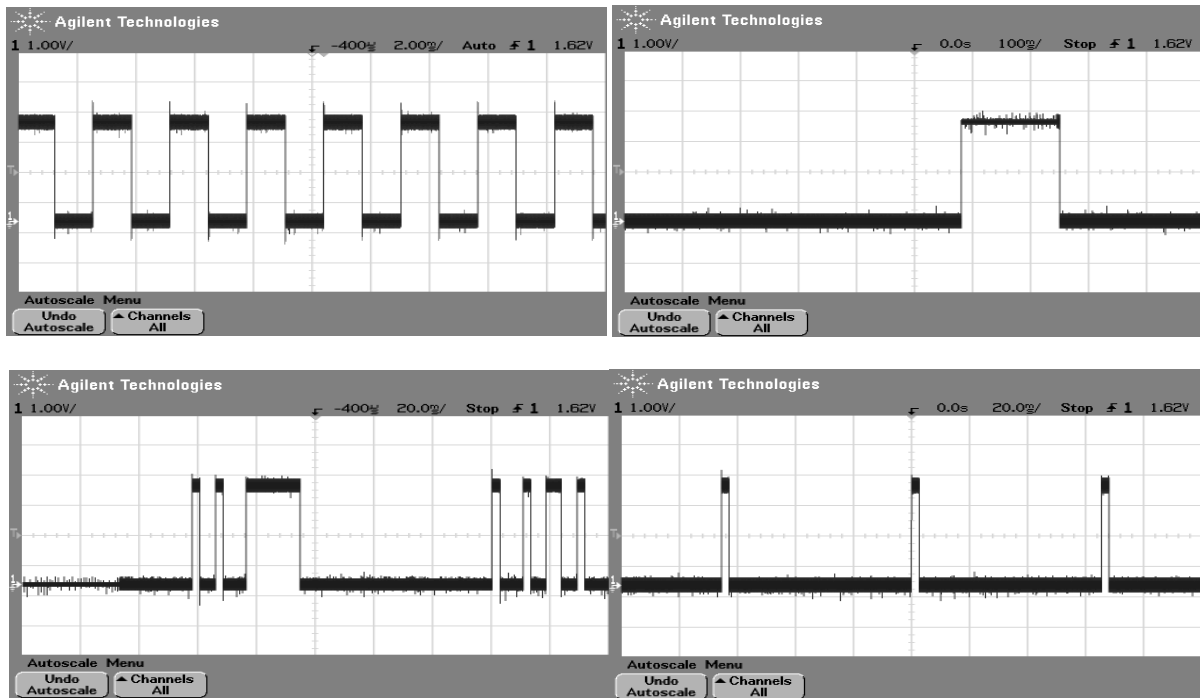


Figure 36. AFE SPI Programming Verification. SCLK (top left); SRESET(top right); SDATA (bottom left); SEN (bottom right)

We were also able to verify that the AFE's internal memory TGC registers were getting programmed by sending the appropriate commands to read the register contents for any chosen address. We observed this data on the SDOOUT line and displayed in hexadecimal format onto the Altera DE2 FPGA Development Board's 7-segment display.

As for the digitized output signal from the AFE's analog to digital converter, we tasked ourselves with verifying that the LVDS output had a common mode output voltage of 0.9-1.5V and transmitted data at 25MSPS. We applied 2Vpp pulses at the input pin of channel 1 of the AFE, applied no particular gain on the AFE's Variable Gain

Amplifiers, and observed a differential, digitized signal at the output pin of channel 1 on the AFE. The test setup is shown below, followed by the test results:

 


Figure 37. AFE LVDS Output Verification Setup

Observing the output data on an oscilloscope, we verified that the output data transmitted differentially at a low voltage of 1.12V. We placed each differential output pin on a separate oscilloscope channel, and used the oscilloscope's math functionality to observe the overall differential output signal. To verify bit rate, we used cursors to count the number of low bits and high bits within a 50nS window.

 


Figure 38. AFE LVDS Output Verification

We counted 15 bits in such a window. Given that each sample is comprised of 12 bits for our AFE chip, we verified that we were correctly achieving a data rate at about 25MSPS, according to our calculations:

$$Data\ Rate = \frac{15\ bits}{50 \times 10^{-9}\ sec} \times \frac{sample}{12\ bits} = 25MSPS \quad (38)$$

### 3.5 FPGA

Our FPGA PCB was fabricated by the ECE parts shop and tested. The board's pin assignment schematic and construction are provided as Figures 39 and 40 in Appendix A.5. Despite many small modifications in numerous attempts to make the board operational, complete functionality of the board was not obtained. Requirement 1 was verified by connecting an oscilloscope at the output of the 30MHz oscillator and observing its frequency and amplitude. Though the signal was quite noisy and included 60Hz components from the wall power, 30MHz components were detected. Requirement 2 was verified by attempting to load the EPCS16 memory with a test program and having Quartus II verify that the program contents were correctly written. Unfortunately, the Cyclone III was unable to program itself from the EPCS16 upon startup. The nCSO bit on the FPGA should have been pulled low to initialize configuration, but this never occurred. The possible reasons for this issue are plentiful, and it was decided that an Altera DE2 board would be used instead to verify remaining requirements. Without the Cyclone III and its LVDS inputs, Requirement 3 could not be verified. For requirement 6, an oscilloscope was connected to the PULSE control signal output and verified to be 50ns wide and 3.3Vpp. Requirements 4 and 5 were verified in conjunction with iPhone requirements 2 and 3. The DE2 was connected to the iPhone via audio cable, and a scan

was initiated by the iPhone. This triggered the FPGA to repeatedly read and send data from a memory buffer of manually entered scan data to the iPhone. An LED verified the correct scan state on the DE2, and the Xcode console correctly read the data received from the FPGA.

### 3.6 iPhone Software

All requirements for the iPhone software were verified. At the time of demo, the device was fully charged to fulfill requirement 1. As described in Section 3.5, Requirements 2 and 3 were verified in conjunction with the FPGA. Requirement 4 covers smaller features of the user interface, which were all manually verified on the device. For requirement 4e, MMS of a scan image must be done after the scan image is saved to the user's camera roll on the iPhone. It is an iPhone SDK limitation that an MMS cannot be sent directly from a 3<sup>rd</sup> party application. For requirement 4f, the ability to select "phakic" or "aphakic" for eye type eliminates the need for a separate "change sound velocity" button, as selecting eye type is preferred to entering a sound velocity manually.

### 3.7 Power Electronics

In order to verify the proper operation of our power electronics module, we tested each component under the conditions prescribed by the power electronics requirements and verifications. Specifically, the output voltage of each converter and regulator must remain within 5% of its nominal value throughout a DC input voltage sweep from 6.5V to 9.5V. This specific range of input voltages was chosen because a 9V battery can provide anywhere between 6.5V and 9.5V, depending on its charge [12]. The test setup is illustrated below in Figure 41.

 


Figure 41. Power Electronics Test Setup

Essentially, we connected a tunable DC power supply to the input of the power electronics module and probed the output of each converter and regulator with a digital multimeter. The output values were recorded and verified for tolerance satisfaction. The test results are provided in Table 3 below, and they verify that each component of the power electronics module correctly regulates its nominal voltage level.

Table 3. Power Electronics Test Results

Component	Nominal Voltage (V)	Min. Voltage (V)	Max. Voltage (V)	Max. Error
Boost converter	+30.00	+31.40	+31.40	4.7%
Buck converter	+5.00	+5.17	+5.17	3.4%
Buck converter	+1.80	+1.80	+1.80	0.0%
Inverting converter	-10.00	-10.11	-10.10	1.1%
Positive regulator	+10.00	+10.09	+10.09	0.9%
Positive regulator	+3.30	+3.32	+3.32	0.6%
Positive regulator	+2.50	+2.53	+2.53	1.2%
Positive regulator	+1.20	+1.22	+1.22	1.7%
Negative regulator	-5.00	-4.98	-4.98	0.4%

## 4 Costs

### 4.1 Parts

**Table 4. Cost of Parts**

Part	Manufacturer	Qty.	Retail Cost (\$)	Bulk Purchase Cost (\$)	Actual Cost (\$)
iPhone 4S (without contract)	Apple	1	699.00	699.00	0.00
iOS Developer License (1-year)	Apple	1	99.00	99.00	99.00
LM311	National Semiconductor	1	0.26	0.12	0.00
EP3C10E144	Altera	1	19.20	19.20	19.20
EPCS16	Altera	1	14.75	14.75	14.75
JTAG Cable	Altera	1	12.99	12.99	12.99
ASV-30.000MHZ-EJ-T	Abricon	1	2.89	0.84	2.89
SJ-43514-SMT 4-pole female jack	CUI	1	1.47	0.43	1.47
CP-35401SP-ND 3.5mm plug	Conn	2	2.80	1.12	2.80
TL497ACN	Texas Instruments	4	2.02	0.81	0.00
KA78L10AZTA	Fairchild Semiconductor	1	0.10	0.10	0.10
MC79L05ACPG	ON Semiconductor	1	0.58	0.14	0.58
MCP1700-3302E/TO	Microchip Technologies	1	0.44	0.28	0.44
MCP1702-1202E/TO	Microchip Technologies	1	0.52	0.36	0.52
MCP1700-2502E/TO	Microchip Technologies	1	0.44	0.28	0.44
MAX4940CTN+	Maxim Integrated Products	1	15.19	15.19	0.00
LA522	Energizer	1	10.00	5.00	9.81
AFE5801	Texas Instruments	1	48.40	48.00	0.00
TX810	Texas Instruments	1	7.68	7.68	0.00
Probe 6000	DGH Technologies	1	699.99	699.99	0.00
<b>Total</b>			<b>1646.58</b>	<b>1628.83</b>	<b>168.38</b>

### 4.2 Labor

**Table 5. Cost of Labor**

Person	Ideal Salary/Hour (\$)	Actual Hours Spent	Labor (x2.5) (\$)
Jonathan Adam	40	240	24,000
Adam Keen	40	240	24,000
Dean Santarinala	40	240	24,000
<b>Total</b>	<b>120</b>	<b>720</b>	<b>72,000</b>

## 5 Conclusion

### 5.1 Accomplishments

Despite our project not attaining full functionality, we are quite pleased with the progress made towards a marketable iPhone Ultrasound system. Overall, we saw that it is feasible to use a 9V battery to power the entire system and expect reasonable battery life of over two hours. We proved that an iPhone could control circuitry to provide pulses to an ultrasonic transducer, and received high-speed digital data from its echo pulses. While unable to check the validity of this data, we modeled an FPGA buffering this data by manually creating a memory bank of scan data. On each pulse command, we could read this data onto the iPhone and display it to the screen. We are also extremely pleased with the full functionality of our iPhone application. The project as a whole demonstrates the feasibility of an iPhone controlled and monitored ultrasound device that could be compacted into a handheld form factor.

### 5.2 Uncertainties

Upon completion of the spring 2012 semester, we look back at our ambitious ultrasound product and find a few incomplete deliverables. Because of the modular nature of our design and testing, we had a relatively simple time rooting out any unresolved issues with our circuitry. Our overall signal data-path remains incomplete with our failure to deliver a programmable and working Altera Cyclone III FPGA board. The inoperable nature of our Cyclone III FPGA remains unknown but a few possible sources of error exist in incorrect board capacitances, suboptimal board layout, or a variety of other problems. Because of this, and the lack of time to implement a backup digital to analog converter (DAC), we were left unable to verify the LVDS output of our AFE chip. Time permitting, we would use a DAC to verify that the input signal of the AFE was being amplified according to the TGC curve and digitized without any bit errors.

With this important data link left incomplete, the overall operation of our ultrasound project is still only theoretically possible given that all the other modular blocks work correctly. After fixing this disconnect in our circuit, more testing and design work would be required to optimize the time gain compensation curve to sync with the returned echo pulses from our transducer. Also, the timing required to send control pulses from the FPGA to individual chips would also require some fine-tuning.

### 5.3 Ethical considerations

Because the end-goal of this device is for medical uses, there are many ethical points we must consider in its design. The following portions of the IEEE Code of Ethics are especially pertinent to our project:

1. "to accept responsibility in making decisions consistent with the safety, health and welfare of the public, and to disclose promptly factors that might endanger the public or the environment;"

Though a-scan ultrasound probes are non-invasive when used properly, incorrect operation or a faulty probe could potentially cause damage to the eye. Special care must be taken to ensure our device is not used on humans until approved by the FDA, and only operated by trained physicians after FDA approval. The probe circuitry must also be designed to emit sound waves within amplitude and frequency limits.

2. "to avoid real or perceived conflicts of interest whenever possible, and to disclose them to affected parties when they do exist;"

Since we are using a donated probe from DGH Technologies, it is important we avoid discussing our project with other medical companies to avoid conflicts of interest.

3. “to be honest and realistic in stating claims or estimates based on available data;”

Our device’s tested performance metrics must be stated clearly and not exaggerated to ensure physicians know what to expect from our device.

9. “to avoid injuring others, their property, reputation, or employment by false or malicious action;”

Our device’s intent is not malicious, but rather potentially beneficial for several groups. We will not falsify any information regarding the device that may lead to personal injury.

## 5.4 Future work

In retrospect, there are many things we would've done differently this semester. To start, we should have taken a bit more time at the beginning to fully understand our system design. This would have been particularly helpful in providing us an earlier realization of the need for an FPGA (or other high-speed controller) on our front-end circuit. Instead, this conclusion wasn't reached until almost a month into the semester, when Mustafa suggested we consider the feasibility of achieving our expected data rates. Designing and fabricating our own breakout boards from the beginning is another major thing we would have done differently. Due to the QFN packing of our front-end ICs, we required breakout boards for modular testing of each component. The universal QFN breakout boards we ordered online were horrendous, and we invested a great deal of effort to make them work. After a long struggle, we decided to simply design our own, and they worked out wonderfully. One last thing we would have done differently would be to order backup components at the same time as our first options. For the transmit pulser, in particular, we had to wait a few days for the MAX4940 to arrive in the mail, after finally giving up on the LM96550.

If we had more time to continue working on this project, we would first debug and test the component of the project that did not reach completion: the LVDS data link between the AFE and FPGA. After that, we would move forward to transform our working prototype into a polished product. In order to enable the LVDS data link, we would need to finish debugging our FPGA board's inability to correctly flash the FPGA from the serial programmer. With an operational FPGA board, we would be able to collect and decode the LVDS data from the AFE. After verifying correct output from the AFE, we would design a single PCB for the entire front-end circuitry to achieve a smaller form factor. Finally, we would optimize the time-gain control amplification of the AFE and synchronize the sample buffer timing of the FPGA.

## References

- [1] S. Byrne, R.Green, "Axial Eye Length Measurements," Ultrasound of the Eye and Orbit, 2nd ed., Ed Philadelphia: Mosby, p. 250, 2002.
- [2] DGH6000 Scanmate A Transducer Data Sheet. DGH Technology Inc., Pennsylvania.
- [3] TX810 Data Sheet. Texas Instruments Inc., Texas. [Online] Available: <http://www.ti.com/lit/ds/symlink/tx810.pdf>
- [4] MAX4940 Data Sheet. Maxim Integrated Products, California. [Online] Available: <http://datasheets.maxim-ic.com/en/ds/MAX4940-MAX4940A.pdf>
- [5] AFE5801 and AFE5851 TGC Calculator. Texas Instruments Inc., Texas. Program documentation. Vers. 1.0. [Online] Available: <http://www.ti.com/litv/zip/sloc145>
- [6] AFE5801 Data Sheet. Texas Instruments Inc., Texas. [Online] Available: <http://www.ti.com/general/docs/lit/getliterature.tsp?genericPartNumber=afe5801&fileType=pdf>
- [7] Serial Configuration (EPCS) Devices Datasheet. Altera Inc., California. [Online]Available: [http://www.altera.com/literature/hb/cfg/cyc\\_c51014.pdf](http://www.altera.com/literature/hb/cfg/cyc_c51014.pdf)
- [8] Manchester Encoder-Decoder for Xilinx CPLDs. Xilinx Inc., California. [Online] Available: [http://www.xilinx.com/support/documentation/application\\_notes/xapp339.pdf](http://www.xilinx.com/support/documentation/application_notes/xapp339.pdf)
- [9] Hijacking Power and Bandwidth from the Mobile Phone's Audio Jack. Kuo, Verma, et. al. [Online] Available: <http://www.eecs.umich.edu/~prabal/pubs/papers/kuo10hijack.pdf>
- [10] W. Haigis. "IOL Calculation Using the SRK II Formula." [Online] Available: <http://www.augenklinik.uni-wuerzburg.de/uslab/ioltxt/srk2e.htm>
- [11] CKSparkline iOSLibrary. Connex Key Solutions. [Online] Available: <http://key-solutions.ca/cksparkline.html>
- [12] Energizer LA522 Data Sheet. Energizer, Missouri. [Online] Available: <http://data.energizer.com/PDFs/la522.pdf>
- [13] TL497ACN Data Sheet. Texas Instruments Inc., Texas. [Online] Available: <http://www.ti.com/lit/ds/symlink/tl497a.pdf>
- [14] KA78L10AZTA Data Sheet. Fairchild Semiconductor, California. [Online] Available: <http://www.fairchildsemi.com/ds/KA/KA78L05A.pdf>
- [15] MC79L05ACPG Data Sheet. ON Semiconductor, Arizona. [Online] Available: [http://www.onsemi.com/pub\\_link/Collateral/MC79L00-D.PDF](http://www.onsemi.com/pub_link/Collateral/MC79L00-D.PDF)
- [16] MCP1700-3302E/TO, MCP17021202E/TO, MCP1700-2502E/TO Data Sheet. Microchip Technology, Arizona. [Online] Available: <http://ww1.microchip.com/downloads/en/DeviceDoc/21826b.pdf>
- [17] EP3C10E144 Data Sheet. Altera Inc., California. [Online] Available: [http://www.altera.com/literature/hb/cyc3/cyc3\\_ciii52001.pdf](http://www.altera.com/literature/hb/cyc3/cyc3_ciii52001.pdf)



- [18] LM96550 Data Sheet. Texas Instruments Inc., Texas. [Online] Available:  
<http://www.ti.com/lit/ds/symlink/lm96550.pdf>
- [19] EP3C10E144 Data Sheet. Altera Inc., California. [Online] Available:  
[http://www.altera.com/literature/hb/cyc3/cyc3\\_ciii52001.pdf](http://www.altera.com/literature/hb/cyc3/cyc3_ciii52001.pdf)
- [20] LM311 Data Sheet. Texas Instruments Inc., Texas. [Online] Available:  
<http://www.ti.com/lit/ds/symlink/lm311.pdf>

## Appendix A Design and Testing Supplements

### A.1 Transducer Probe

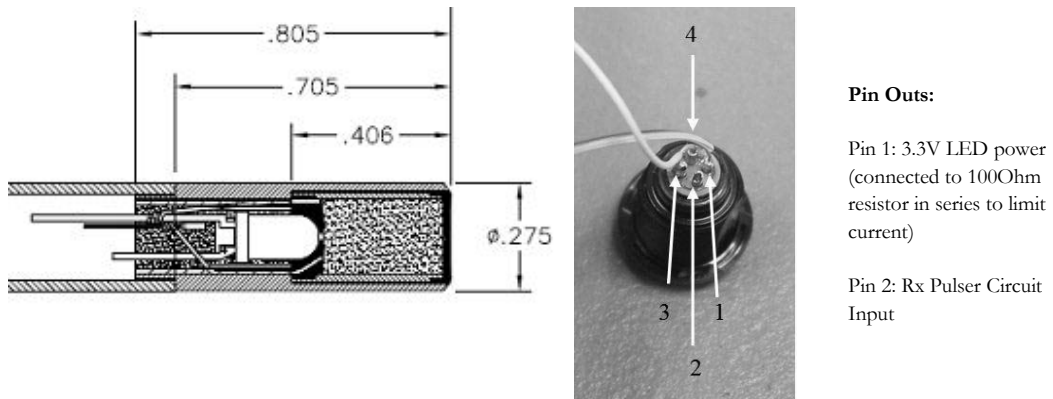


Figure 3. DGH Probe Dimensions and Pin-outs [7]

### A.2 T/R Switch

 


Figure 4. T/R Switch Pin Assignments

 


Figure 5. TX810 Breakout Board

### A.3 Transmit Pulser

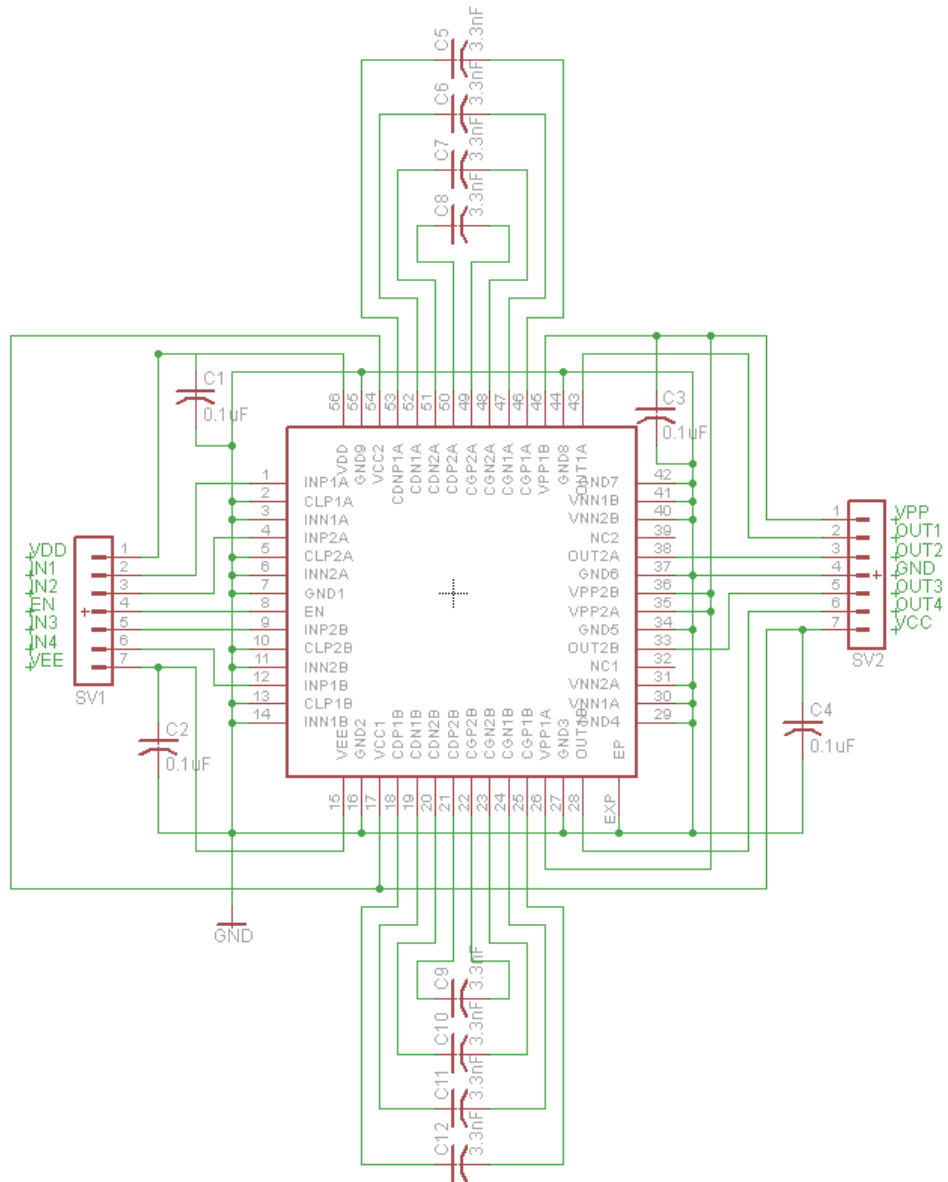


Figure 6. Transmit Pulser Pin Assignments

 


Figure 7. MAX4940 Breakout Board

## A.4 Analog Front End

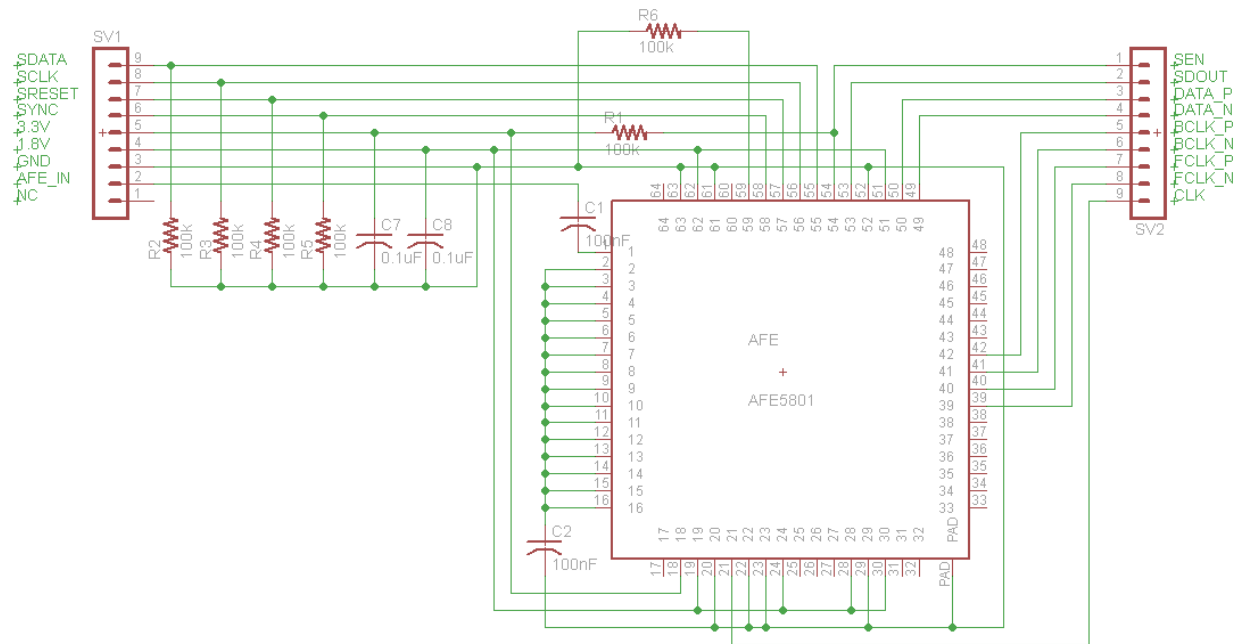


Figure 8. Analog Front End Pin Assignments



Figure 9. AFE5801 Breakout Board

Table 1. AFE Register Configuration

Address	Register Contents	Purpose
x01	23F8	1x Output Rate; External Reference; No Low Noise Suppression; Power Down Channels 1-7 Enable Output
x00	0004	Enable Write to TGC Registers
x99	0020	Enable Soft Sync Mode
x97	0000	Start Gain Level; Disable Interpolation
x95	0000	Establish Start Index
x96	001A	Establish Stop Index
x9B	001A	Set Uniform Gain Slope
x98	0059	Set Hold Gain Time

## A.5 FPGA

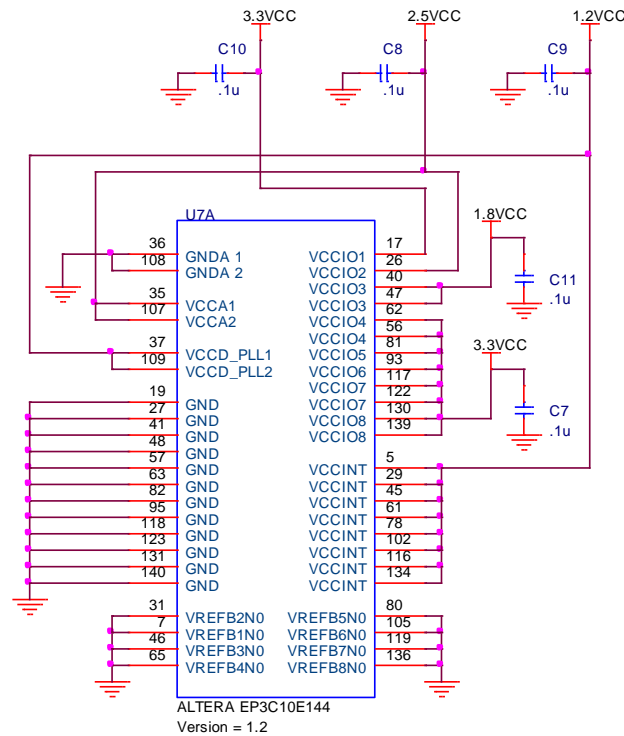


Figure 11. FPGA Power Pin Assignments


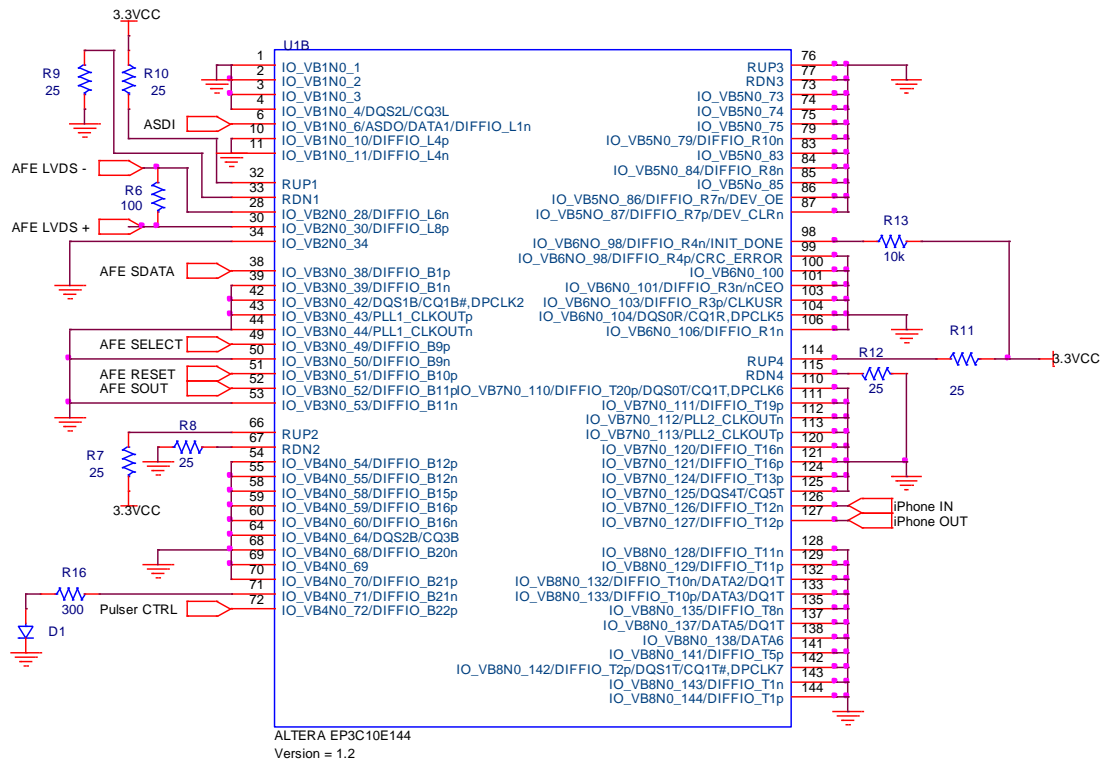



Figure 12. FPGA I/O Pin Assignments

 



**Figure 40. FPGA Printed Circuit Board**

## A.6 iPhone

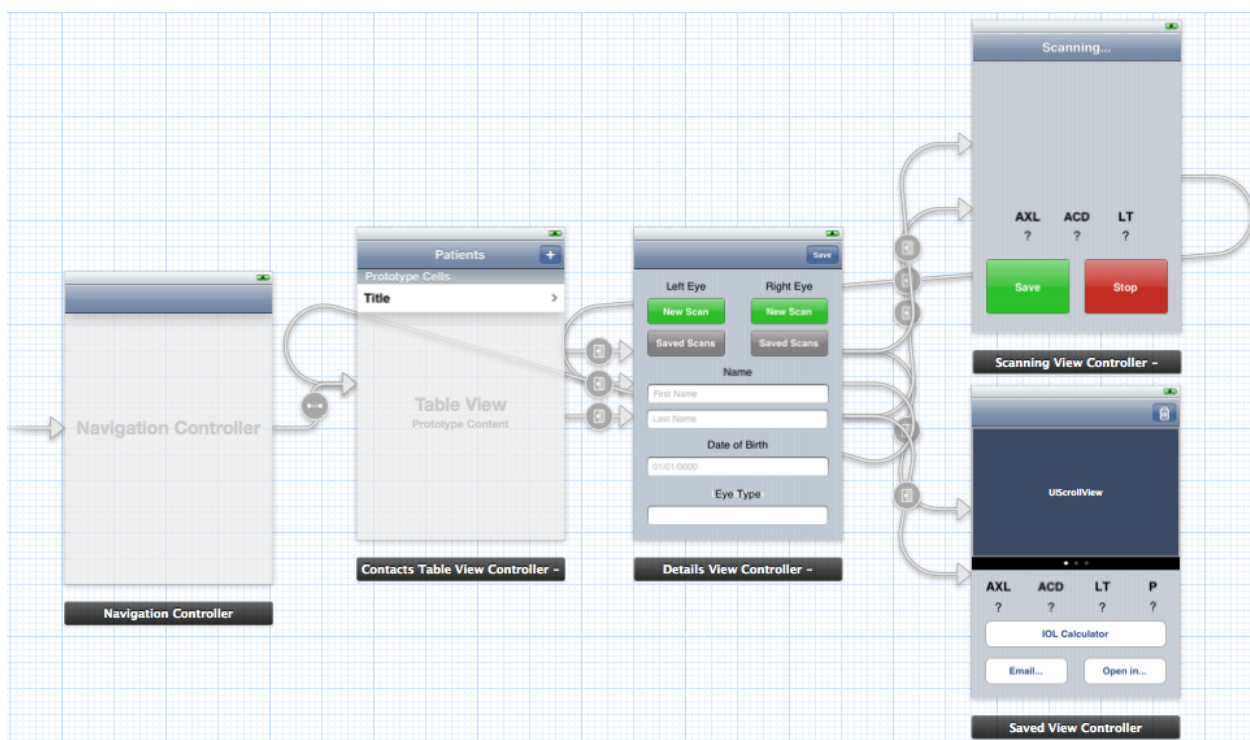


**Figure 19. iPhone Application Flow Diagram**

## A.7 Power Electronics

### A.7.1 Boost Converter

The regulation of +30V was achieved by configuring the TL497ACN as a boost converter. The schematic, provided by the IC's datasheet, is shown in Figure 21 below.

 

**Figure 21. Boost configuration of TL497ACN DC/DC converter [1]**

Calculations in determining appropriate values for the external components are provided below. Note that  $I_{(PK)}$  must be less than 500mA [1], and we expect no more than 50mA to be drawn by components downstream of this converter.

$$I_{(PK)} = 2I_{O(MAX)} \left( \frac{V_{O(MAX)}}{V_I} \right) = 2 \times 50 [mA] \times \left( \frac{31.5 [V]}{7 [V]} \right) = 450 [mA] \quad (12)$$

Since  $t_{ON}$  can be chosen between 25μs and 150μs, I choose  $t_{ON} = 25\mu s$ .

$$L = \frac{V_I}{I_{(PK)}} t_{ON} = \frac{7 [V]}{450 [mA]} \times 25 [\mu s] = 389 [\mu H] \quad (13)$$

Since the ECE Parts Shop does not carry inductors, I ordered a 390μH inductor with 10% tolerance and 0.74A rating (RLB9012-391KL).

$$C_T \cong 12t_{ON} = 300 [pF] \quad (14)$$

$$R_1 = (V_O - 1.2) [k\Omega] = 28.8 [k\Omega] \cong 30 [k\Omega] \quad (15)$$

$$R_{CL} = \frac{0.5 [V]}{I_{(PK)}} = 1.1 [\Omega] \quad (16)$$


Choose a ripple voltage of 250mV.

$$C_O = t_{ON} \frac{\left( \frac{V_{O(MAX)}}{V_I} I_{(PK)} + I_{O(MAX)} \right)}{V_{RIPPLE}} = 207.5 [\mu F] \cong 200 [\mu F] \quad (17)$$

### A.7.2 Buck Converters

The regulation of +5V and +1.8V were achieved by configuring the TL497ACN as a buck converter. The schematic, provided by the IC's datasheet, is shown in Figure 22 below.



 

**Figure 22. Buck configuration of TL497ACN DC/DC converter [1]**

Calculations in determining appropriate values for the external components of each converter are provided below. Note that  $I_{(PK)}$  must be less than 500mA [1]. We expect no more than 50mA to be drawn by components downstream of the +5V converter and no more than 225mA to be drawn by components downstream of the +1.8V converter.

**+5V buck converter:**

$$I_{(PK)} = 2I_{O(MAX)} = 100 [mA] \quad (18)$$

Since  $t_{ON}$  can be chosen between 10μs and 150μs, I choose  $t_{ON} = 20\mu s$ .

$$L = \frac{V_I - V_O}{I_{(PK)}} t_{ON} = \frac{7 [V] - 5 [V]}{100 [mA]} \times 20 [\mu s] = 400 [\mu H] \quad (19)$$

Since the ECE Parts Shop does not carry inductors, we ordered a 390μH inductor with 10% tolerance and 0.74A rating (RLB9012-391KL).

$$C_T \cong 12t_{ON} = 240 [pF] \quad (20)$$

$$R_1 = (V_O - 1.2) [k\Omega] = 3.8 [k\Omega] \cong 3.9 [k\Omega] \quad (21)$$

$$R_{CL} = \frac{0.5 [V]}{I_{(PK)}} = 5.1 [\Omega] \quad (22)$$

Choose a ripple voltage of 50mV.

$$C_O = t_{ON} \frac{\left( \frac{V_I - V_O}{V_O} I_{(PK)} + I_{O(MAX)} \right)}{V_{RIPPLE}} = 36 [\mu F] \cong 33 [\mu F] \quad (23)$$

**+1.8V buck converter:**

$$I_{(PK)} = 2I_{O(MAX)} = 450 [mA] \quad (24)$$

Since  $t_{ON}$  can be chosen between 10μs and 150μs, we choose  $t_{ON} = 25\mu s$ .

$$L = \frac{V_I - V_O}{I_{(PK)}} t_{ON} = \frac{7 [V] - 1.8 [V]}{450 [mA]} \times 25 [\mu s] = 289 [\mu H] \quad (25)$$

Since the ECE Parts Shop does not carry inductors, we ordered a 270 $\mu$ H inductor with 10% tolerance and 0.94A rating (RLB9012-271KL).

$$C_T \cong 12t_{ON} = 300 [pF] \quad (26)$$

$$R_1 = (V_O - 1.2) [k\Omega] = 0.6 [k\Omega] \cong 620 [\Omega] \quad (27)$$


$$R_{CL} = \frac{0.5 [V]}{I_{(PK)}} = 1.1 [\Omega] \quad (28)$$

Choose a ripple voltage of 25mV.

$$C_O = t_{ON} \frac{\left( \frac{V_I - V_O}{V_O} I_{(PK)} + I_{O(MAX)} \right)}{V_{RIPPLE}} = 953 [\mu F] \cong 1000 [\mu F] \quad (29)$$

### A.7.3 Inverting Converter

The regulation of -10V was achieved by configuring the TL497ACN as an inverting converter. The schematic, provided by the IC's datasheet, is shown in Figure 23 below.

 

**Figure 23. Inverting configuration of TL497ACN DC/DC converter [1]**

Calculations in determining appropriate values for the external components of the converter are provided below. Note that  $I_{(PK)}$  must be less than 500mA [1]. We expect no more than 50mA to be drawn by components downstream of this converter.

$$I_{(PK)} = 2I_{O(MAX)} \left( 1 + \frac{|V_O|}{V_I} \right) = 2 \times 50 [mA] \times \left( 1 + \frac{10 [V]}{7 [V]} \right) = 243 [mA] \quad (30)$$

Since  $t_{ON}$  can be chosen between 25 $\mu$ s and 150 $\mu$ s, we choose  $t_{ON} = 50\mu$ s.

$$L = \frac{V_I}{I_{(PK)}} t_{ON} = \frac{7 [V]}{243 [mA]} \times 50 [\mu s] = 144 [\mu H] \cong 150 [\mu H] \quad (31)$$

Since the ECE Parts Shop does not carry inductors, we ordered a 150 $\mu$ H inductor with 10% tolerance and 1.15A rating (RLB9012-151KL).

$$C_T \cong 12t_{ON} = 600 [pF] \cong 560 [pF] \quad (32)$$

$$R_1 = (V_O - 1.2) [k\Omega] = 8.8 [k\Omega] \cong 9.1 [k\Omega] \quad (33)$$

$$R_{CL} = \frac{0.5 [V]}{I_{(PK)}} = 2.1 [\Omega] \cong 2.0 [\Omega] \quad (34)$$

Choose a ripple voltage of 50mV.

$$C_O = t_{ON} \frac{\left( \frac{V_L}{|V_O|} I_{(PK)} + I_{O(MAX)} \right)}{V_{RIPPLE}} = 220 [\mu F] \quad (35)$$

Choose rectifier to be a standard 1N4002 diode.

#### A.7.4 Voltage Regulators

The regulation of +10V, +3.3V, +2.5V, +1.2V, and -5V were achieved by employing fixed voltage regulators onto their respective source converter's output. Figure 24 below shows the regulators connected to their respective DC/DC converters with appropriate input and output decoupling capacitors.

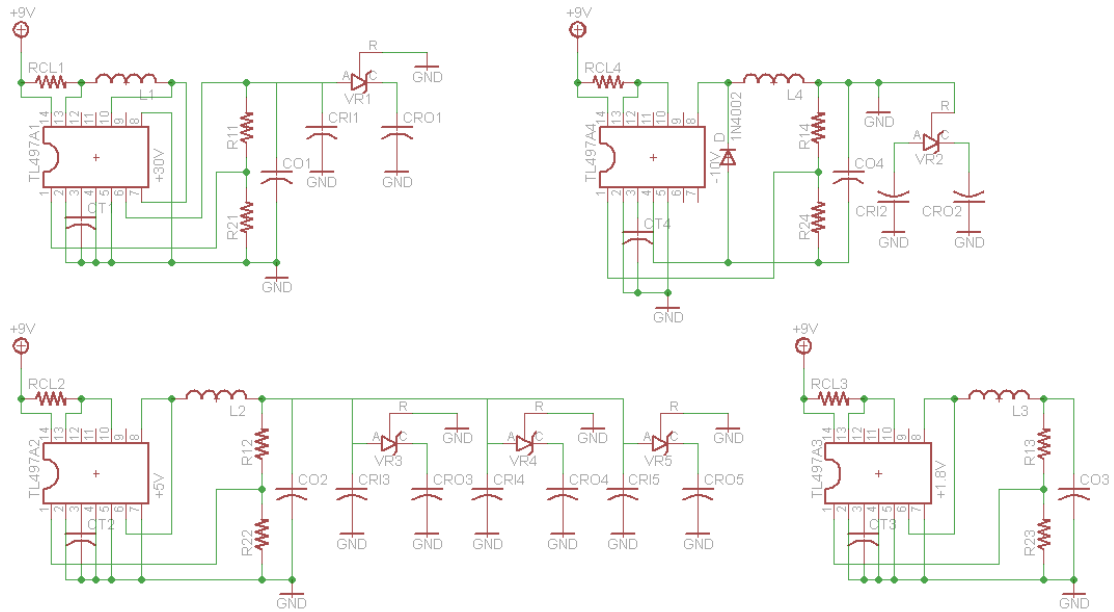


Figure 24. Power Electronics Schematic including Voltage Regulators

## Appendix B Table 6. Requirement and Verification Table

Probe Requirements	Verification	Verified?
1. Fixation LED must light up. a. LED must draw 16mA or less from 3.3V Power Electronics b. Probe must be attached to circuit ground	1. Observe that the Fixation LED lights up a. A current draw of 16mA or less is measured across the 100Ohm series resistor. b. The probe nodes are correctly connected to 3.3V and ground	YES
2. Transducer must convert 30V pulse input into sound wave oscillating at 9.5-10.5 MHz	2. Use pulse generator to drive transducer using a 30V, 10MHz input pulse. Observe return echo voltage signal on an oscilloscope, noting their peak amplitude values and a nominal frequency of 9.5-10.5 MHz.	YES
3. Transducer must convert return echo sound waves to voltage signal.	3. Use pulse generator to drive transducer using a 30V, 10MHz input pulse. Observe return echo voltage signal on an oscilloscope, noting their peak amplitude values and the nominal frequency.	YES
<i>Contingency Plan: Temporarily use Storz probe until DGH Technologies can be contacted for a replacement ultrasound probe.</i>		

T/R Switch Requirements	Verification	Verified?
1. Diode Bridge and Voltage Clamp must prevent high voltage input spikes (greater than 2 Vpp) to leak to the output.	1. Apply 30V pulse to the input end of Measure output voltage on DMM. Verify that the output signal does not exceed 2 Vpp.	YES
<i>Contingency Plan: Replace malfunctioning TX810 chip with spare TX810 Chip</i>		

AFE Requirements	Verification	Verified?
1. Input SPI data on SDATA bus must have: a. a logic level high voltage between 1.4-3.6V b. a logic level low voltage of less than 0.8V	1. Use a logic analyzer to observe data communications on the SPI bus. Verify logic levels are: a. between 1.4-3.6V for a high data bit b. less than 0.8V for a low data bit	YES
2. SDATA must correctly latch on the rising edge of SCLK.	2. Use a logic analyzer to observe data communications on the SPI bus. Verify SDATA bits correctly latch on the rising edge of SCLK.	YES
3. Output LVDS signal should have a common mode output voltage of 0.9-1.5V	3. Measure output voltage at nodes D1P and D1M on a DMM. Voltage output should read between 0.9-1.5V.	YES
4. Output LVDS signal should maintain a data rate of between 25-35 MSPS .	4. Use a digital waveform analyzer to observe data communications on the LVDS bus. Verify data rate of between 25-35 MSPS.	YES
<i>Contingency Plan: Replace malfunctioning AFE5801 chip with spare AFE5801 Chip.</i>		

FGPA Requirements	Verification	Verified?
1. Clock must operate properly a. 30 MHz frequency $\pm 1\%$ b. $3.3V_{pp} \pm 5\%$	1. Connect oscillator pins to Vcc and GND. Probe clock output with oscilloscope. a. A clock frequency of 30 MHz frequency $\pm 1\%$ is measured at the clock output b. Clock logic level of $3.3V_{pp} \pm 5\%$ is measured at the clock output.	YES
2. Serial Programmer must program FPGA correctly with Active Serial (AS) programming.	2. Connect USB Blaster cable to board using 10pin connector. Use Quartus II software to load a sample program onto FPGA using AS programming. Quartus II loads the program successfully with no errors.	YES
3. FPGA must receive and buffer incoming AFE data correctly.	3. Implement test RAM array (8x12bit) on FPGA. Send eight 12bit frames of known test data over LVDS protocol at 360MSPS into RAM. Memory array is read out correctly in 1bit increments to the FPGA's LED.	NO
4. FPGA must correctly interpret Manchester encoded command signals sent at 8820 baud rate or higher. c. FPGA LED is turned on when x01 is received. d. FPGA LED is turned off when x02 is received.	4. Setup signal generator to make Manchester encoded bytes of x01 and x02 using an AC signal of 8820 baud and $2.76V_{pp}$ . a. LED turns on when x01 is sent from signal generator. b. LED turns off when x02 is sent from signal generator.	YES
5. FPGA must correctly send Manchester encoded data at 8820 baud rate or higher. a. DC offset of sent signal is within $\pm 0.5mV$ . b. $V_{pp}$ of sent signal is between 1mV and 2mV. c. Data is correctly encoded.	5. Connect oscilloscope to FPGA signal output. Send a known Manchester encoded byte using a digital signal at 8820 baud repeatedly once per second from the FPGA. Repeat this verification for several known bytes. a. DC offset of sent signal is measured on oscilloscope to be within $\pm 0.5mV$ . b. $V_{pp}$ of sent signal is measured on oscilloscope to be between 1mV and 2mV. c. Data byte waveform seen on oscilloscope is correct Manchester encoded byte.	YES
6. FPGA must correctly send digital pulses to the Pulser CTRL line. a. $V_p$ of pulse is $3V \pm 5\%$ . b. Pulse width is $50ns \pm 1\%$ .	6. Connect oscilloscope to Pulser CTRL signal output. Send pulse signal from FPGA repeatedly at a frequency of 1Hz. a. $V_p$ of pulse measured with oscilloscope is $3V \pm 5\%$ . b. Pulse width measured with oscilloscope is $50ns \pm 1\%$ .	YES
<i>Contingency Plan: Use Altera DE2 Board instead of Cyclone III board.</i>		

Transmit Pulser Requirements	Verification	Verified?
1. The Vout0 node transmits a nominal +30V, 50ns-wide pulse upon receiving a 50ns-wide digital pulse on its Pin0 node.	1. Using a pulse generator, send a 50ns-wide pulse of +3.3V amplitude to Pin0. Verify that a +30V, 50ns-wide pulse is instantaneously transmitted from Vout0.	YES
<i>Contingency Plan: Replace malfunctioning Transmit Pulser, or use a different Transmit Pulser (TX734).</i>		

Power Electronics Requirements	Verification	Verified?
1. <ul style="list-style-type: none"> <li>a. 9V lithium battery must provide a voltage between +6.5V and +9.5V</li> <li>b. Battery must be connected to the 30V boost converter</li> <li>c. Battery must be connected to the 5V buck converter</li> <li>d. Battery must be connected to the 1.8V buck converter</li> <li>e. Battery must be connected to the -10V inverting converter</li> </ul>	1. <ul style="list-style-type: none"> <li>a. A voltage between +6.5V and +9.5V is measured across the battery's terminals.</li> <li>b. A voltage between +6.5V and +9.5V is measured at the input node of the 30V boost converter.</li> <li>c. A voltage between +6.5V and +9.5V is measured at the input node of the 5V buck converter.</li> <li>d. A voltage between +6.5V and +9.5V is measured at the input node of the 1.8V buck converter.</li> <li>e. A voltage between +6.5V and +9.5V is measured at the input node of the -10V inverting converter.</li> </ul>	YES
2. <ul style="list-style-type: none"> <li>a. The output node of the 30V boost converter must regulate a nominal voltage of +30V, within a tolerance of <math>\pm 5\%</math></li> <li>b. Boost converter must be connected to the Transmit Pulser</li> <li>c. Boost converter must be connected to the 10V LDO Regulator</li> </ul>	2. <ul style="list-style-type: none"> <li>a. A voltage between +28.5V and +31.5V is measured at the output node of the 30V boost converter.</li> <li>b. A voltage between +28.5V and +31.5V is measured at the VPP nodes of the Transmit Pulser.</li> <li>c. A voltage between +28.5V and +31.5V is measured at the input node of the 10V LDO Regulator.</li> </ul>	YES
3. <ul style="list-style-type: none"> <li>a. The output node of the 5V buck converter must regulate a nominal voltage of +5V, within a tolerance of <math>\pm 5\%</math></li> <li>b. Buck converter must be connected to the T/R Switch</li> <li>c. Buck converter must be connected to the 3.3V LDO Regulator</li> <li>d. Buck converter must be connected to the 2.5V LDO Regulator</li> <li>e. Buck converter must be connected to the 1.2V LDO Regulator</li> </ul>	3. <ul style="list-style-type: none"> <li>a. A voltage between +4.75V and +5.25V is measured at the output node of the 5V buck converter.</li> <li>b. A voltage between +4.75V and +5.25V is measured at the VP node of the T/R Switch.</li> <li>c. A voltage between +4.75V and +5.25V is measured at the input node of the 3.3V LDO Regulator.</li> <li>d. A voltage between +4.75V and +5.25V is measured at the input node of the 2.5V LDO Regulator.</li> </ul>	YES

	e. A voltage between +4.75V and +5.25V is measured at the input node of the 1.2V LDO Regulator.	
4. a. The output node of the 1.8V buck converter must regulate a nominal voltage of +1.8V, within a tolerance of $\pm 5\%$ b. Buck converter must be connected to the AFE c. Buck converter must be connected to the FPGA	4. a. A voltage between +1.71V and +1.89V is measured at the output node of the 1.8V buck converter. b. A voltage between +1.71V and +1.89V is measured at the AVDD18 and DVDD18 nodes of the AFE. c. A voltage between +1.71V and +1.89V is measured at the VCCIO3 node of the FPGA.	YES
5. a. The output node of the -10V inverting converter must regulate a nominal voltage of -10V, within a tolerance of $\pm 5\%$ b. Inverting converter is connected to the Transmit Pulser	5. a. A voltage between -9.5V and -10.5V is measured at the output node of the -10V inverting converter. b. A voltage between -9.5V and -10.5V is measured at the VPF, VDN, and VSUB nodes of the Transmit Pulser.	YES
6. a. The output node of the 10V LDO Regulator must regulate a nominal voltage of +10V, within a tolerance of $\pm 5\%$ b. LDO Regulator is connected to the Transmit Pulser	6. a. A voltage between +9.5V and +10.5V is measured at the output node of the 10V LDO Regulator. b. A voltage between +9.5V and +10.5V is measured at the VNF and VDD nodes of the Transmit Pulser.	YES
7. a. The output node of the 3.3V LDO Regulator must regulate a nominal voltage of +3.3V, within a tolerance of $\pm 5\%$ b. LDO Regulator must be connected to the FPGA c. LDO Regulator must be connected to the AFE d. LDO Regulator must be connected to the T/R Switch e. LDO Regulator must be connected to the Transmit Pulser	7. a. A voltage between +3.135V and +3.465V is measured at the output node of the 3.3V LDO Regulator. b. A voltage between +3.135V and +3.465V is measured at the VCCIO1, VCCIO4, VCCIO5, VCCIO6, VCCIO7, VCCIO8, RUP1, RUP2, and RUP4 nodes of the FPGA. c. A voltage between +3.135V and +3.465V is measured at the AVDD node of the AFE. d. A voltage between +3.135V and +3.465V is measured at the VD node of the T/R Switch. e. A voltage between +3.135V and +3.465V is measured at the VLL, EN, and MODE nodes of the Transmit Pulser.	YES
8. a. The output node of the 2.5V	8. a. A voltage between +2.375V and	YES

<p>LDO Regulator must regulate a nominal voltage of +2.5V, within a tolerance of <math>\pm 5\%</math></p> <p>b. LDO Regulator must be connected to the FPGA</p>	<p>+2.625V is measured at the output node of the 2.5V LDO Regulator.</p> <p>b. A voltage between +2.375V and +2.625V is measured at the VCCIO2, VCCA1, VCCA2 nodes of the FPGA.</p>	
<p>9.</p> <p>a. The output node of the 1.2V LDO Regulator must regulate a nominal voltage of +1.2V, within a tolerance of <math>\pm 5\%</math></p> <p>b. LDO Regulator must be connected to the FPGA</p>	<p>9.</p> <p>a. A voltage between +1.14V and +1.26V is measured at the output node of the 2.5V LDO Regulator.</p> <p>b. A voltage between +1.14V and +1.26V is measured at the VCCINT, VCC_PLL1, and VCC_PLL2 nodes of the FPGA.</p>	YES
<p>10.</p> <p>a. The output node of the -5V Negative Regulator must regulate a nominal voltage of -5V, within a tolerance of <math>\pm 5\%</math></p> <p>b. Negative Regulator must be connected to the T/R Switch</p> <p>c. Negative Regulator must be connected to the Transmit Pulser</p>	<p>10.</p> <p>a. A voltage between -4.75V and -5.25V is measured at the output node of the -5V Negative Regulator.</p> <p>b. A voltage between -4.75V and -5.25V is measured at the VN node of the T/R Switch.</p> <p>c. A voltage between -4.75V and -5.25V is measured at the VNN node of the Transmit Pulser.</p>	YES
<p><i>Contingency Plan #1: Replace malfunctioning power electronics IC.</i></p> <p><i>Contingency Plan #2: Choose a different power electronics IC.</i></p> <p><i>Contingency Plan #3: If a DC/DC converter continues to fail, choose to use a regulator instead; if a regulator continues to fail, choose to use a DC/DC converter instead.</i></p>		

iPhone 4S Requirements	Verification	Verified?
1. Device must be charged above 50%.	1. Go to iPhone settings and turn on battery percentage under General->Usage. Verify percentage is above 50%. If not, charge device.	YES
2. iPhone must correctly interpret Manchester encoded data received at 8820 baud rate or higher.	2. Setup signal generator to make a Manchester encoded byte of xA9 using an AC signal of 8820 baud and 1.5mV <sub>pp</sub> with 0V DC offset. Connect the signal generator to the iPhone's microphone input. The iPhone will correctly display xA9 to the screen.	YES
3. iPhone must correctly send Manchester encoded command signals at 8820 baud rate or higher. <p>a. DC offset of sent signal is within <math>\pm 0.5\text{mV}</math>.</p> <p>b. V<sub>pp</sub> of sent signal is 2.76V<sub>pp</sub> <math>\pm 5\%</math>.</p> <p>c. Data is correctly encoded.</p>	3. Connect oscilloscope to iPhone left audio output. Turn iPhone volume to 100%. Send x01 using Manchester encoding from the iPhone at 8820 baud at a frequency of 1Hz. <p>a. DC offset of sent signal is measured on oscilloscope to be within <math>\pm 0.5\text{mV}</math>.</p> <p>b. V<sub>pp</sub> of sent signal is measured on oscilloscope to be 2.76V<sub>pp</sub> <math>\pm 5\%</math>.</p>	YES



	c. Data byte waveform seen on oscilloscope is the correct Manchester encoded byte.	
4. User interface should handle user inputs correctly. a. Start scan b. Stop scan c. Save scan d. Email scan e. MMS scan f. Change sound velocity	4. Navigate between user interface views to access various commands. a. Pressing “start scan” switches to view 4. b. Pressing “stop scan” switches to view 3. c. Pressing “save scan” saves the last scan to the iPhone camera roll. d. Pressing “email scan” switches to compose email view with scan image attached. e. Pressing “MMS scan” switches to MMS view with scan image attached. f. Pressing “change sound velocity” allows the user to manually enter a value for sound velocity which changes subsequent scan data.	YES
<i>Contingency Plan: Use an Android phone.</i>		

Overall AEL Measurement Requirements	Verification	Verified?
1. Upon performing an A-scan with our device, calculated depths should be within 0.1mm of the actual thickness.	1. Two polystyrene test blocks will be used to verify the accuracy of our device. Each will be of known thickness (measured with digital calipers). One will have a thickness equal to a typical anterior chamber depth. The other will have a thickness equal to a typical axial eye length. These correspond to the smallest and largest length measurements to be calculated. The percent difference between expected values and measurements when performed in a sequential experiment should be minimal (<6.7% or within $3\sigma$ ).	YES
2. AEL Measurements must be performed on tissues similar to structures in the human eye.	2. AEL measurements will be taken on sample animal eyeballs procured from the Meat Sciences Laboratory or the College of Veterinary Medicine. Compare animal AEL lengths with known values for animal and human.	YES