Seven identical resistors ( $R = 10 \Omega$ ) are connected to a battery (E = 13 V) as shown in the figure.



1) The resistors  $R_5$  and  $R_7$  are in

- a. neither series nor parallel.
- b. series.
- c. parallel.
- 2) What is the current through the battery?
  - a. *I* <sub>battery</sub> = 0.186 A b. *I* <sub>battery</sub> = 2.6 A c. *I* <sub>battery</sub> = 1.3 A
- 3) What is the power dissipated by resistor  $R_6$ ?
  - a.  $P_{6}$ = 16.9 J/s b.  $P_{6}$ = 1.88 J/s c.  $P_{6}$ = 5.63 J/s
- 4) What is the voltage across resistor  $R_4$ ?

a.  $V_4 = 4.33$  V b.  $V_4 = 8.67$  V c.  $V_4 = 6.5$  V

Three resistors ( $R_1 = 10 \Omega$ ,  $R_2 = 15 \Omega$ ,  $R_3 = 25 \Omega$ ) are connected to two batteries ( $E_1$  is unknown,  $E_2 = 13 \text{ V}$ ) as shown in the figure.



5) The resistors  $R_2$  and  $R_3$  are in

a. series.

b. parallel.

c. neither series nor parallel.

- 6) Which of the following equations is NOT correct:
  - a.  $I_1 R_1 + E_1 = 0$ b.  $-I_3 R_3 + E_1 - E_2 = 0$ c.  $-I_3 R_3 + I_1 R_1 - E_2 = 0$ d.  $-I_2 R_2 - E_1 = 0$ e.  $-I_3 R_3 - I_2 R_2 - E_2 = 0$
- 7) The current  $I_3$  through resistor  $R_3$  is measured to be 0.48 amps, in the direction shown by the arrow. What is the voltage across battery  $E_1$ ?
  - a.  $E_1 = 13$  V b.  $E_1 = 25$  V c.  $E_1 = 1$  V
- 8) Now battery  $E_1$  is replaced by a battery with voltage 13 V. What is  $I_2$  the current through resistor  $R_2$  with this new battery in place?

a.  $I_2 = -0.867$  A b.  $I_2 = 0.325$  A c.  $I_2 = -1.19$  A

A circuit is composed of a battery with voltage V, a resistor R, two capacitors,  $C_1$  and  $C_2$ , and two switches,  $S_1$  and  $S_2$ , as shown. Initially the capacitors are uncharged and the switches are both open. At time t = 0,  $S_1$  is closed.



9) At t = 0, what is the voltage,  $V_{C1}$ , the voltage across capacitor  $C_1$ ?

- a.  $V_{C1} = VC_1 / (C_1 + C_2)$ b.  $V_{C1} = 0$ c.  $V_{C1} = V$
- 10) What is the charge,  $Q_{C2}$ , on capacitor  $C_2$  at time  $t = RC_{eff}$  where  $C_{eff}$  is the effective capacitance of the combination of  $C_1$  and  $C_2$ .

a. 
$$Q_{C2} = (1 - e^{-1}) VC_2$$
  
b.  $Q_{C2} = e^{-1}VC_1C_2 / (C_1 + C_2)$   
c.  $Q_{C2} = (e^{-1}VC_2)$   
d.  $Q_{C2} = e^{-1}VC_2 / (C_1 + C_2)$   
e.  $Q_{C2} = (1 - e^{-1}) VC_1C_2 / (C_1 + C_2)$ 

11) After a long time,  $t > RC_{\text{eff}}$ ,  $S_1$  is opened and then, at  $t=t_2S_2$  is closed. What is the magnitude of the current,  $|I_R|$ , through the resistor immediately after switch  $S_2$  is closed?

a.  $|I_R| = V/R$ b.  $|I_R| = (1 - e^{-1})V/R$ c.  $|I_R| = VC_2/(R(C_1 + C_2))$ d.  $|I_R| = VC_1/(R(C_1 + C_2))$ e.  $|I_R| = e^{-1}V/R$ 

A charged particle, initially at rest at point a, is accelerated through a potential difference, V, between points a and b. The particle enters a uniform magnetic field, B, directed perpendicular to the plane of the page. While in this magnetic field, the particle travels in a semicircle of diameter d.



12) What is the direction of the magnetic field?

- a. Not enough information to determine.
- b. Into the page.
- c. Out of the page.
- 13) If the experiment is repeated with another particle e that has the same charge, but twice the mass, how would *d* change?
  - a. *d* would increase by √2.
    b. *d* would double.
    c. *d* would be the same.
- 14) Let *T* be the amount of time the particle is in the shaded region that contains the magnetic field. If we double *V* (keeping the charge, the mass of the particle, and the magnetic field unchanged), what will happen to *T*?
  - a. d will double.
  - b. *T* will stay the same.
  - c. T will increase by  $\sqrt{2}$ .

An infinite current sheet is composed of an infinite array of small wires with spacing a = 0.35 cm, each carrying current I = 3 A out of the page, as shown in the figure. For this problem you may assume that  $d \gg a$  so that you may treat the array of wires as a continuous sheet of current.



15) At the point labelled A, the magnetic field points

a. into the page.b. out of the page.c. to the left

16) The magnitude of the field,  $|\mathbf{B}|$ , at point A, a distance d = 40 cm from the current sheet is

- a.  $|\mathbf{B}| = 1.71 \times 10^{-4} \text{ T}$ b.  $|\mathbf{B}| = 9.42 \times 10^{-6} \text{ T}$ c.  $|\mathbf{B}| = 0.00108 \text{ T}$ d.  $|\mathbf{B}| = 5.39 \times 10^{-4} \text{ T}$ e.  $|\mathbf{B}| = 1.5 \times 10^{-6} \text{ T}$
- 17) If the array of wires has a thickness b = 0.088 cm, what is the average current density, J, of this current sheet?

a.  $J = 3.87 \times 10^{6} \text{ A/m}^{2}$ b.  $J = 9.74 \times 10^{5} \text{ A/m}^{2}$ c.  $J = 85700 \text{ A/m}^{2}$ 

A square current loop, with sides L = 0.15 m, carries a current I = 0.6 A, flowing in the direction shown. The loop is in a uniform 0.3 T magnetic field, **B**, that points along the *y*-axis. The loop can pivot without friction about the *z*-axis, as shown. The view along *z* defines the rotation angle,  $\theta$ . When the loop lies in the *x*-*z* plane (as in the left diagram),  $\theta=0$ .



18) For which orientations is the magnitude of the torque exerted on the loop by the magnetic field a maximum?

a.  $\theta = 90^{\circ}$ , 270° b.  $\theta = 0^{\circ}$ , 180° c.  $\theta = 45^{\circ}$ , 135°

19) What is the *z* component of the torque on the loop when  $\theta = 120^{\circ}$ ?

a.  $\tau_z = -0.00351$  Nm b.  $\tau_z = -0.00405$  Nm c.  $\tau_z = 0.00405$  Nm d.  $\tau_z = 0.00203$  Nm e.  $\tau_z = -0.00203$  Nm

20) At what orientation is the potential energy of the loop a minimum?

a.  $\theta = 90^{\circ}$ b.  $\theta = 0^{\circ}$ c.  $\theta = 180^{\circ}$ 

Copper wire with resistivity  $\rho = 1.68 \times 10^{-8} \Omega m$ , and cross sectional area A =  $7.85 \times 10^{-5} m^2$  is formed into a circular loop of radius r = 0.3 m. The loop is rotating about the y axis with a constant angular velocity  $\omega$  in a uniform magnetic field *B* pointing in the positive z direction as shown in the figure.



21) What is the resistance of the loop?

- a.  $R = 4.03 \times 10^{-4} \Omega$ b.  $R = 8.91 \times 10^{-9} \Omega$ c.  $R = 1.93 \times 10^{-5} \Omega$
- 22) At the instant shown in the figure (loop is flat in the *xy* plane), the magnitude of the induced emf around the loop is

# a. zero.b. a maximum.

- 23) As the loop continues to rotate (right side coming out of the page (+z), and left side going into the page (-z) the direction of the induced current is
  - a. counter clockwiseb. clockwise
- 24) A second loop with twice the radius of the first is created from the same type of copper wire and rotated with the same angular velocity  $\omega$ . Compare  $I_1$  the maximum current induced in the original loop, with  $I_2$ , the maximum current induced in the new loop.
  - a.  $I_2 = 4I_1$ b.  $I_2 = I_1$ c.  $I_2 = 2I_1$

A solid cylindrical conductor of radius R has a current I flowing into the page as shown in the figure.



25) What is the magnetic field  $\vec{B}$  at the point  $a\hat{y}$  with 0 < a < R (i.e. inside the conductor, directly above the center)?

a. 
$$\vec{B} = rac{\mu_0 I}{2\pi a} \hat{y}$$
  
b.  $\vec{B} = -rac{\mu_0 I}{2\pi a} \hat{y}$   
c.  $\vec{B} = rac{\mu_0 I}{2\pi a} \hat{x}$   
d.  $\vec{B} = rac{\mu_0 I a}{2\pi R^2} \hat{y}$   
e.  $\vec{B} = rac{\mu_0 I a}{2\pi R^2} \hat{x}$ 

26) What is the magnetic field  $\vec{B}$  at the point  $b\hat{x}$  with b > R (e.g. outside the conductor, directly to the right of the center)?

a. 
$$\vec{B} = -\frac{\mu_0 I}{2\pi b}\hat{y}$$
  
b.  $\vec{B} = -\frac{\mu_0 I}{2\pi b}\hat{x}$   
c.  $\vec{B} = \frac{\mu_0 I}{2\pi b}\hat{y}$ 

27) A wire carrying current *I*, <u>out of the page</u> is now placed directly above the conducting cylinder at position (x,y) = (0,2b). The magnitude of the magnetic field at the center of the conductor  $|\vec{B}_{0,0}|$  is

a. 
$$|\vec{B}_{0,0}| = \frac{\mu_0 I}{4\pi b} - \frac{\mu_0 I}{2\pi R}$$
  
b.  $|\vec{B}_{0,0}| = 0$   
c.  $|\vec{B}_{0,0}| = \frac{\mu_0 I}{4\pi b}$