1. Sketch the incremental model and compute an expression for incremental gain, $A_V = \frac{v_{out}}{v_{in}}$ for the circuits shown below. You may assume all the transistors are biased in saturation, and $g_m r_{ds} \gg 1$ but $r_{ds} \neq \infty$.

